

Razavi: Basic Circuit Theory I


Linyang Lee

Outline

- Electric Quantities/Devices
- Circuit Laws
- Analytic Techniques
- Circuit Theorems
- RL , RC , RLC
- Op-Amps


Electric Quantities

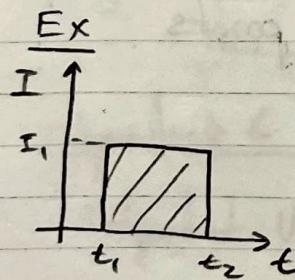- Charge (Q) (coulombs)
- Current occurs when charge moves
- $I = \frac{dQ}{dt}$
 - ① Current has value & direction
 - ② Open circuit $\rightarrow I = 0$
 - ③ $Q = \int_{t_1}^{t_2} I dt$ between times t_1, t_2




$$Q = \int_{t_1}^{t_2} I_1 dt = (t_2 - t_1) I_1$$

Circuit that creates this current.

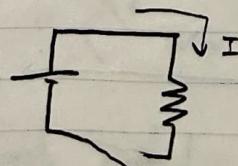


close switch @ t_1 , open @ t_2 .

- Voltage (V)

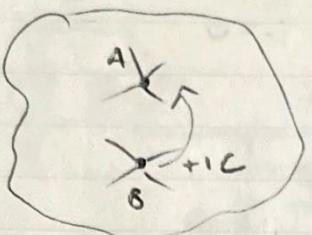

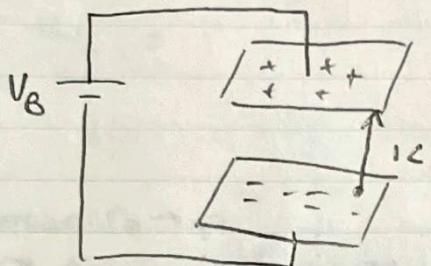$V_A - V_B =$ the amount of energy necessary to take a positive unit of charge from B to A.



$V_B =$ Energy needed to bring charge from lower plate to upper plate


Important points

- ① A voltage has a value & a sign.



$$\begin{matrix} \frac{1}{2}v_1 \\ - \end{matrix} \quad \begin{matrix} \frac{1}{2}v_2 \\ + \end{matrix}$$

- ② Voltage is meaningful only between two points

- ③ A short circuit guarantees $V=0$.

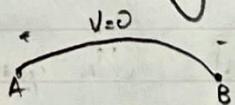


Ex

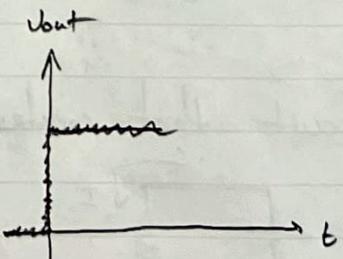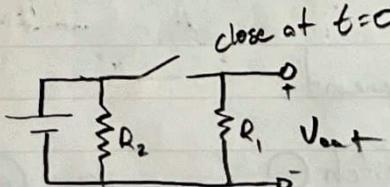



No change when R_c added.

Electric Devices

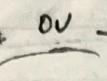- wire  ideal $\Rightarrow R=0, C=0, L=0$

$$V = IR$$

- switch

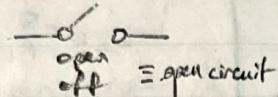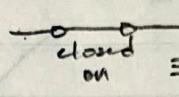  \equiv short circuit

- voltage source



$$V_s \phi_+ \frac{1}{T} \phi_-$$

constant w/ time

Defn.

A two-terminal device whose voltage does not depend on the current through it

Example

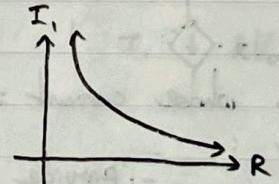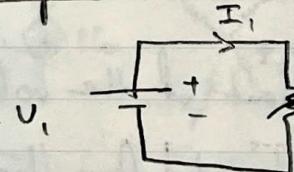


Independent & Dependent Voltage Sources








- Independent Voltage source - independent of other quantities in the circuit

- Dependent Voltage source - depends on other quantity in circuit

e.g.

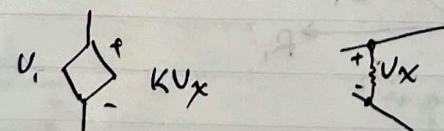

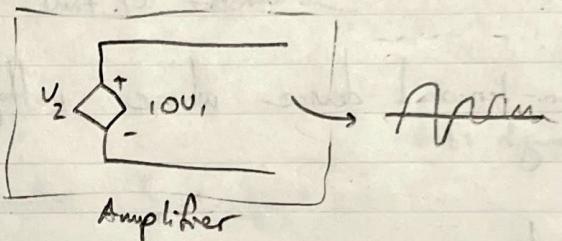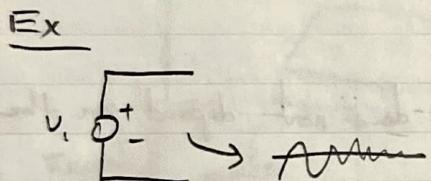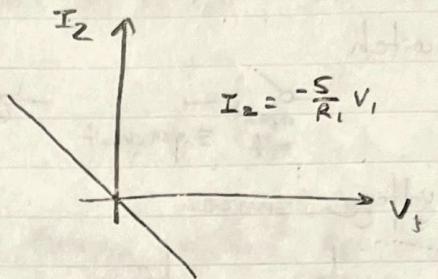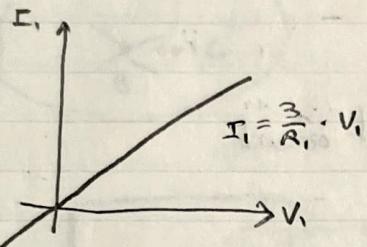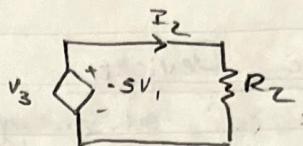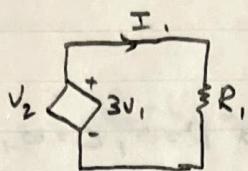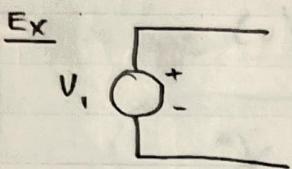good model for complex circuits. (e.g. amplifiers)





Current Source

- A 2 terminal device whose current is independent of the voltage across it




- provide a good model for other devices such as transistors.

Example

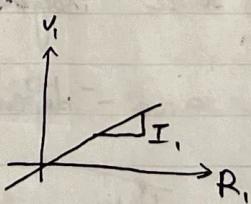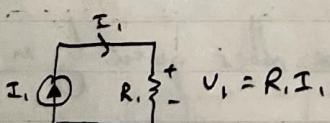

Example


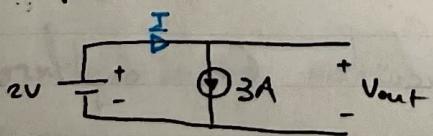


$$V_{out} = 2 \text{ V.}$$

$$I = 3 \text{ A}$$


Example

How do we charge a battery?

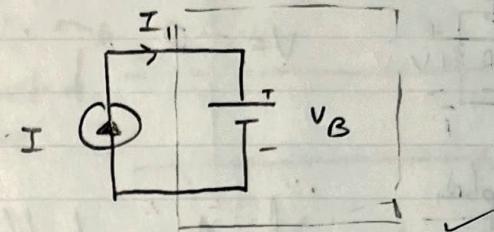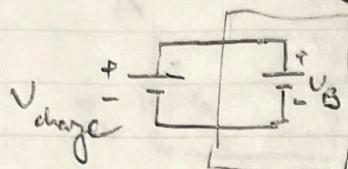


I is very large "

Example

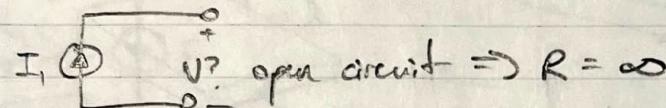


$V = I_s R \rightarrow \infty$ open current source " bad

Dependent Current Sources


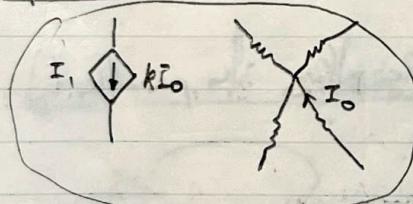


Multiple of current

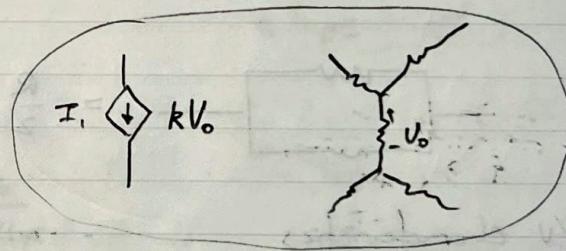

Dependent on voltage


Example

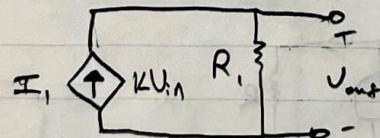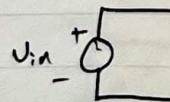


$$V_{out} = R_1 (K V_{in})$$

Acts as amplifier


Example

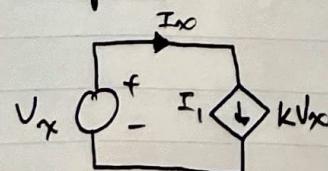


$$I_x = K V_x$$

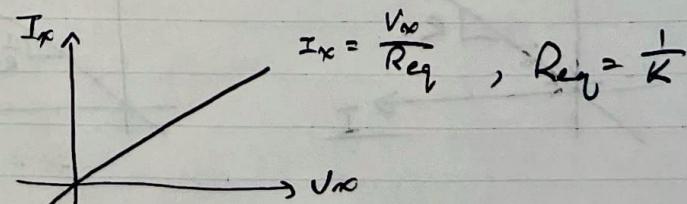

Resistors & Ohm's Law

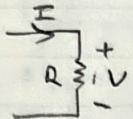


$$V = IR$$

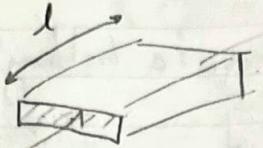


$$R = \frac{\rho l}{A} \quad \text{resistivity } \rho$$

Example


what happens if A is doubled?

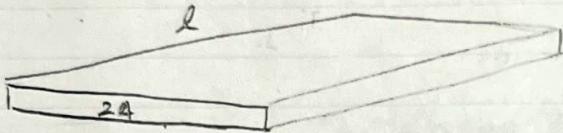

$$R \rightarrow \frac{R}{2}$$

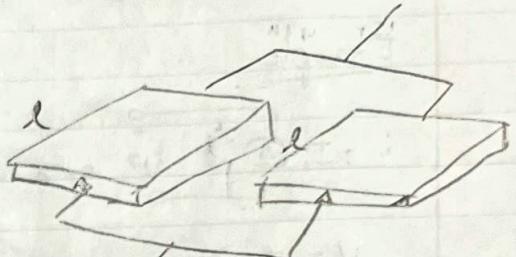

$$R \rightarrow \frac{R}{2}$$

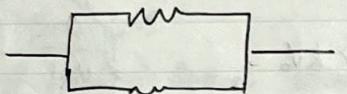


$$= \frac{R}{2}$$




(Resistors in parallel)

I/V characteristics


$$V = IR, I = \frac{V}{R}$$

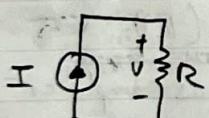

Different causes & effects

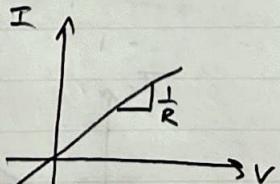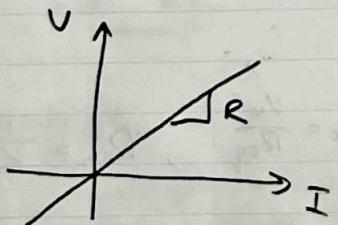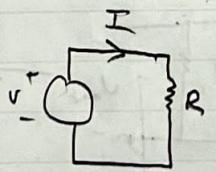


Example

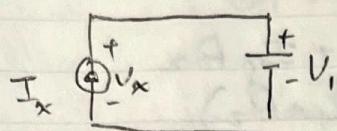


$$V_x = V_1 \rightarrow$$

independent of
 I_x

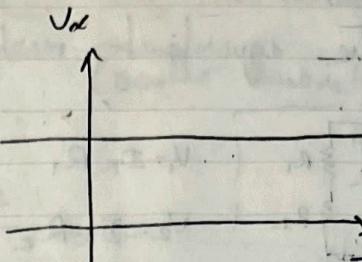


V/I characteristic
slope 0.

Example

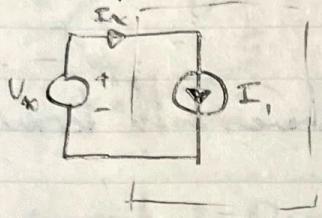


$$I_x = I_1$$

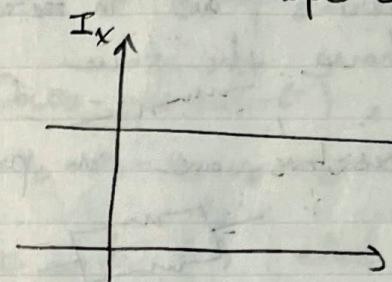



I/V characteristic
slope 0.

Application of Ohm's Law

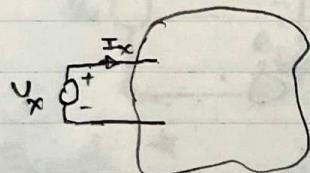


$$R_{eq} = \frac{V_x}{I_x}$$

Example

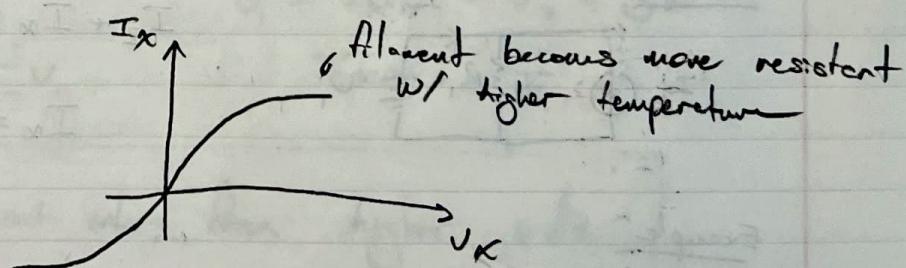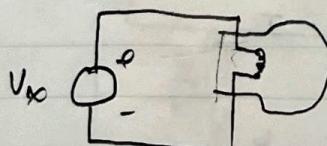

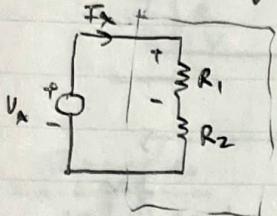Example

Find the equivalent resistance of this topology.



$$V_1 = I_x R_1$$

$$V_2 = I_x R_2$$

$$V_x = I_x R_1 + I_x R_2$$


$$= I_x (R_1 + R_2)$$

$$R_{eq} = R_1 + R_2 \quad (\text{resistors in series})$$

Details


Two resistors are in series if they share only one terminal and have the same current.

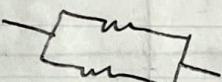Two resistors are in parallel if they share both terminals.



KCL & KVL


- KCL

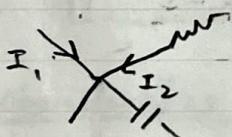

$$\sum_j I_j = 0 \quad (\text{charge conservation})$$

$$\sum I_{\text{entering}} = \sum I_{\text{existing}}$$


Example

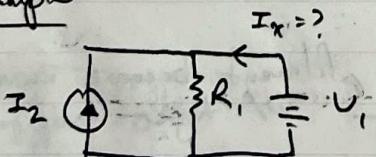

$$I_2 + I_x = \frac{V_1}{R_1}$$

$$I_x = \frac{V_1}{R_1} - I_2$$

Example

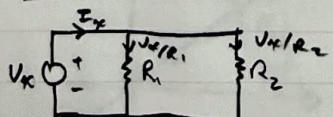

$$I_x = \frac{V_x}{R_1} + \frac{V_x}{R_2}$$


$$R_{eq} = \frac{V_x}{I_x} = \frac{1}{\frac{1}{R_1} + \frac{1}{R_2}} = \frac{R_1 R_2}{R_1 + R_2}$$

Observations: $R_{eq} = \frac{R_1 R_2}{R_1 + R_2} < R_1, R_2$ ($\parallel \rightarrow$ less resistance)

$R_1 \rightarrow 0 \Rightarrow R_{eq} \rightarrow 0$ (smaller dominates)

$R_1 \rightarrow \infty \Rightarrow R_{eq} = R_2$

- KVL

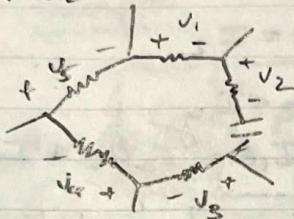


$$\sum V_j = 0 \text{ around a loop}$$

Approach 1: Down potential (-) , else (+)

$$-V_1 - V_2 - V_3 - V_4 - V_5 - V_6 = 0$$


Approach 2: Opposite, see negative write (-) , else (+) .

Example

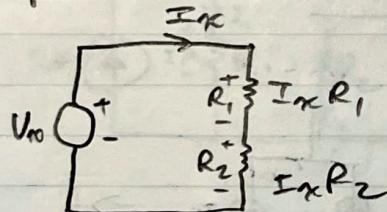


$$V_{ix} - I_x R_1 - I_x R_2 = 0$$

Example *

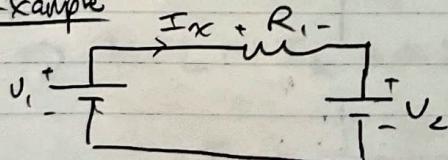


$$V_1 - I_x R_1 - V_2 = 0$$

$$I_x = \frac{V_1 - V_2}{R_1}$$

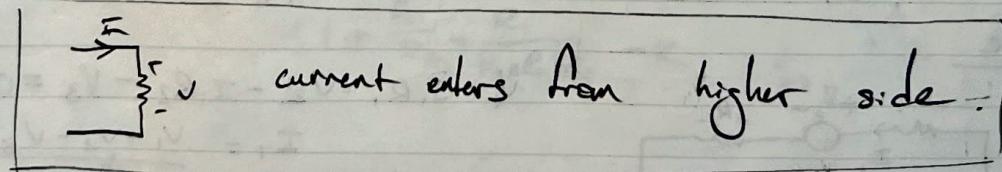


Example

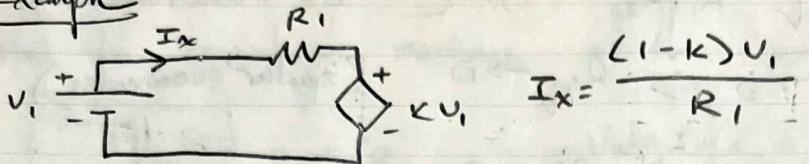

$$I_x = \frac{(1-k)V_1}{R_1}$$

Example

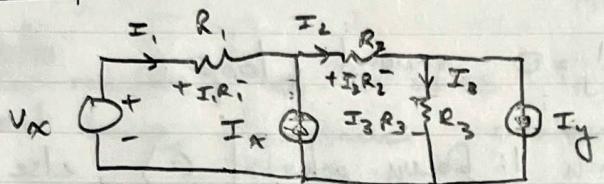


$$I_1 + I_x = I_2$$

$$I_2 = I_3 + I_y$$




$$V_{ix} = I_1 R_1 + I_2 R_2 + I_3 R_3$$

Mechanics of KVL & KCL

- Series Voltage Sources

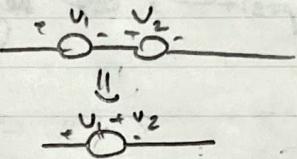


- parallel current sources

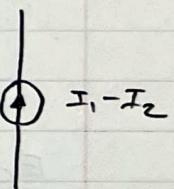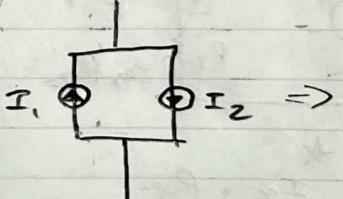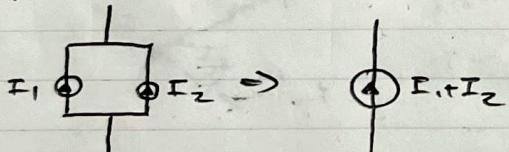


- Resistors in series/parallel

Example

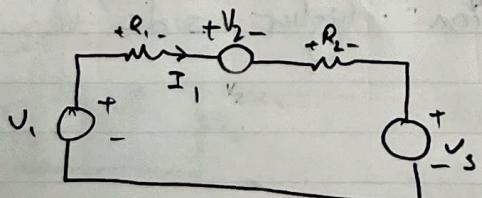


$$V_1 - I_1 R_1 - V_2 - I_1 R_2 - V_3 = 0$$

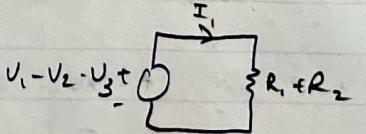
$$I_1 = \frac{V_1 - V_2 - V_3}{R_1 + R_2}$$




Example

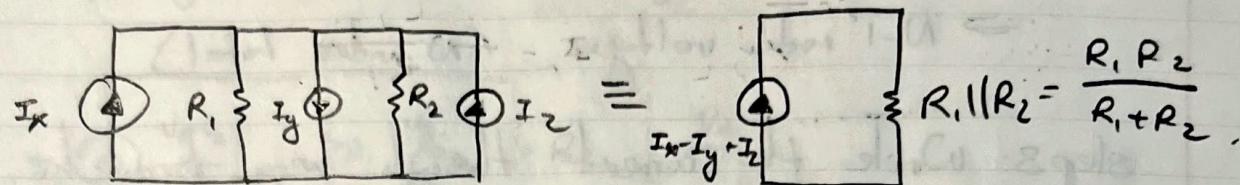

Example

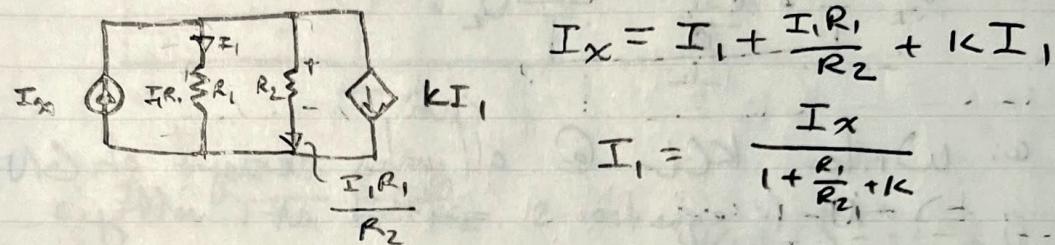

Example

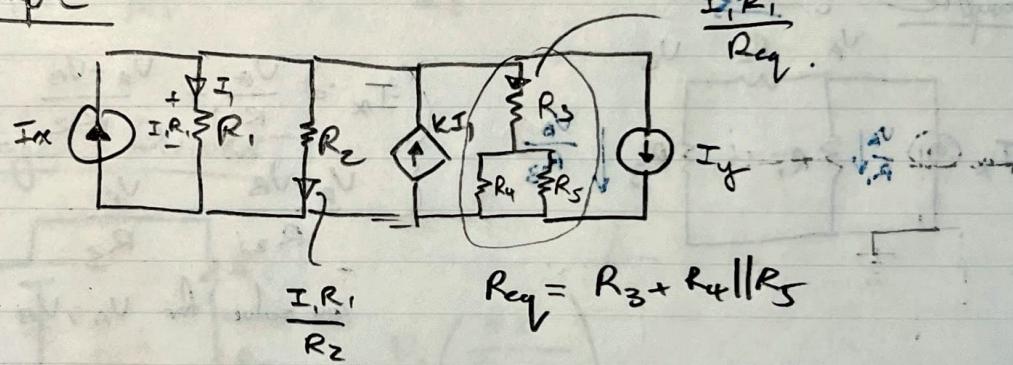


$$\Rightarrow \text{KCL: } I_x + K I_1 = I_1 \frac{I_1 R_1}{R_2} + \frac{I_1 R_1}{R_3 + R_4 \parallel R_5} + I_y$$

$$I_1 = \frac{I_x - I_y}{1 + \frac{R_1}{R_2} + \frac{R_1}{R_3 + R_4 \parallel R_5} - K}$$


Node Analysis

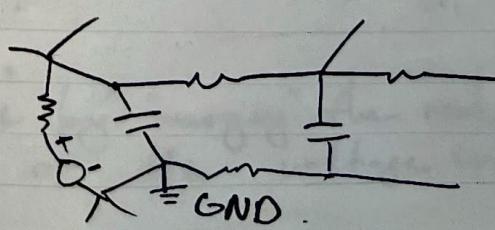Step 1: Select reference node
(the "ground")




Step 2: Assign voltages with respect to ground & other nodes.
 $\Rightarrow N-1$ node voltages (N nodes total)

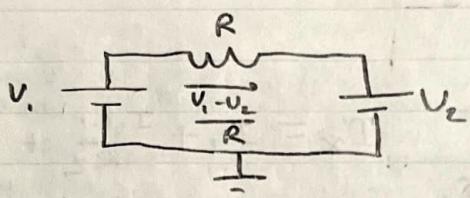Step 3: Write the current through every branch.



Step 4: Write KCL @ all nodes except at GND
 $\Rightarrow N-1$ equations \Rightarrow find $N-1$ voltages


Example

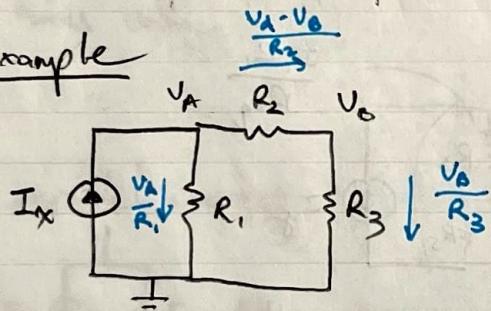

$$\left\{ \begin{array}{l} I_x = \frac{V_A}{R_1} + \frac{V_A - V_B}{R_2} \\ \frac{V_A - V_B}{R_2} = \frac{V_B}{R_3} \end{array} \right.$$

can solve for V_A, V_B


Example

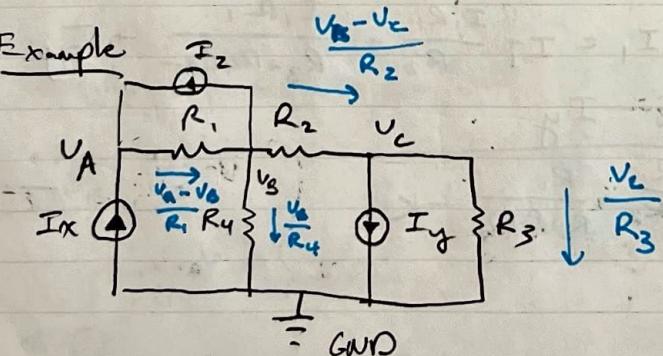

$$\left\{ \begin{array}{l} I_x + I_2 = \frac{V_A - V_B}{R_1} \\ \frac{V_A - V_B}{R_1} = \frac{V_B - V_C}{R_2} + \frac{V_B}{R_3} + I_3 \\ \frac{V_B - V_C}{R_2} = I_4 + \frac{V_C}{R_3} \end{array} \right.$$


can solve V_A, V_B, V_C

Example

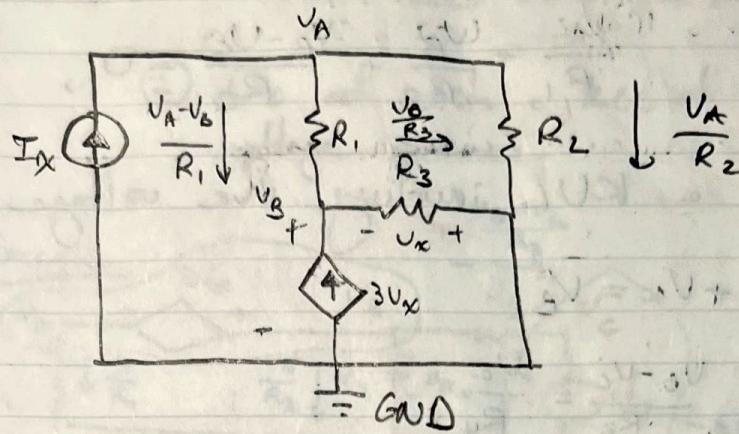

$$\left. \begin{array}{l} KCL: \\ \left\{ \begin{array}{l} I_{in} = \frac{V_A - V_B}{R_1} + \frac{V_A}{R_2} \\ \frac{V_A - V_B}{R_1} + 3V_X = \frac{V_B}{R_3} \end{array} \right. \\ KVL: \\ \left\{ \begin{array}{l} V_B + V_X = 0. \end{array} \right. \end{array} \right.$$


Voltage Divider

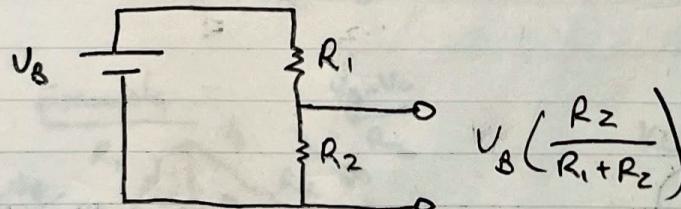

$$\left. \begin{array}{l} \text{Example} \\ \text{Circuit diagram:} \\ \text{KCL:} \\ \left. \begin{array}{l} \frac{V_B - V_C}{R_3} + \frac{V_C}{R_4} = I_x \\ \frac{V_B - V_C}{R_3} + \frac{V_B}{R_2} = I_x \\ I_x + \frac{V_A}{R_1} = 0 \end{array} \right. \end{array} \right.$$

With voltage source:

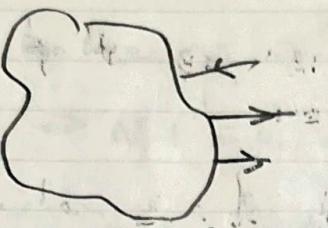Step 5: Form a "supernode" by "merging" the node on the two sides of the voltage source



\Rightarrow write a KCL for this "supernode".

$$\frac{V_A}{R_1} + \frac{V_B}{R_2} + \frac{V_B - V_C}{R_3} = 0.$$


Step 6: Write a KVL involving the voltage source

$$V_A + V_{x0} = V_B$$


so now:

$$\left\{ \begin{array}{l} \frac{V_B - V_C}{R_3} = \frac{V_C}{R_4} \\ \frac{V_A}{R_1} + \frac{V_B}{R_2} + \frac{V_B - V_C}{R_3} = 0 \\ V_A + V_{x0} = V_B \end{array} \right.$$

A Note on writing KVLs

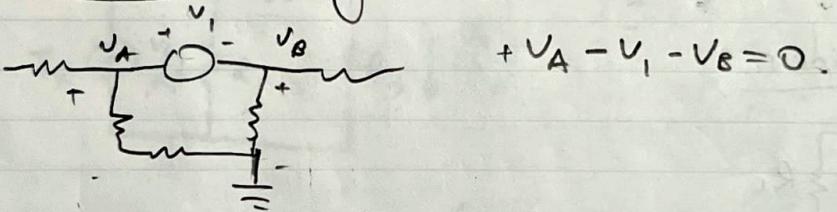

Example

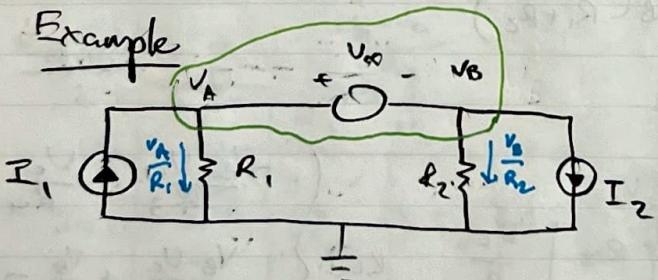


Supernode

$$\left\{ \begin{array}{l} V_A - V_x - V_B = 0 \\ I_1 = \frac{V_A}{R_1} + \frac{V_B}{R_2} + I_2 \end{array} \right.$$

Summary: ① Every voltage source reduces # of KCLs by 1.
 \Rightarrow Need to write KVL.

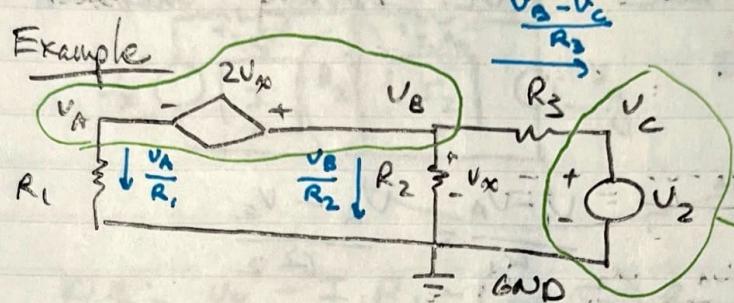② Do not write a KCL at either terminal of a voltage source.




No need for supernode because connected to ground.
 \Rightarrow causes repeat equation

$$\text{KCL: } \frac{V_A}{R_1} + \frac{V_B}{R_2} + \frac{V_B - V_C}{R_3} = 0$$

$$\text{KVL: } V_A + 2V_x - V_B = 0$$

$$V_C - V_2 = 0$$

$$V_B - V_{x0} = 0$$

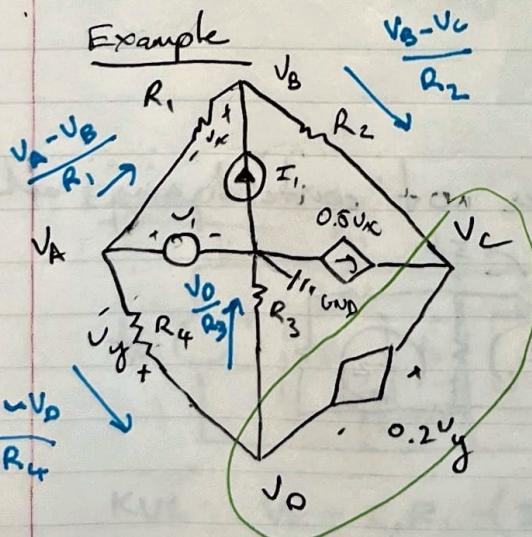

$$\text{KCL: } \frac{V_A - V_B}{R_1} + I_1 = \frac{V_B - V_C}{R_2}$$

$$\frac{V_B - V_C}{R_2} + 0.5V_x + \frac{V_A + V_D}{R_4} = \frac{V_D}{R_3}$$

$$\text{KVL: } V_D + 0.2V_y - V_C = 0$$

$$V_A = V_1$$

$$V_A + V_x - V_B = 0$$

$$V_0 + V_y - V_D = 0$$

Summary: Started w/ 5 nodes

Called one ground \rightarrow 4 nodes

Two voltage sources \rightarrow lose 2 KCL


2 KCL left

Write 2 KVL w/ voltage sources

Write 2 more KVL involving unknown voltages

V_A, V_B :


Example

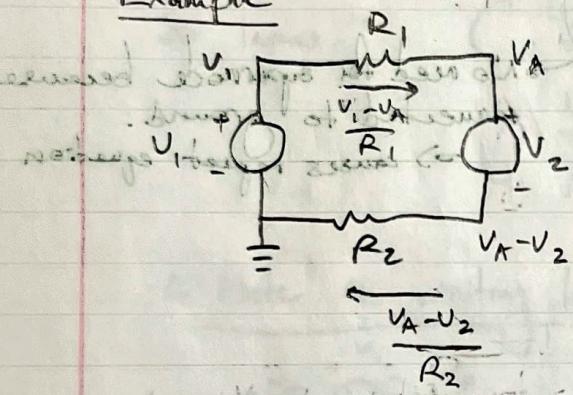

$$\frac{V_A - V_B}{R_1} = \frac{V_A - V_B}{R_2}$$

$$\Rightarrow V_A = \frac{V_1}{R_1} + \frac{V_2}{R_2}$$


$$\frac{V_A - V_B}{R_2}$$

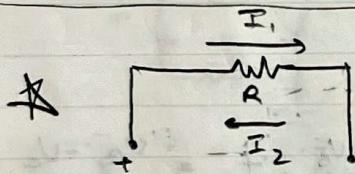

$$-V = (I_1 - I_2)R$$

Mesh Analysis

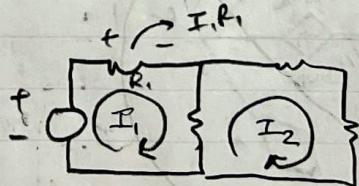- A mesh is a loop that does not contain any other loops within it.




Three steps:

- ① Identify all of the meshes and assign a current to each.

- ② Write the voltage drops on the circuit
- ③ Write KVL around every mesh.

Example

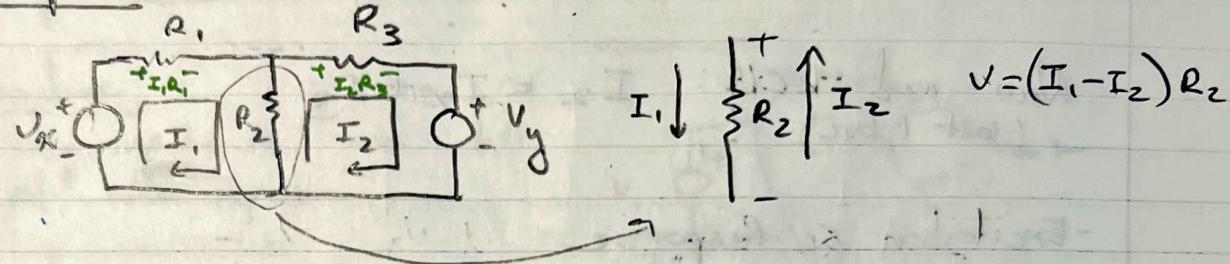

$$\text{KVL: } V_x - I_1 R_1 - (I_1 - I_2) R_2 = 0$$

$$(I_1 - I_2) R_2 - I_2 R_3 - V_y = 0$$

Two Observations

① Node Analysis is KCL centric


Has difficulty w/ voltage sources

② Mesh Analysis is KVL centric

Handles voltage sources easily

Has difficulty w/ current sources.

Example

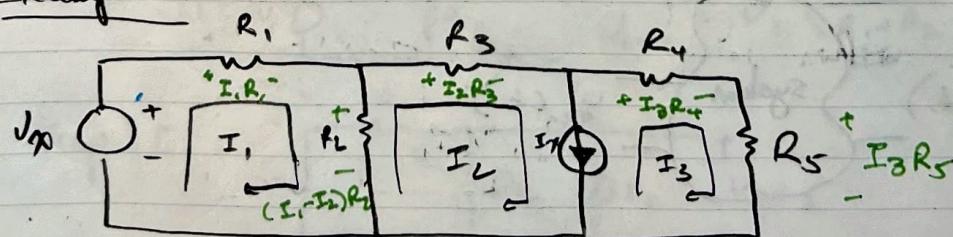

$$\text{KVL: } V_x - I_1 R_1 - (I_1 - I_2) R_2 = 0$$

$$(I_1 - I_2) R_2 - I_2 R_3 + ? = 0$$

↳ current source does not satisfy
KVL's law!

Solution: Merge two meshes into one "supermesh"

$$\Rightarrow (I_1 - I_2)R_2 + I_2R_3 + I_3R_4 + I_3R_5 = 0$$

Avoids current source.


Now need KCL: $I_2 = I_x + E_3$
(last 1 kvl)

- Excitation & Response



Independent sources = excitations, aka "inputs"

Other quantities:

Responses, aka "outputs"

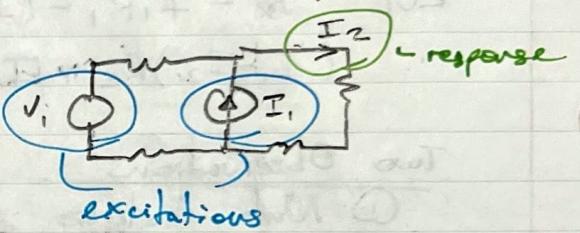

Linearity *

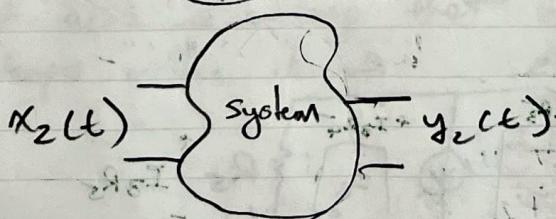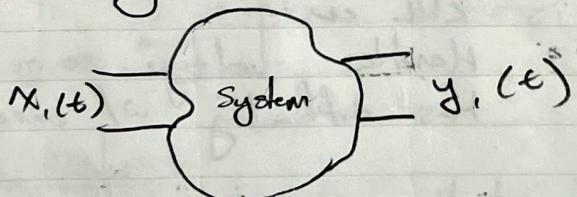

Linearity:


$$\alpha x_1(t) + \beta x_2(t) \xrightarrow{\text{System}} \alpha y_1(t) + \beta y_2(t)$$

Superposition


In a linear system, the total response to multiple excitations is equal to the sum of the corresponding responses.

Procedure

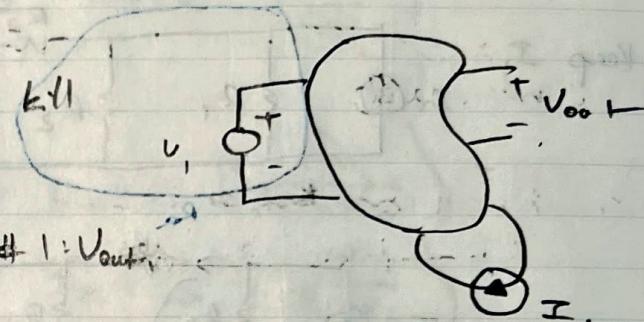- keep input # 1 and kill all other inputs.
- Find response to input # 1: $V_{out,1}$.
- Repeat for each input: $V_{out,2}, V_{out,3}, \dots$
- Total response = $V_{out,1} + V_{out,2} + \dots$




Example

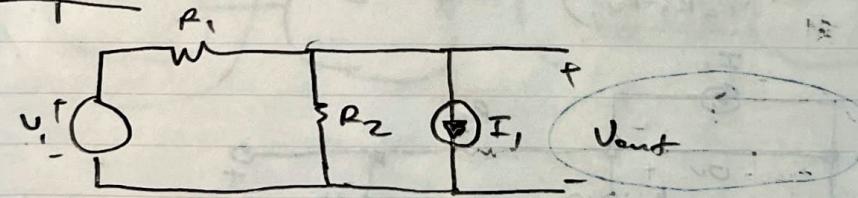

$$\text{Keep } V_1: \quad V_{out,1} = V_1 \left(\frac{R_2}{R_1 + R_2} \right) \quad (\text{voltage divider})$$

Keep I_1 :

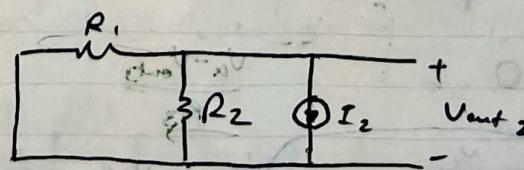


$$V_{out} = V_{out,1} + V_{out,2} = V_1 \frac{R_2}{R_1 + R_2} - I_1 \frac{R_1 R_2}{R_1 + R_2}$$



$$V_{out,2} = -(R_1/R_2) I_1$$

$$= -I_1 \frac{R_1 R_2}{R_1 + R_2}$$

Example

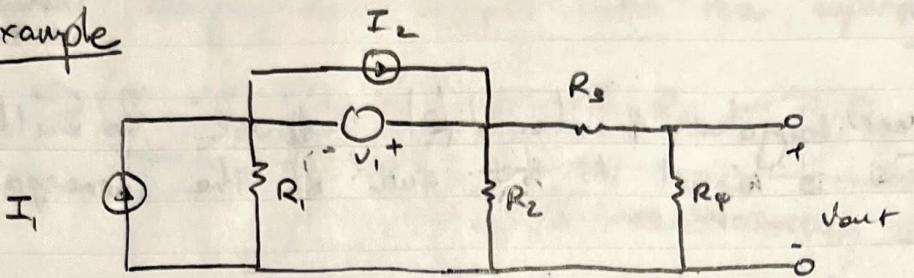


Keep I_s :

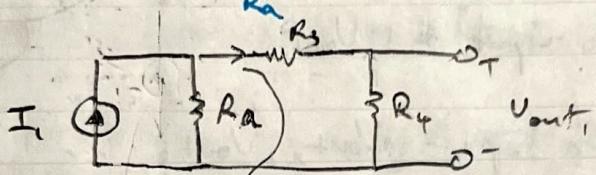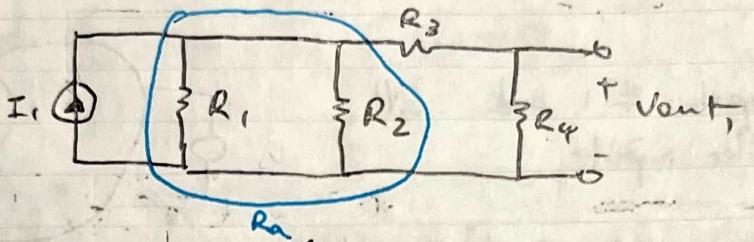

$$I_1 \left(\frac{R_a}{R_a + R_3 + R_4} \right), \text{ current divider}$$

$$V_{out_1} = I_1 \left(\frac{R_a}{R_a + R_3 + R_4} \right) \cdot R_4$$

Keep I_2 :

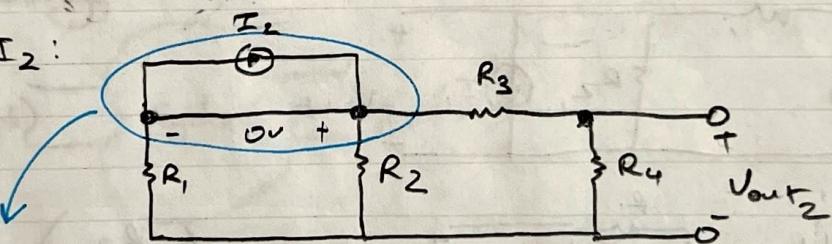


Current prefers path of least resistance

$$\rightarrow V_{out_2} = 0$$

$$\frac{V_a - V_{out_2}}{R_3}$$

Keep V_1 :

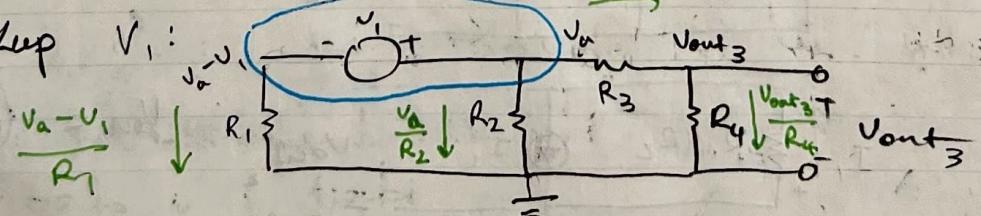


$$KCLs: \frac{V_a - V_{out3}}{R_3} = \frac{V_{out3}}{R_4}$$

$$\frac{V_a - V_1}{R_1} + \frac{V_a}{R_2} + \frac{V_a - V_{out3}}{R_3} = 0$$

$$V_{out} = V_{out1} + V_{out2} + V_{out3}$$


Current Divider

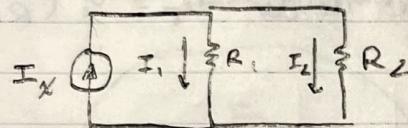


$$I_1 = I_x \left(\frac{R_2}{R_1 + R_2} \right)$$

$$I_2 = I_x \left(\frac{R_1}{R_1 + R_2} \right)$$

Thevenin's Theorem

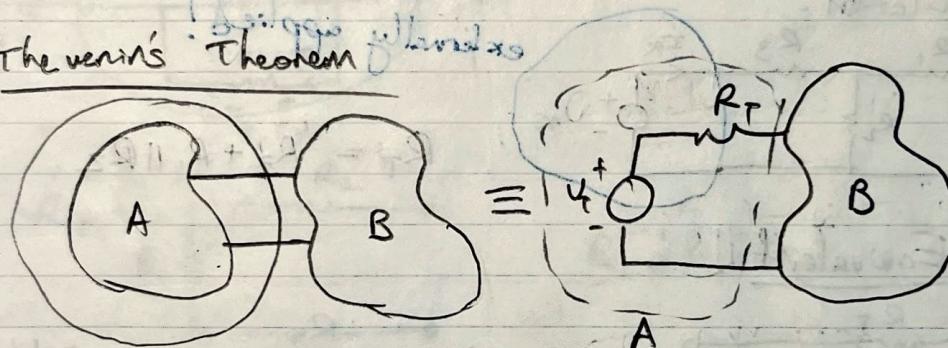


- Calculating V_T

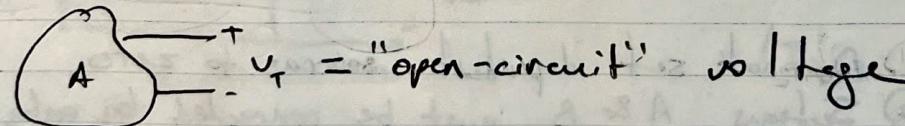

- Calculating R_T :

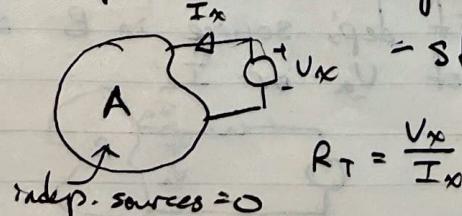
- Step 1: Set all independent sources in section A to zero.



$$R_T = \frac{V_x}{I_x}$$

- Step 2: Find resistance between the output wires of section A.
(Apply voltage, measure current)


Example

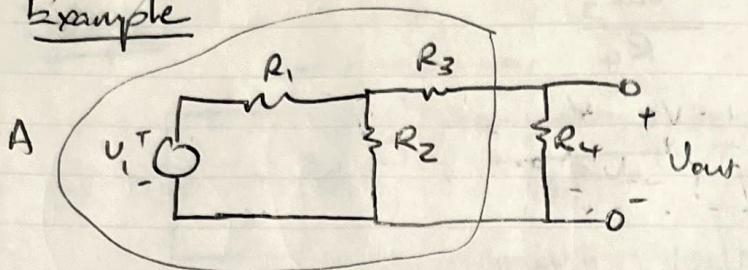

V_T calculation:


$$\Rightarrow \text{voltage divider: } V_T = V_1 \left(\frac{R_2}{R_1 + R_2} \right)$$

R_T calculation:

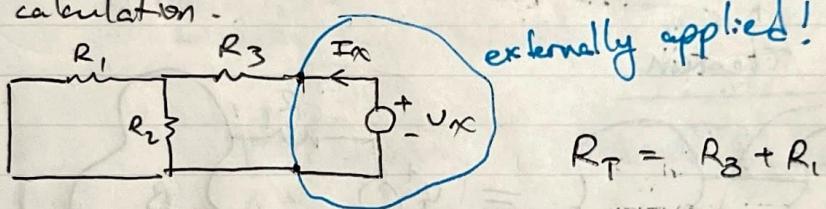

$$R_T = R_3 + R_1 \parallel R_2$$

Thevenin Equivalent

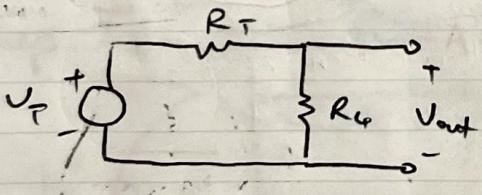



$$V_{out} = \frac{R_4}{R_4 + R_3 + R_1 \parallel R_2} \cdot V_T$$

$$= V_1 \left(\frac{R_2}{R_1 + R_2} \right) \left(\frac{R_4}{R_4 + R_3 + R_1 \parallel R_2} \right)$$



- Notes:
- ① Do not set dependent sources to zero.
 - ② Sections A & B must be connected by only 2 wires.
 - ③ Section A cannot control a dependent source in section B.

↳ Thevenin's will lose that interaction

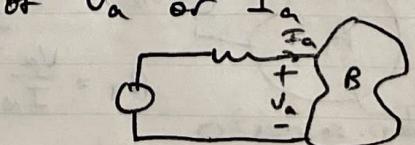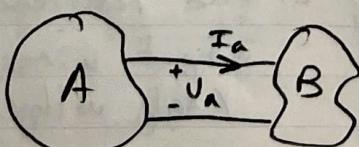↳ exception: if dep. source in B is a function of V_A or I_A




Example

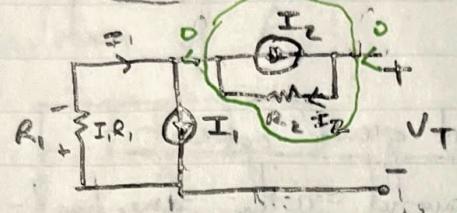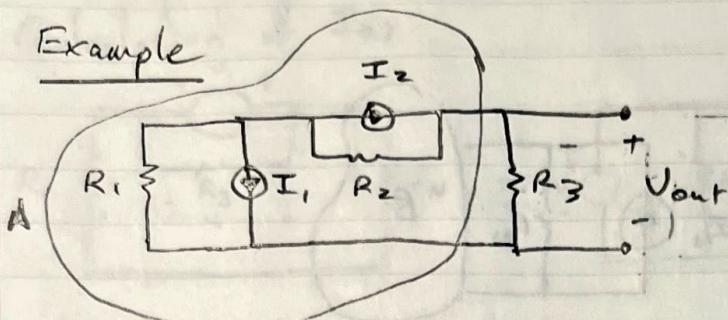


$$KUL: V_T - I_2 R_2 + I_1 R_1 = 0$$

$$V_T = I_2 R_2 - I_1 R_1$$

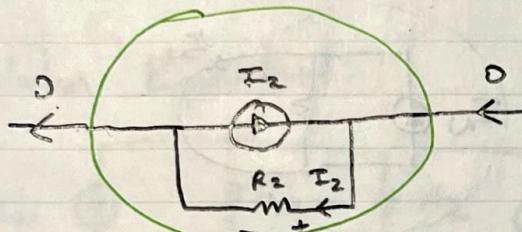


$R_T:$

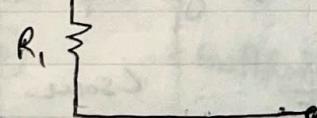

$$R_T = R_1 + R_2$$


Thevenin Equivalent

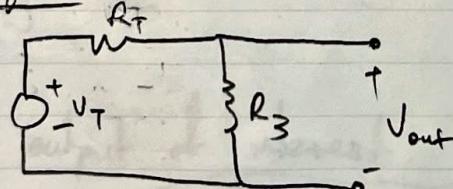


$$V_{out} = V_T \left(\frac{R_3}{R_3 + R_T} \right)$$

$$= (I_2 R_2 - I_1 R_1) \left(\frac{R_3}{R_1 + R_2 + R_3} \right)$$


Norton's Theorem

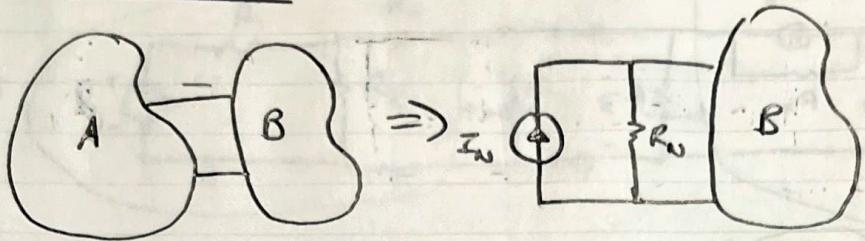


Calculation of I_N :

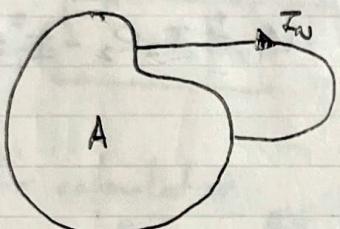

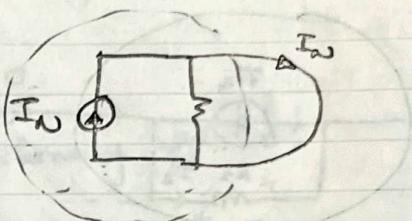"short-circuit" current.
Be careful with direction!





Calculation of R_N :

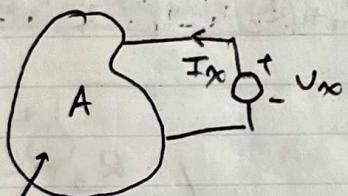

Indep. sources = 0


$$R_N = \frac{V_A}{I_X} \quad (\text{same as Thevenin's})$$

Example

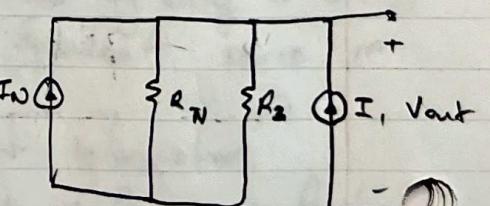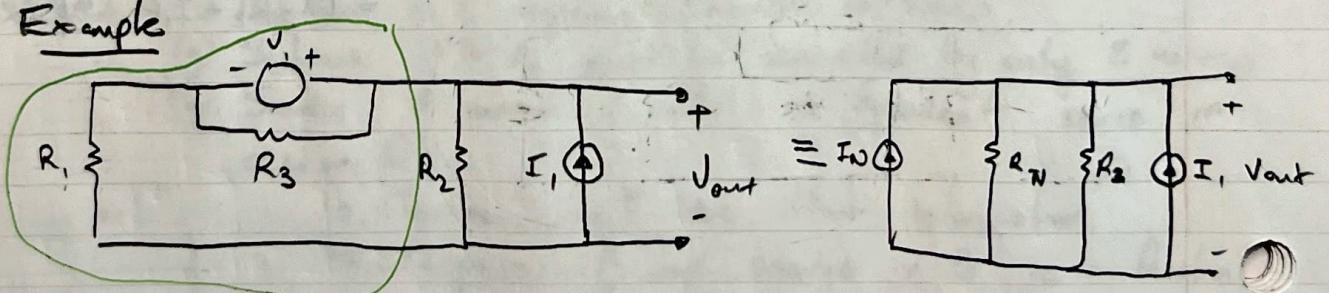

easy to handle
so use Norton's.

Calculation of I_N :

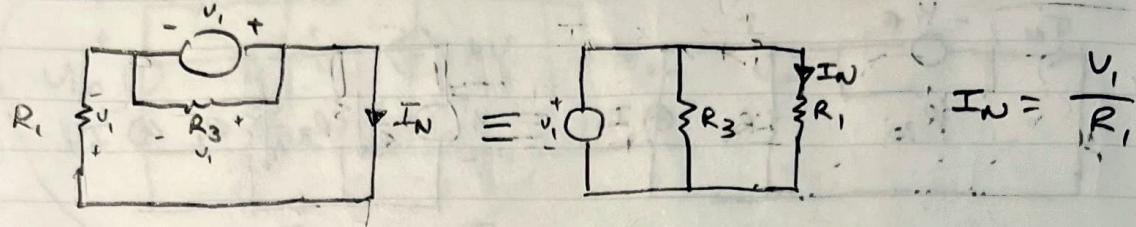


$$I_N = \frac{v_1}{R_1}$$

Calculation of R_N :




$$R_N = R_1$$

Norton Equivalent:

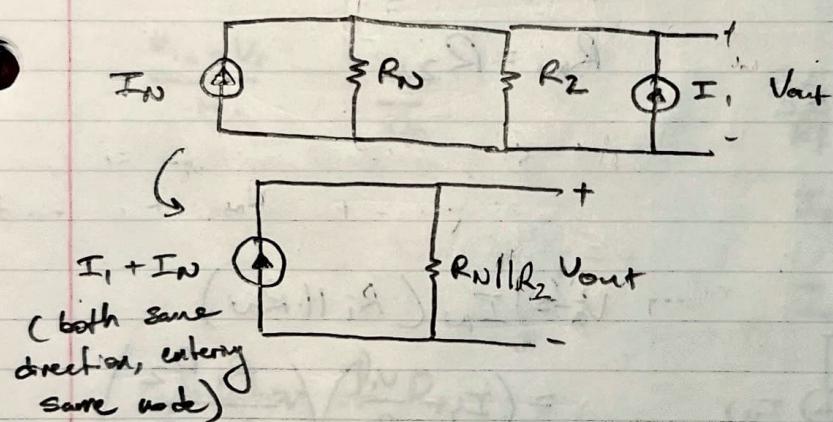


$$V_{out} = (I_1 + \frac{v_1}{R_1}) \left(\frac{R_1 R_2}{R_1 + R_2} \right)$$

Another output of interest:

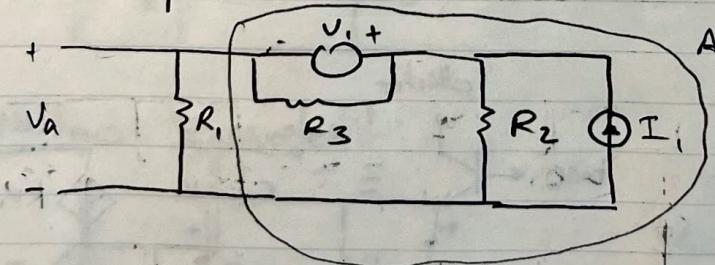


Calculation of I_N :

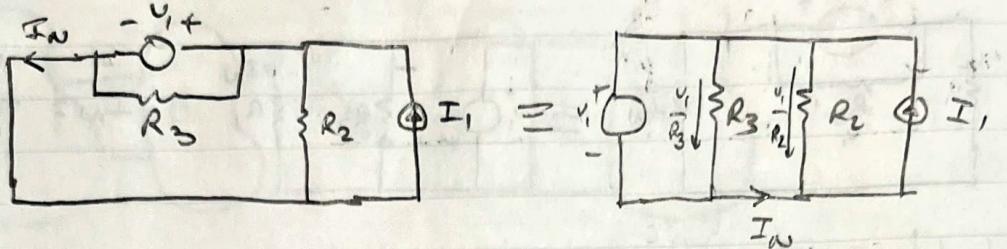

$$\frac{v_i}{R_2} + I_N = I_1$$


$$I_N = I_1 - \frac{v_i}{R_2}$$

Calculation of R_N :

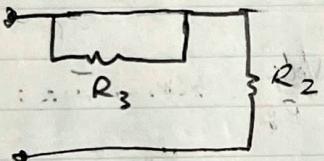

$$R_N = R_2$$



Norton Equivalent:

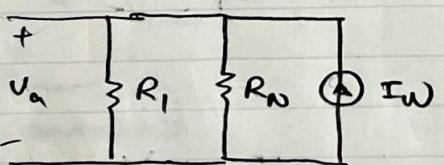


$$v_o = I_N (R_1 \parallel R_N)$$


$$= \left(I_1 - \frac{v_i}{R_2} \right) \left(\frac{R_1 R_N}{R_1 + R_N} \right)$$

Amplifier Example

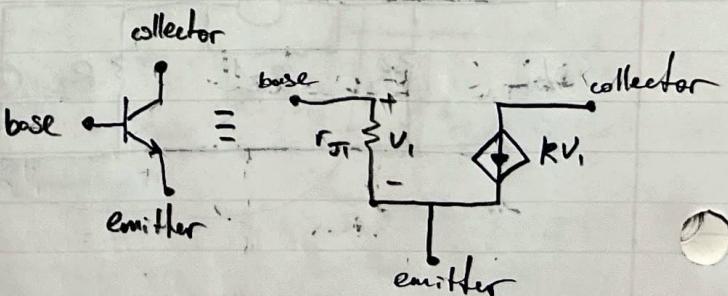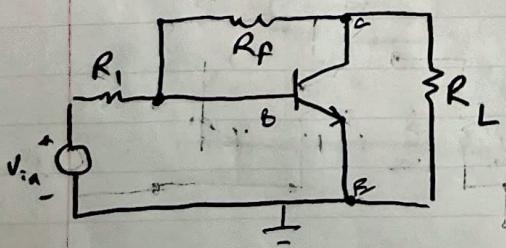

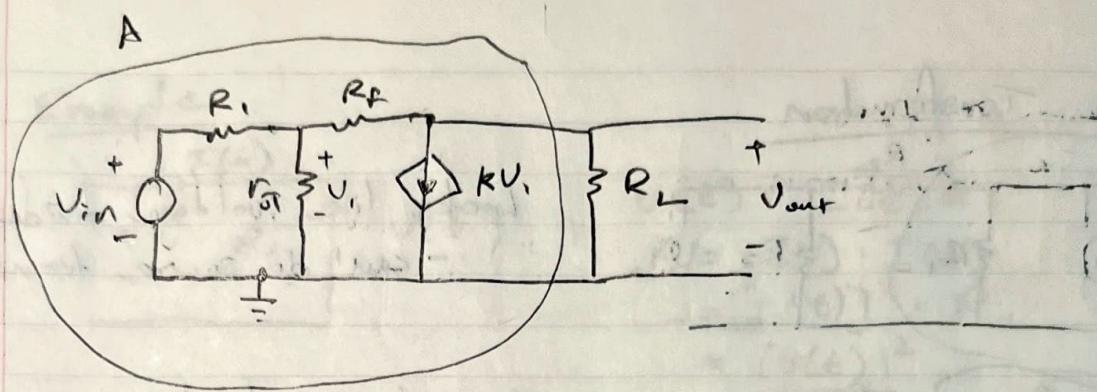

Calculation of I_{IN} :

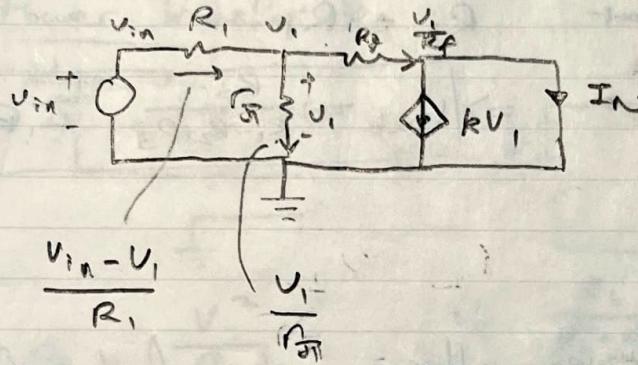

$$KCL: \frac{V_{in} - V_i}{R_1} = \frac{V_i}{R_f} + \frac{V_i}{R_{in}}$$


$$V_i = \frac{V_{in}}{R_1} \left(\frac{1}{R_1} + \frac{1}{R_{in}} + \frac{1}{R_f} \right)$$

$$\frac{V_i}{R_f} = RV_i + I_N$$

$$I_N = \frac{V_i}{R_f} - RV_i$$


$$I_N = V_i \left(\frac{1}{R_f} - R \right)$$

Calculation of R_N :

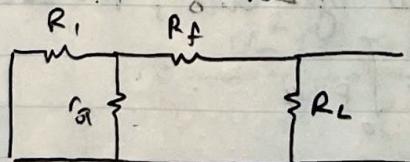


$$R_N = (R_f + R_L) // R_1 // R_{in}$$

Norton's Equivalent:

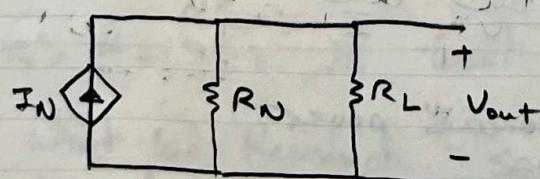

$$V_{out} = I_N (R_N // R_L)$$

Source Transformation

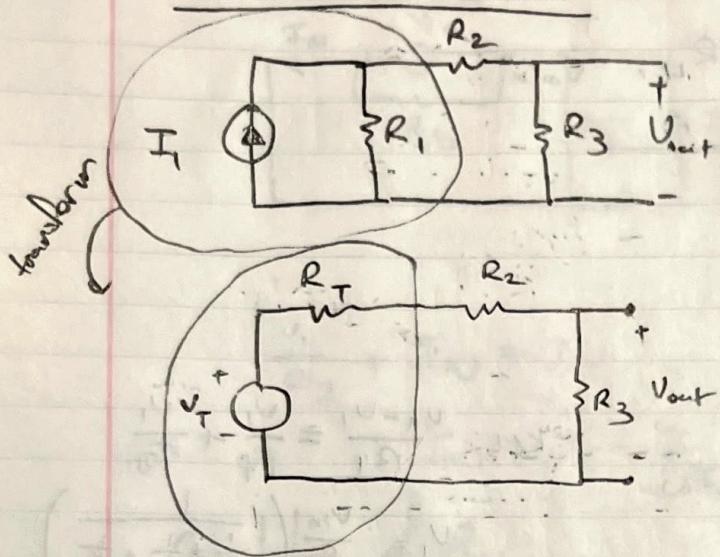

Looks like voltage divider
- can do source transformation

Thevenin's equivalent:

$$V_T = I_s R_1$$

$$R_T = R_1$$

$$\Rightarrow V_{out} = \frac{R_3}{R_1 + R_2 + R_3} \cdot I_s R_1$$

Energy

$$Q = C V \quad \text{assume voltage is constant for large } Q.$$

$$dE = (dQ) V.$$

$$= V dQ$$

Power: $P = \frac{dE}{dt}$ e.g. 20W light bulb, $P = 20W$.

$$20W = \frac{20J}{1\text{ sec}}$$

$$E = \int P dt$$


Power in Circuits:

$$dE = V dQ$$

$$P = \frac{dE}{dt} = \underbrace{\frac{dE}{dQ}}_V \cdot \underbrace{\frac{dQ}{dt}}_I = V(t) I(t)$$

Instantaneous power

Example

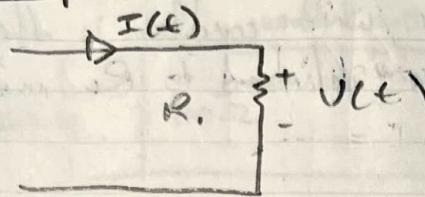


$$V(t) = I(t)R,$$

$$P = V(t) \cdot I(t)$$

$$= [I(t)]^2 \cdot R,$$

$$= \frac{[V(t)]^2}{R},$$


Power Transfer

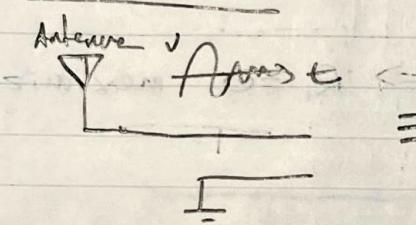

source resistance

load resistor

$$R_T \approx 50\Omega$$

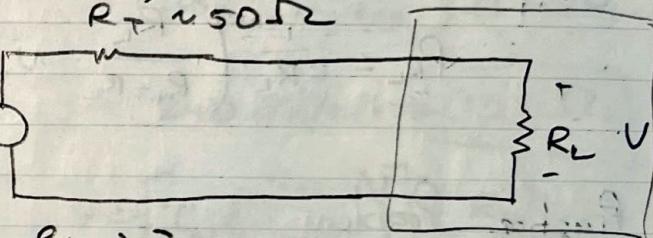

$$P_{R_L} = \frac{V^2}{R_L} = \frac{\left(V_T \cdot \frac{R_L}{R_L+R_T}\right)^2}{R_L} = \frac{V_T^2 \cdot R_L}{(R_L+R_T)^2}$$

$$0 = \frac{dP_{R_L}}{dR_L} = \frac{(R_L+R_T)^2 \cdot V_T^2 - V_T^2 R_L (2(R_L+R_T))}{(R_L+R_T)^4}$$

$$= \frac{V_T^2 (R_L+R_T) [R_L+R_T - 2R_L]}{(R_L+R_T)^4}$$


$$= \frac{V_T^2 (R_L+R_T)}{(R_L+R_T)^4} (R_T - R_L)$$

$\Rightarrow R_L = R_T$ is local max for P_{R_L} .

Want load Resistance = source Resistance for max power transfer.

\Rightarrow "matched condition".

Caution

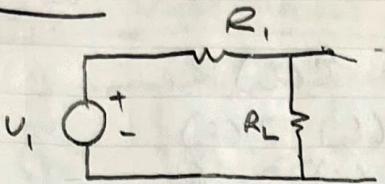


Under what condition is the power delivered to R_L maximum?

① $R_L = R_i$ (only if R_L is variable but R_i is fixed)

② if R_i is not fixed, but R_L is.


$$P_{R_L} = \frac{1}{R_L} \left(\frac{R_L}{R_i + R_L} \cdot V_s \right)^2 \Rightarrow R_i = 0 \text{ maximizes } P_{R_L}$$

Practice Problem

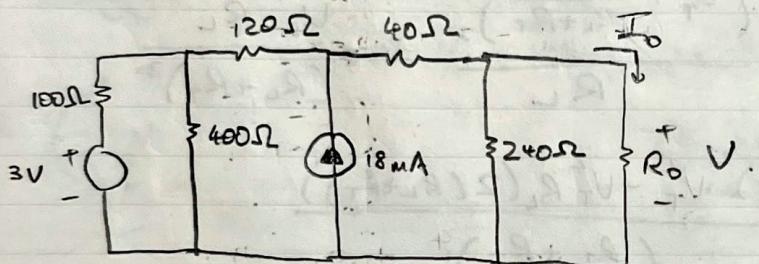

Solve for I_o , then find V_o in terms of R_o .

Calculating I_N :

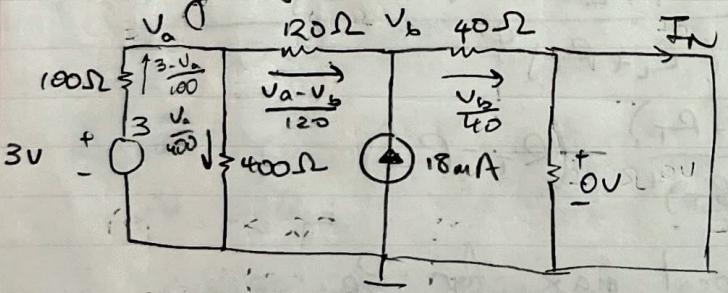


$$\begin{cases} \frac{3-V_a}{100} = \frac{V_a}{400} + \frac{V_a-V_b}{120} \\ \frac{V_a-V_b}{120} + \frac{18}{100} = \frac{V_b}{40} \end{cases}$$

$$I_N = \frac{V_b}{40}$$

$$I_N = \frac{V_b}{40} = \frac{1}{40} A$$


= $\frac{1}{40} A$ is a negative solution

Calculating R_N :

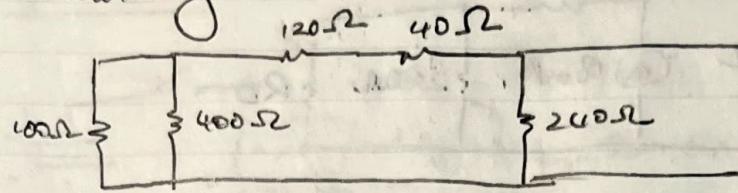

$$= \frac{160\Omega}{100\Omega(400\Omega)} = \frac{160}{100 + 400} \Rightarrow R_N = (160 + 100)(400) / 11240$$

$$= 240 / 11240 = \boxed{120\Omega}$$


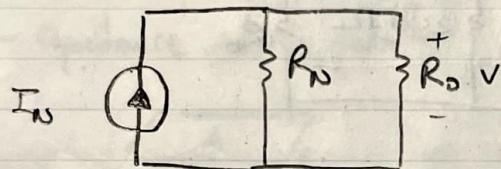


$$V = \left[I_N \left(\frac{R_N}{R_N + R_o} \right) \right] (R_o)$$

$$= 3 \left(\frac{R_o}{120 + R_o} \right)$$







$$I_o = 3 \left(\frac{1}{120 + R_o} \right)$$

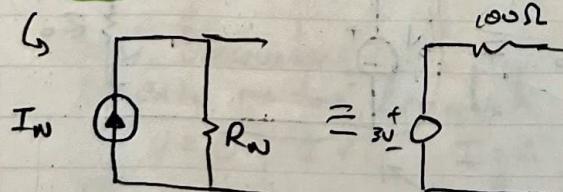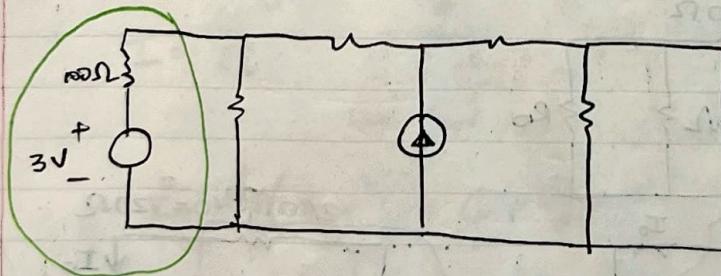Alternate solution with source transformation:



$$I_N = \frac{3}{100} = 30 \mu A$$


$$R_N = 100\Omega$$

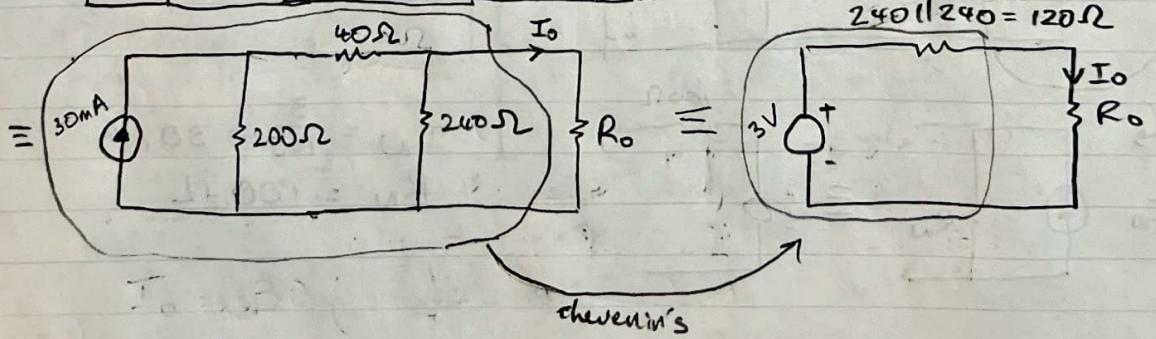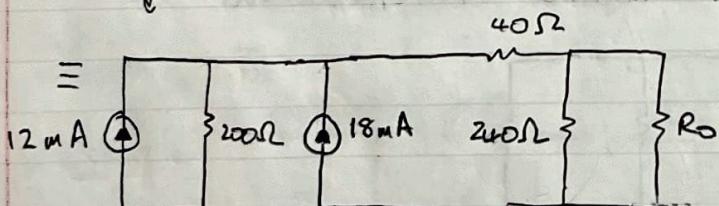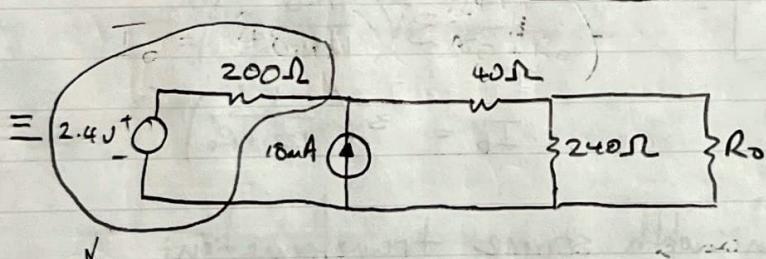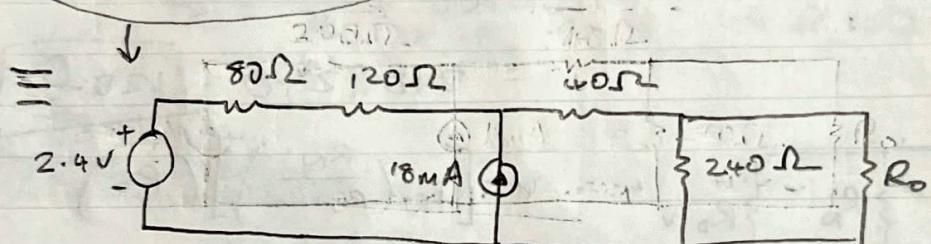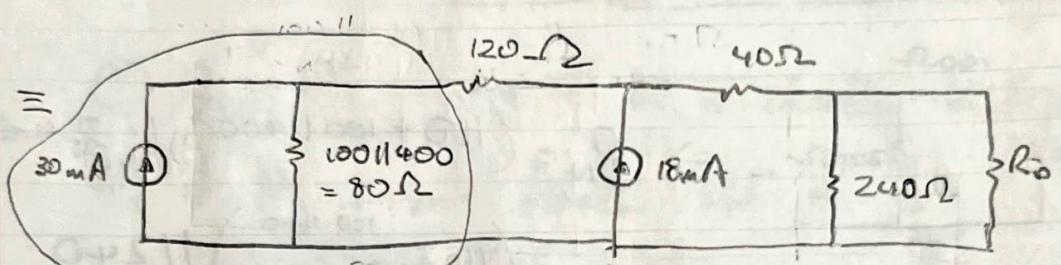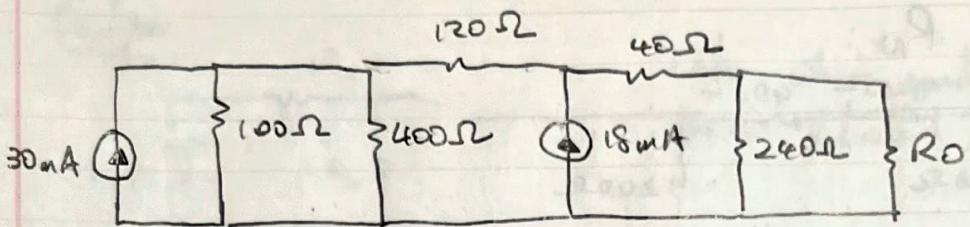

$$T_0 = \frac{\omega}{120 + R_s}$$

$$U_0 = \frac{3R_0}{120 + R_0}$$

Capacitors

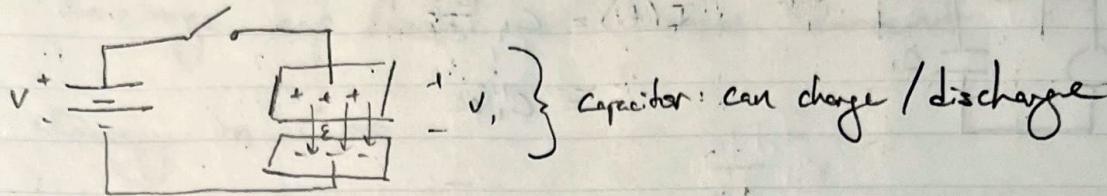


} capacitor: can charge / discharge

Definition of Capacitance

$$C = \frac{Q}{V} \quad \Rightarrow \quad C_1 = \frac{Q}{V}$$

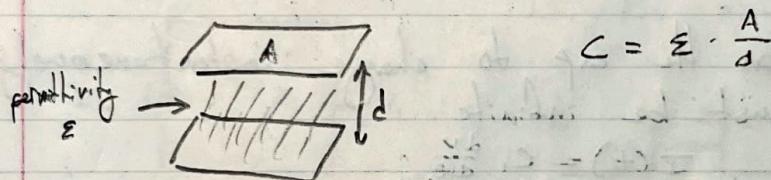- capacitance of a parallel-plate structure



- current-voltage relationships

$$I = \frac{dQ}{dt} \quad \text{and} \quad C_1 \frac{1}{V} \uparrow$$

$$I = \frac{d}{dt}(C_1 V) = C_1 \frac{dV}{dt}$$


Some Observations:

① Unlike resistors for which $V=0 \Rightarrow I=0$, capacitors can have $V=0, I \neq 0$; $I=0, V \neq 0$



② Voltage can be found from the current

$$V = \frac{1}{C_1} \int_0^t I dt$$

Example

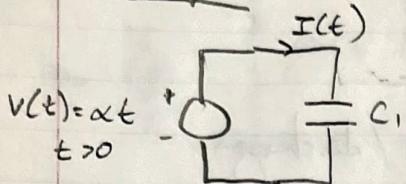
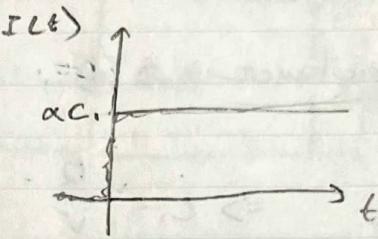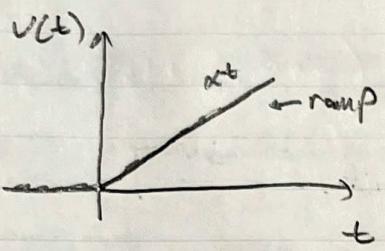
$$I(t) = C_1 \frac{dV}{dt} = C_1 \alpha$$





Important Points

- ① If voltage on cap is constant, $I = C_1 \frac{dV}{dt} = 0$.
- ★ ② For the voltage on the cap to change instantaneously, the current must be infinite.
↳ derives from $I(t) = C_1 \frac{dV}{dt}$.

\Rightarrow If current available is $< \infty$, cap voltage cannot jump in zero time.

Example

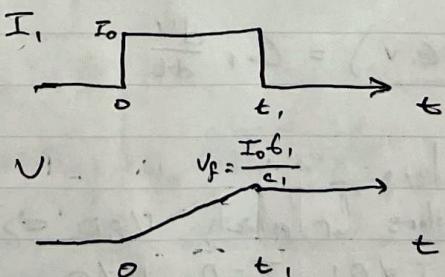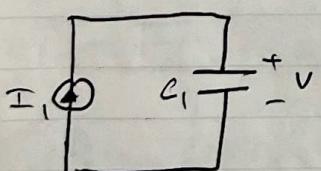


$$V(t) = \frac{1}{C_1} \int_0^t I dt = \frac{I_0 t_1}{C_1}$$

Voltage as area under current vs. time waveform:

↳ charge cap faster with more current




• Energy in Caps

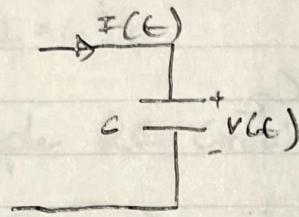


$$P = V(t)I(t)$$

$$\begin{aligned} E &= \int P dt = \int V(t) [C \frac{dV}{dt}] dt \\ &= \frac{1}{2} CV^2 \end{aligned}$$

Example

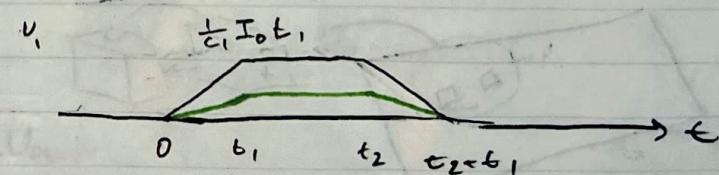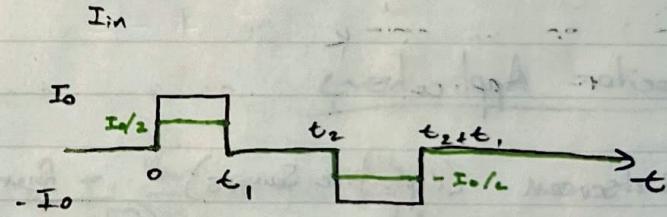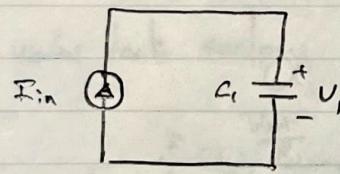

• Series & Parallel Caps

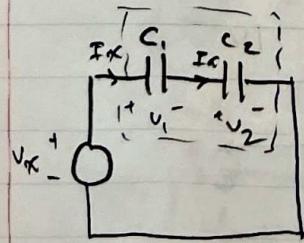


$$V_1 = \frac{1}{C_1} \int I_x dt$$

$$V_2 = \frac{1}{C_2} \int I_x dt$$


$$V_x = \left(\frac{1}{C_1} + \frac{1}{C_2} \right) \int I_x dt$$

$$\begin{aligned} V_x - V_1 - V_2 &= 0 \\ \Rightarrow V_x &= V_1 + V_2 \end{aligned}$$
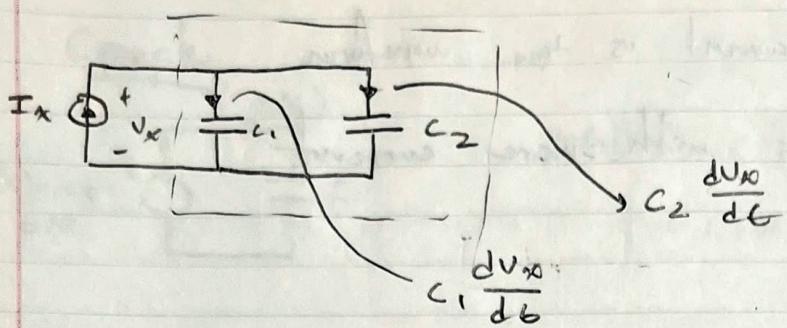
$$\Rightarrow \frac{1}{C_{eq}} = \frac{1}{C_1} + \frac{1}{C_2}$$



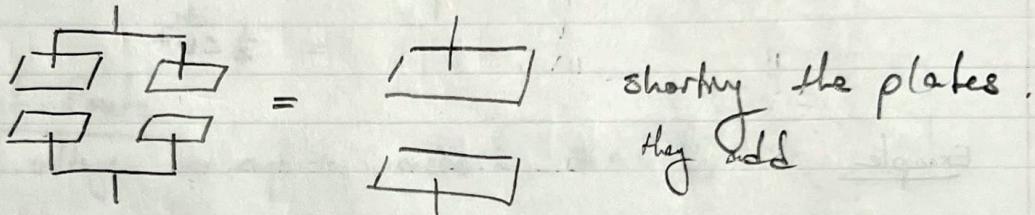
$$I_x = (C_1 + C_2) \frac{dV_{x0}}{dt} \Rightarrow C_{eq} = C_1 + C_2$$




Capacitor Applications

- Touchscreen (capacitive Sensors)

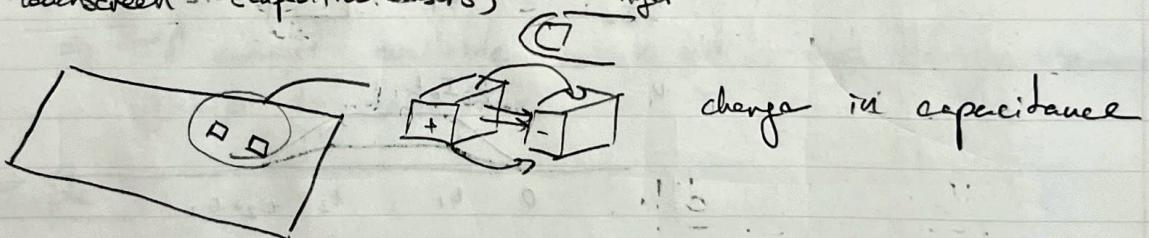



- Parasitic Caps

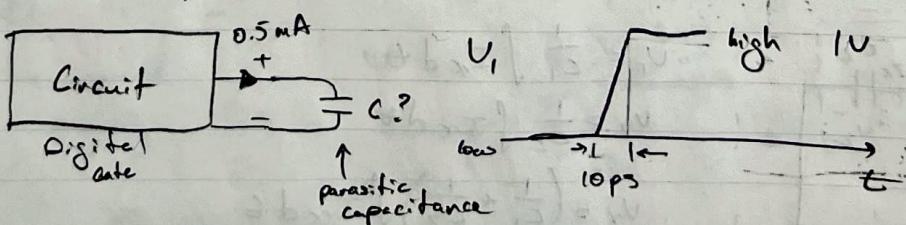



$$I = C \frac{dU}{dt}$$

$$0.5 \text{ mA} = C \frac{1 \text{ V}}{10 \text{ ps}} \Rightarrow C = 5 \times 10^{-15} \text{ F} = 5 \text{ fF}$$


A Note on Caps

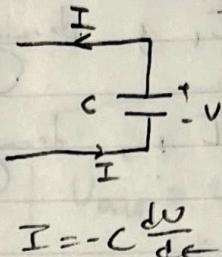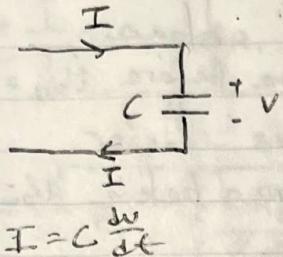

Simple RC Circuit

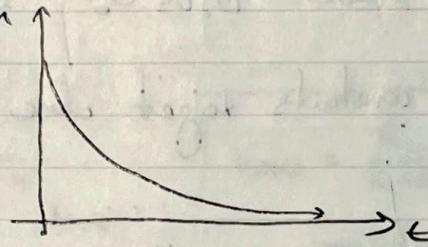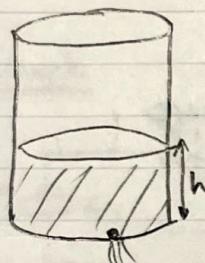

water tank analogy

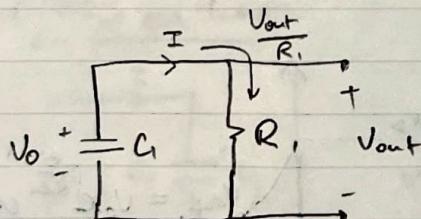

$$I = \frac{V_{out}}{R_1} = -\frac{1}{R_1 C_1} \frac{dV_{out}}{dt}$$

$$V_{out}(0) = V_0$$

$$\frac{V_{out}}{R_1} = -C_1 \frac{dV_{out}}{dt}$$

$$\int_0^t \frac{dt}{-R_1 C_1} = \int_{V_0}^{V_{out}} \frac{dV_{out}}{V_{out}}$$

$$-\frac{t}{R_1 C_1} = \ln \left(\frac{V_{out}}{V_0} \right)$$

$$V_{out} = V_0 e^{-\frac{t}{R_1 C_1}}$$

① The decay rate depends on $R, L, = \tau$ ("time constant")

For $\tau_2 > \tau_1$, decay becomes slower
(more time before $V_{out} = V_0 e^{-1}$)

$\tau_3 < \tau_1$, decay becomes faster
(less time before $V_{out} = V_0 e^{-1}$)

② $V_{out}(t=\tau) = V_0 e^{-1} = 0.37 V_0$

$$V_{out}(t=2\tau) = V_0 e^{-2} = 0.14 V_0$$



$$V_{out}(t=3\tau) = V_0 e^{-3} = 0.05 V_0 \approx 0$$

Three time constants together close to zero.

Current:

$$I = \frac{V_{out}}{R_1} = \frac{V_0}{R_1} e^{-\frac{t}{R_1 L}}$$



Example

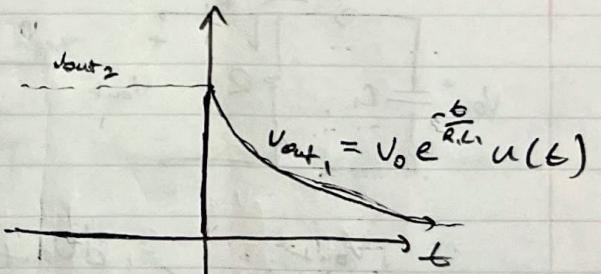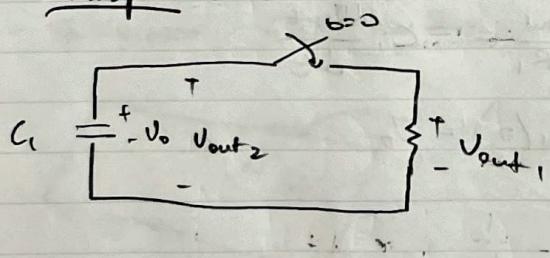

V_{out1} jumps; V_{out2} does not.


↳ Need to multiply by $u(t)$ (unit step function)

Example

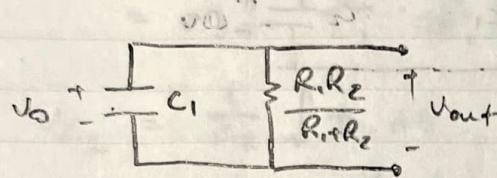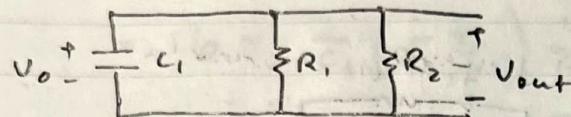



$$\left. \begin{aligned} V_{out} &= V_o e^{-\frac{t}{T}} \\ T &= \frac{R_1 R_2}{R_1 + R_2} C_1 \end{aligned} \right\}$$

Example

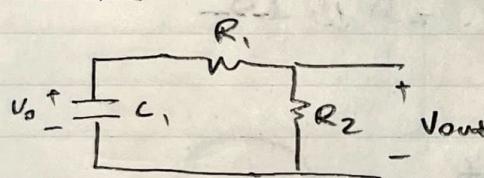

$$\left. \begin{aligned} V_{out} &= \frac{R_2}{R_1 + R_2} \left(V_o e^{-\frac{t}{T}} \right) \\ T &= (R_1 + R_2) C_1 \end{aligned} \right\}$$

Notes on Caps

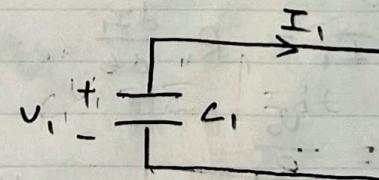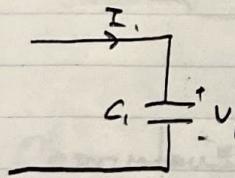



$$\Delta V_1 = \frac{1}{C_1} \int I_1 dt$$

$$\Delta V_1 = -\frac{1}{C_1} \int I_1 dt$$

After integration we must include a constant and, based on the initial condition(s), find its value.

Two-Capacitor Problem

Water Analogy

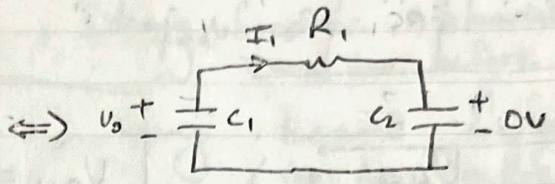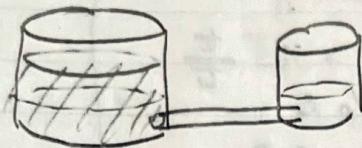

$$V_0 - \frac{1}{C_1} \int I_1 dt \pm \frac{I_1}{C_1} = +I_1 R_1 - C_2 \frac{1}{I_2} + \frac{1}{C_2} \int I_2 dt$$

$$V_0 - \frac{1}{C_1} \int I_1 dt = I_1 R_1 + \frac{1}{C_2} \int I_2 dt$$

$$V_0 - \left(\frac{1}{C_1} + \frac{1}{C_2} \right) \int I_1 dt = I_1 R_1$$

$$-\left(\frac{1}{C_1} + \frac{1}{C_2} \right) I_1 = R_1 \frac{dI_1}{dt}$$

$$I_1(t=0) = \frac{V_0}{R_1}$$

$$\Rightarrow \int_0^t \frac{1}{R_1} \left(\frac{1}{C_1} + \frac{1}{C_2} \right) dt = \int \frac{dI_1}{I_1}$$

$$-\frac{1}{R_1} \left(\frac{1}{C_1} + \frac{1}{C_2} \right) t = \ln \left(\frac{I_1(t)}{\frac{V_0}{R_1}} \right)$$


$$I_1(t) = \frac{V_0}{R_1} e^{-\frac{t}{\tau}}$$

$$\tau = R_1 \left(\frac{C_1 C_2}{C_1 + C_2} \right)$$

$\Rightarrow C_1, C_2$ in series

$$\begin{aligned}
 V_{C_1} &= V_0 - \frac{1}{C_1} \int_0^t \frac{V_0}{R_1} e^{-\frac{t}{\tau}} dt \\
 &= V_0 - \frac{1}{C_1} (-\tau) \frac{V_0}{R_1} e^{-\frac{t}{\tau}} + \frac{1}{C_1} (-\tau) \frac{V_0}{R_1} \\
 &= V_0 + \frac{\tau}{C_1} \cdot \frac{V_0}{R_1} e^{-\frac{t}{\tau}} - \frac{\tau}{C_1} \cdot \frac{V_0}{R_1}.
 \end{aligned}$$
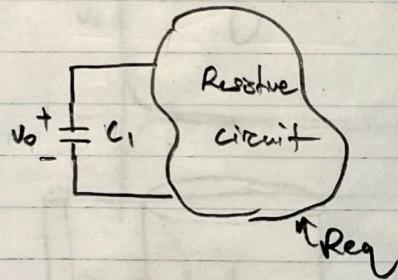
$$\begin{aligned}
 V_{C_2} &= \frac{1}{C_2} \int I_1 dt \\
 &= \frac{1}{C_2} \cdot \int_0^t \frac{V_0}{R_1} e^{-\frac{t}{\tau}} dt \\
 &= \frac{I_1}{C_2} \left(\frac{V_0}{R_1} \right) \left(1 - e^{-\frac{t}{\tau}} \right)
 \end{aligned}$$




$$\tau = R_{\text{eq}} C_1$$

Observations

- ① Is charge conserved? Yes.
- ② Is energy conserved? No.


e.g.

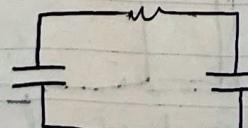

$$\text{At } t=0, \epsilon = \frac{1}{2} C_1 V_0^2$$


$$\begin{aligned}
 \text{At } t=\infty, \epsilon &= \frac{1}{2} C_1 \left(\frac{V_0 C_1}{C_1 + C_2} \right)^2 + \frac{1}{2} C_2 \left(\frac{V_0 C_1}{C_1 + C_2} \right)^2 \\
 &= \frac{1}{2} \left(\frac{V_0^2 C_1^2}{C_1 + C_2} \right)
 \end{aligned}$$

Energy lost to resistor.

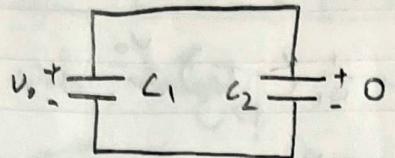

Two capacitor paradox.

Due to conservation of Q :

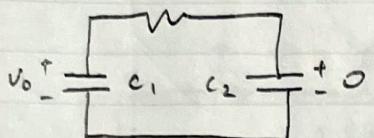

$$\text{At } t=0, Q = C_1 V_0$$



$$\text{At } t=\infty, Q = C_1 V_{\infty} + C_2 V_{\infty}.$$

$$V_{\infty} (C_1 + C_2) = C_1 V_0$$

$$V_{\infty} = V_0 \left(\frac{C_1}{C_1 + C_2} \right)$$



③ Effect of Cap values. "Charge sharing"

C_1 : large C_2 : small

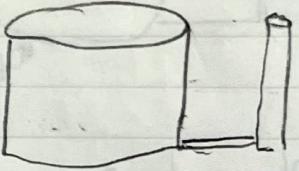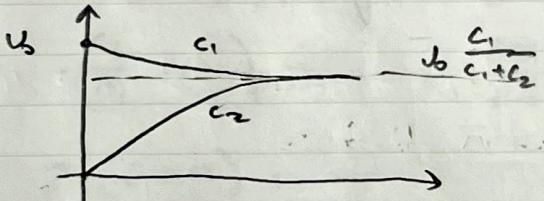



water analogy
(don't need much water to fill C_2)

C_1 : small C_2 : large

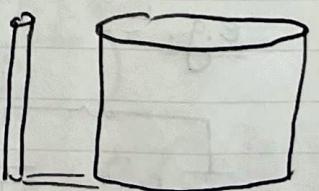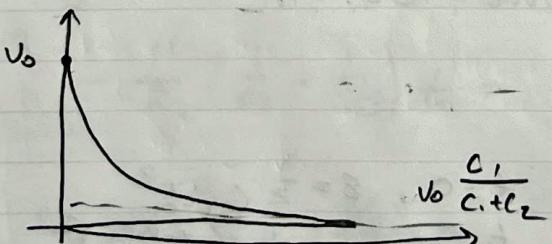


(Need lots of water to fill C_2)

④ what happens as $R_1 \downarrow$?

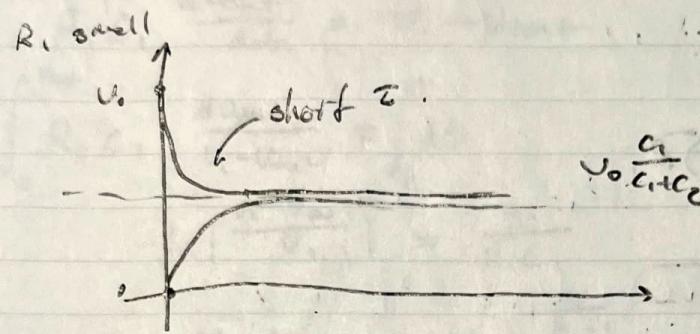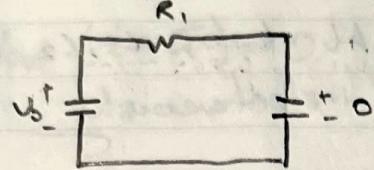


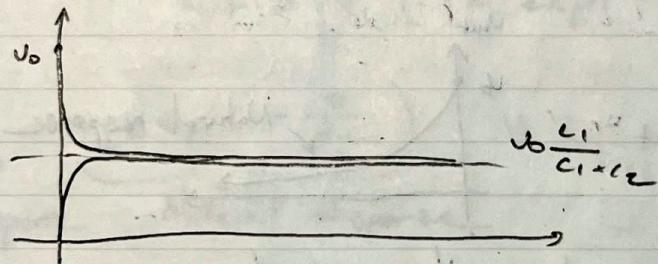
$$R_1 \rightarrow 0, \tau \rightarrow 0, \frac{V_0}{R_1} = I \rightarrow \infty$$




\Rightarrow Instantaneous change in V_{C_1} & V_{C_2}
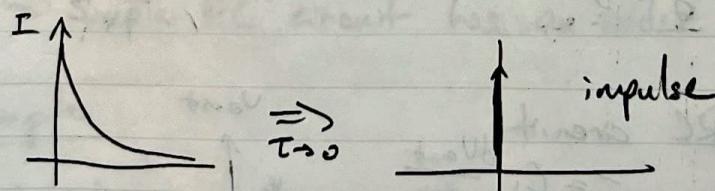
$$I = \frac{V_0}{R_1} e^{-\frac{t}{\tau}}$$





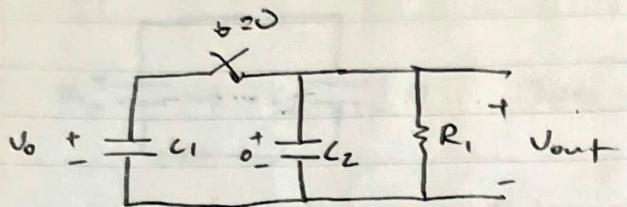

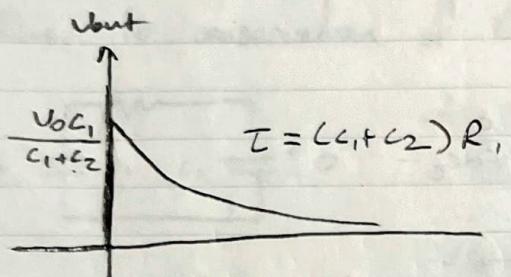At $t=0$; C_1, C_2 store charge
instantaneously



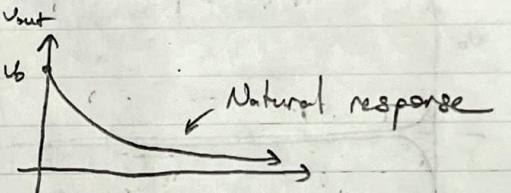
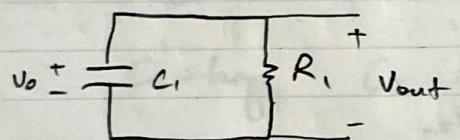
- Source-Free Circuits (Circuits with no explicit inputs)



- Driven Circuits: (Circuits with explicit inputs)

$$x(t) \rightarrow y(t)$$

- Simple Driven RCL circuit

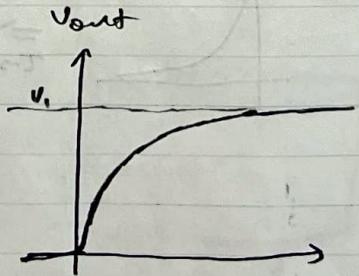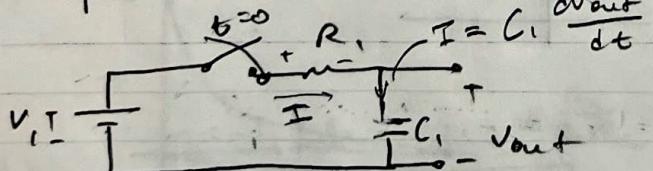

$$\text{KVL: } V_1 - I R_1 - V_{out} = 0$$

$$\left\{ \begin{array}{l} V_i = R.C_1 \frac{dV_{out}}{dt} + V_{out} \\ V_{out}(t=0^+) = 0 \quad (\text{Cap voltage cannot jump because } I < \infty) \end{array} \right.$$

$$R.C_1 \frac{dV_{out}}{dt} = V_i - V_{out}$$

$$\int_0^{V_{out}} R.C_1 \frac{dV_{out}}{V_i - V_{out}} = \int_0^t dt$$

$$-\ln \left| \frac{V_i - V_{out}}{V_i} \right| = \frac{t}{R.C_1}$$

$$V_i - V_{out} = V_i e^{-\frac{t}{R.C_1}}$$

$$V_{out} = \left[V_i \left(1 - \exp \left(-\frac{t}{R.C_1} \right) \right) \right] u(t)$$


$$V_i - \underbrace{V_i \exp \left(-\frac{t}{R.C_1} \right)}_{\text{Forced Response}} \underbrace{\exp \left(-\frac{t}{R.C_1} \right)}_{\text{Natural Response}}$$

Forced Response: Response that is left at $t = \infty$

- "Order" of a circuit = Order of a diff. equation
 \Rightarrow Simple RC circuit has an order of 1.


Example

Plot the current.

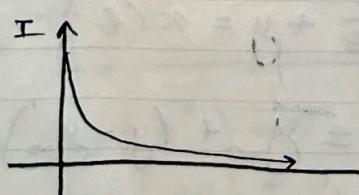

$$\begin{aligned} I(t) &= \frac{1}{R.C_1} V_i \exp \left(-\frac{t}{R.C_1} \right) \cdot C_1 \cdot u(t) \\ &= \frac{V_i}{R} \exp \left(-\frac{t}{R.C_1} \right) u(t) \end{aligned}$$

Property of Impulse function

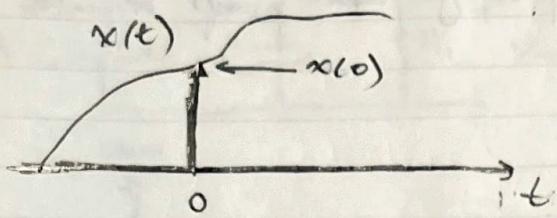

$$x(t)\delta(t) = x(0)\delta(t)$$

(Remember $\delta(t)=0 \forall t \neq 0$ and $\int_{-\infty}^{\infty} \delta(t) dt = 1$)

$$V_{out} = V_1 \left(1 - \exp\left(-\frac{t}{\tau}\right)\right) u(t)$$

$$\frac{d}{dt} V_{out} = \frac{V_1}{\tau} \exp\left(-\frac{t}{\tau}\right) u(t) + V_1 \left(1 - \exp\left(-\frac{t}{\tau}\right)\right) \delta(t)$$


because $\frac{d}{dt} u(t) = \delta(t)$

- derivative of step = impulse.

$$\frac{d}{dt} V_{out} = \frac{V_1}{\tau} \exp\left(-\frac{t}{\tau}\right) u(t) + V_1 (1 - \exp 0) \delta(t)$$


$$\frac{dV_{out}}{dt} = \frac{V_1}{\tau} \left(\exp\left(-\frac{t}{\tau}\right) u(t)\right) \text{ as expected.}$$

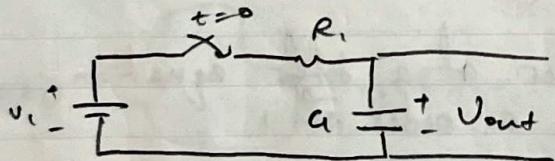• Shortcut Method for First-Order Circuits



$$\begin{cases} R, C, \frac{dV_{out}}{dt} + V_{out} = U_1 \\ V_{out}(t=0) = 0 \end{cases}$$

General First-Order System:

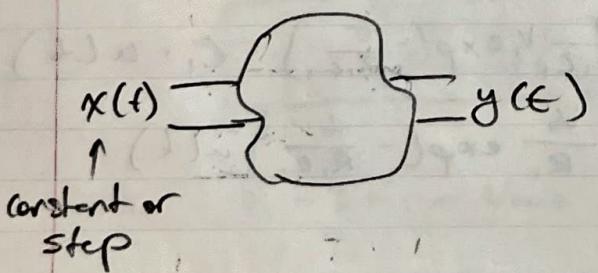

$$\alpha \frac{dy}{dt} + y = x(t)$$


$$y(t) = y_\infty + (y_0 - y_\infty) \exp\left(-\frac{t}{\tau}\right)$$

$$y_\infty = y(t=\infty)$$

Necessary that coefficient of
y is 1.

$$y_0 = y(t=0)$$

$$\tau = \alpha$$

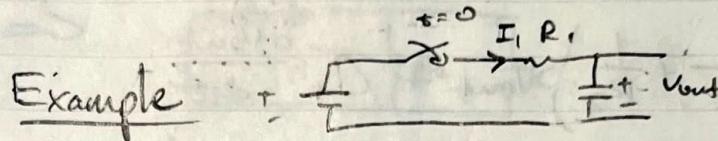


$$\begin{aligned} V_{\text{out}} &= V_{\text{out},\infty} + (V_{\text{out},0} - V_{\text{out},\infty}) \exp^{-\frac{t}{\tau}} \\ &= V_1 + (0 - V_1) \exp^{-\frac{t}{\tau}} \\ &= (V_1 - V_1 \exp^{-\frac{t}{\tau}}) u(t) \end{aligned}$$

Example

$$\text{Find } I_1(t) = ?$$


$$\begin{aligned} I_1(t) &= I_{1,\infty} + (I_{1,0} - I_{1,\infty}) \exp^{-\frac{t}{\tau}} \\ &= 0 + \left(\frac{V_1}{R_1} - 0\right) \exp^{-\frac{t}{\tau}} \\ &= \frac{V_1}{R_1} \exp^{-\frac{t}{\tau}} u(t) \end{aligned}$$

Example

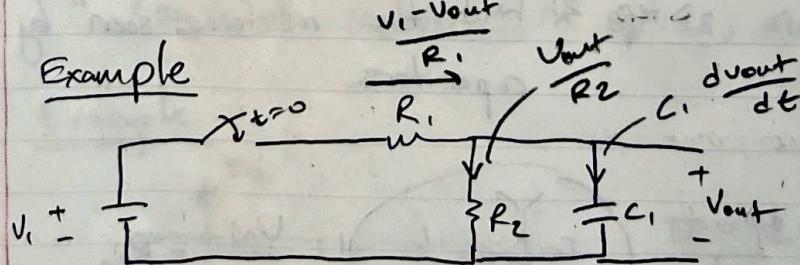

$$V_{\text{out}}(0^+) = 0$$
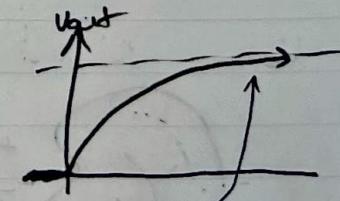
$$V_{\text{out}}(\infty) = V_1 \frac{R_2}{R_1 + R_2}$$



$V_{\text{out}} = \text{constant}$
 C_1 open circuit

$$V_1 + \frac{1}{\frac{1}{R_1 + R_2} + \frac{1}{C_1}}$$

To find τ : Write diff. eq.

$$KCL: \frac{V_1 - V_{out}}{R_1} = \frac{V_{out}}{R_2} + C_1 \frac{dV_{out}}{dt}$$

$$\frac{V_1}{R_1} = \left(\frac{1}{R_1} + \frac{1}{R_2} \right) V_{out} + C_1 \frac{dV_{out}}{dt}$$


$$- \frac{V_1}{R_1} \cdot \frac{R_1 R_2}{R_1 + R_2} = V_{out} + C_1 \left(\frac{R_1 R_2}{R_1 + R_2} \right) \frac{dV_{out}}{dt}$$

$$\Rightarrow \tau = \frac{R_1 R_2}{R_1 + R_2} C_1$$

Using $y(t) = y_{\infty} + (y_0 - y_{\infty}) e^{-\frac{t}{\tau}}$ as the solution:

$$V_{out} = \frac{R_2}{R_1 + R_2} V_1 \left(1 - e^{-\frac{t}{\tau}} \right) u(t)$$

Finding τ by inspection:

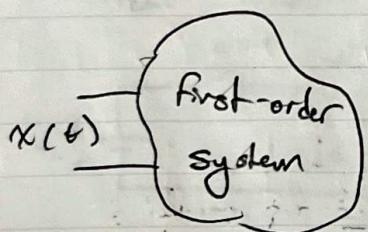


Step 1: Set all independent sources and initial conditions to 0.

Step 2: Find the resistance "seen" by the capacitors.






take cap out.
⇒

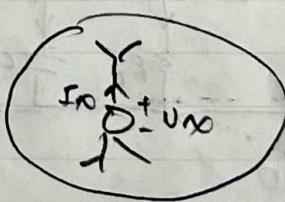

$$\frac{V_R}{I_R} = R_{eq}$$

Step 3: $\tau = R_{eq} C$.

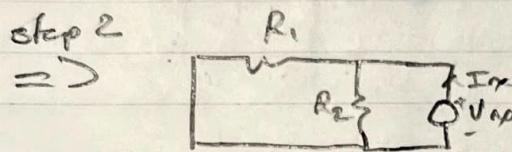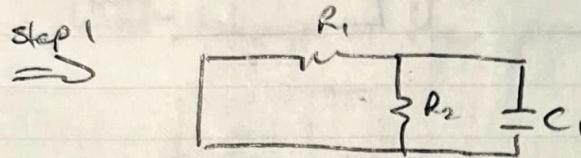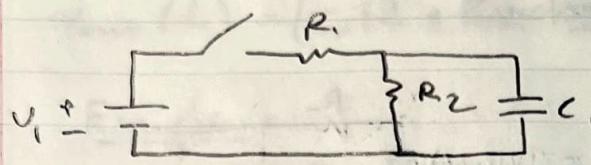


$$R_{eq} = R_1 \parallel R_2$$

$$= \frac{R_1 R_2}{R_1 + R_2}$$


$$T = C_1 \frac{R_1 R_2}{R_1 + R_2}$$

Example

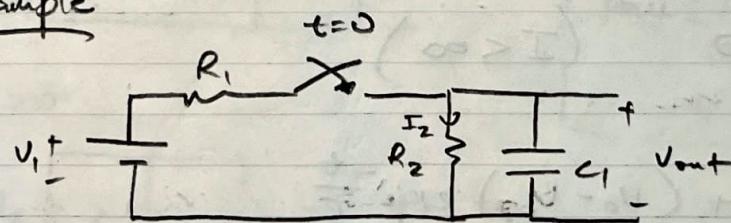


Vout same as in previous example
(switch & resistor in series, swap did nothing)

Example


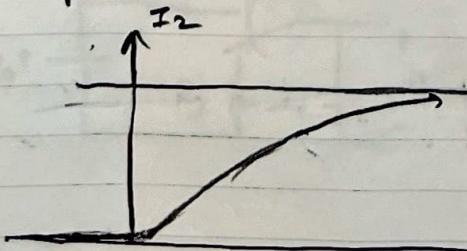


$$\frac{V_1 R_2}{R_1 + R_2}$$

- Note on switches & step functions

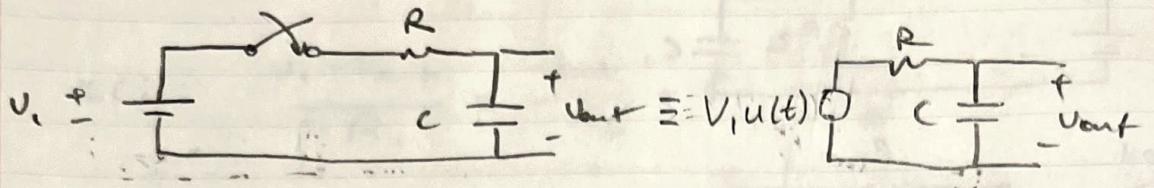


Example

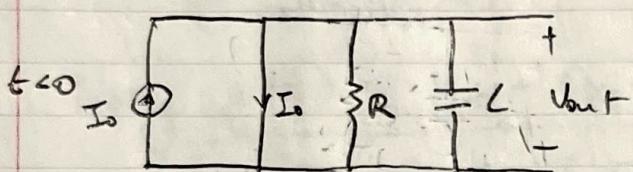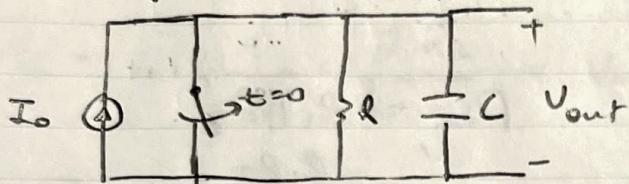

I_0 flows entirely through the switch ($V_{out} = 0$).

$$V_{out}(t=0^+) = 0 \quad (I < \infty)$$
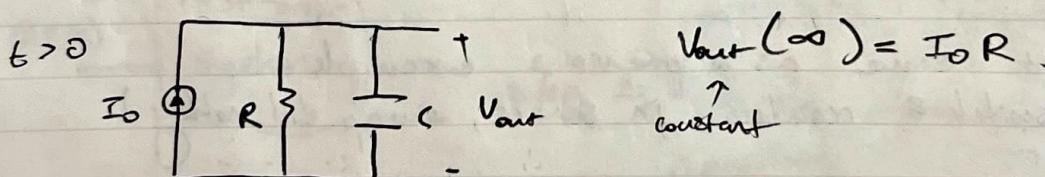
$$V_{out}(t) = V_\infty + (V_0 - V_\infty) \exp^{-\frac{t}{\tau}}$$




τ calculation:

$$\frac{1}{R} \cdot C \frac{1}{T} \Rightarrow \tau = RC.$$

$$V_{out}(t) = (I_0 R + (0 - I_0 R) \exp^{-\frac{t}{RC}}) u(t)$$

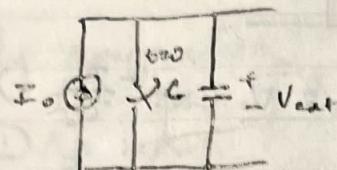Example

What happens in the previous example if $R \rightarrow \infty$?




$$V_{out}(0^-) = 0$$

$$V_{out}(0^+) = 0$$

$$V_{out}(t) = \frac{1}{C} \int_0^t I_0 dt = \frac{I_0 t}{C} u(t)$$

Example

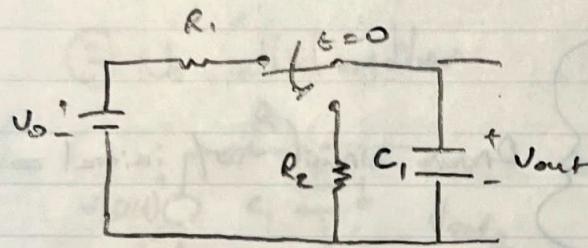


$$V_{out}(t < 0) = V_0$$


$$V_{out}(t = 0^+) = V_0$$

$$\begin{aligned} V_{out}(t > 0) &= V_0 \exp(-\frac{t}{R_1 C_1}) \\ &= V_0 \exp(-\frac{t}{R_2 C_1}) \end{aligned}$$

$t > 0$

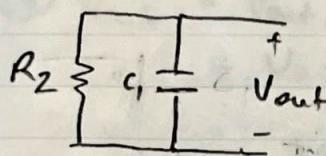

Example

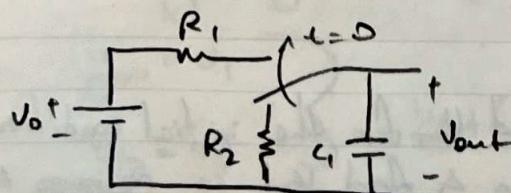


$$V_{out}(t < 0) = 0$$

$$V_{out}(t = 0^+) = 0$$

$$V_{out}(t > 0) = V_0 \left(1 - \exp\left(\frac{-t}{R_1 C_1}\right)\right)$$


$$V_{out}(t) = V_0 \left(1 - \exp\left(\frac{-t}{R_1 C_1}\right)\right) u(t)$$

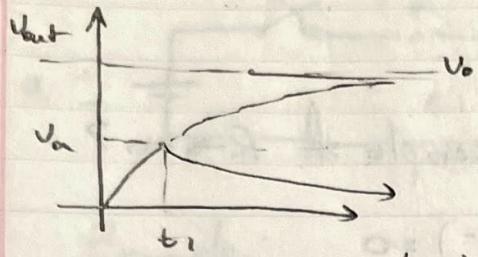At $t = t_1$, switch goes back to position 1.




$$V_a = V_o \left(1 - \exp^{-\frac{t_1}{R_1 C_1}}\right)$$

$t > t_1$:

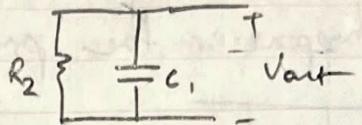

$$\begin{aligned} V_{out} &= V_a \exp^{-\frac{t-t_1}{R_2 C_1}} \\ &= V_a \exp^{-\frac{t}{R_2 C_1}} \end{aligned}$$

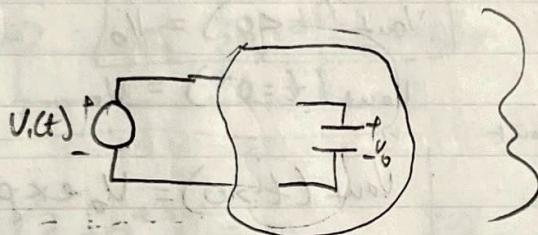How do we analyze a driven circuit w/ an initial condition?



Driven circuit w/ initial condition



Method 1: Solve the diff. eq. w/ the initial condition (\Rightarrow)

$$\begin{aligned} U_{in} + \text{---} &\quad I = C_1 \frac{dV_{out}}{dt} \\ &\quad \left\{ \begin{array}{l} U_{in} = R_1 C_1 \frac{dV_{out}}{dt} + V_{out} \\ V_{out}(0^+) = V_0 \end{array} \right. \end{aligned}$$

Method 2: Use superposition


- ① Assume no input & find V_{out} for the initial condition
- ② Assume no initial condition & find V_{out} in response to input
- ③ Add the two responses.

Example

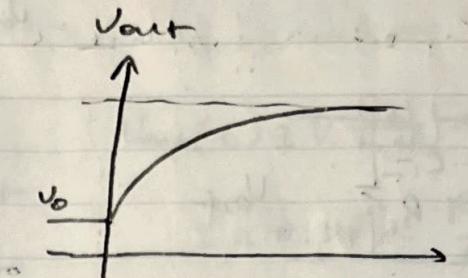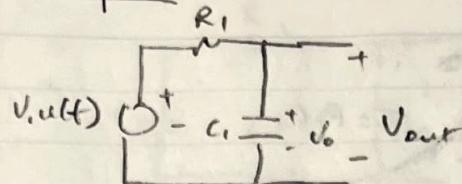


Apply superposition:

① No input:

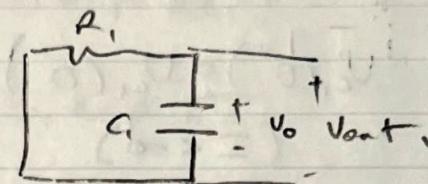

$$V_{out,1} = V_0 \exp\left(-\frac{t}{R_1 C_1}\right)$$

② No initial condition

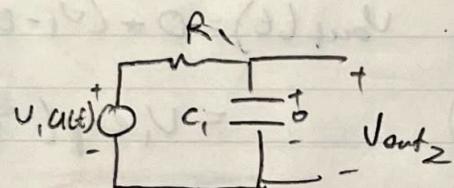

$$V_{out,2} = V_1 \left(1 - \exp\left(-\frac{t}{R_1 C_1}\right)\right)$$

$$\begin{aligned} \textcircled{3} \quad V_{out} &= V_{out,1} + V_{out,2} \\ &= V_0 \exp\left(-\frac{t}{\tau}\right) + V_1 \left(1 - \exp\left(-\frac{t}{\tau}\right)\right) \end{aligned}$$




$$\tau = R_1 C_1, \quad t > 0$$

$$\text{Alternatively: } y(t) = y_\infty + (y_0 - y_\infty) \exp^{-\frac{t}{\tau}}$$

$$\left. \begin{array}{l} y_\infty = V_1 \\ y_0 = V_0 \end{array} \right\} \quad V_{out}(t) = V_1 + (V_0 - V_1) \exp^{-\frac{t}{\tau}}$$

$\tau = R_1 C_1$


Example

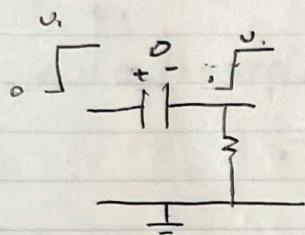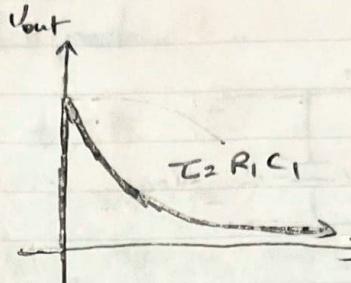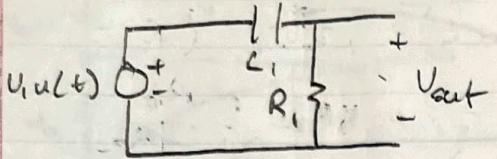

$$V_{C_1}(0^+) = V_{C_1}(0^-) = 0 \\ (I < \infty)$$

$$y_\infty = 0, \quad y_0 = U_1$$


$$\tau:$$

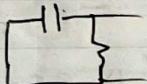



$$\tau = R_1 C_1$$

$$V_{out}(t) = 0 + (U_1 - 0) \exp(-\frac{t}{\tau}) \\ = U_1 \exp(-\frac{t}{\tau}) u(t).$$


Example

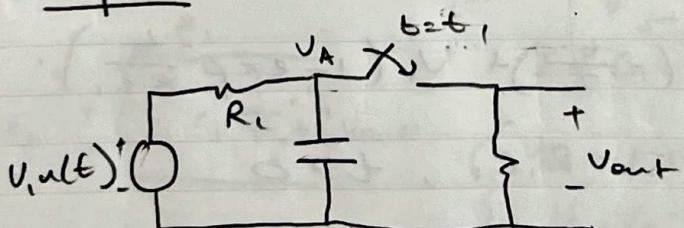
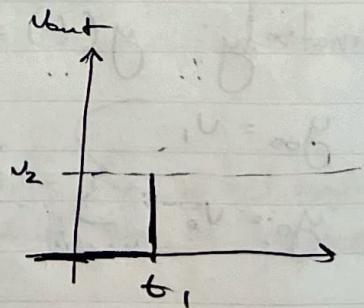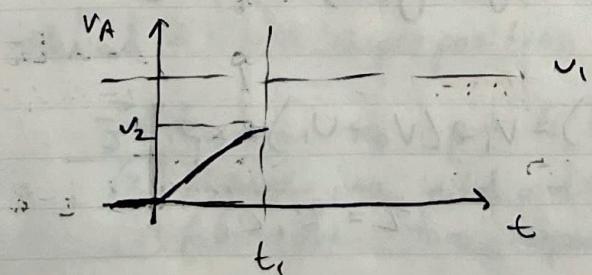
$$V_{out}(t < 0) = 0 \\ V_{out}(0^+) = 0$$



$t > t_1$

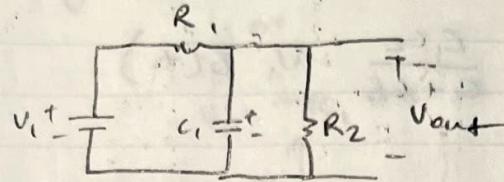

$$V_{\text{out}}(t) = V_1 \frac{R_2}{R_1 + R_2} + \left(V_2 - V_1 \frac{R_2}{R_1 + R_2} \right) e^{-\frac{t-t_1}{\tau}}$$

$$\tau = R_1 \| R_2 = \frac{R_1 R_2}{R_1 + R_2}$$




$$t < t_1: V_A = (V_1 - V_1 e^{-\frac{t-t_1}{R_1 C_1}}) u(t)$$

$$\Rightarrow V_2 = V_A(t_1) = V_1 - V_1 e^{-\frac{t_1}{R_1 C_1}}$$

Example




Part a)

$$V_{\text{in}} = V_1 u(t)$$

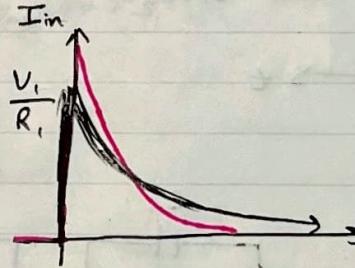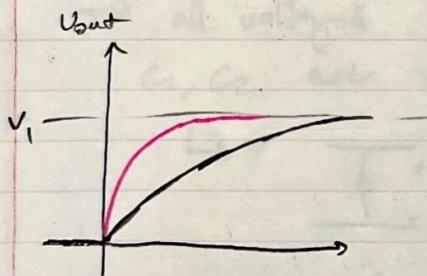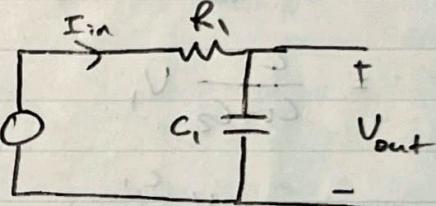


$$R_2 \rightarrow 0$$

Part b)

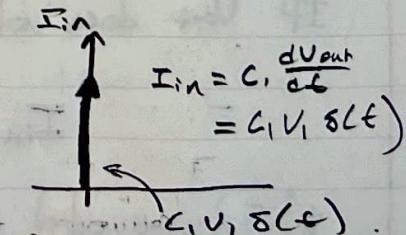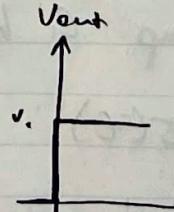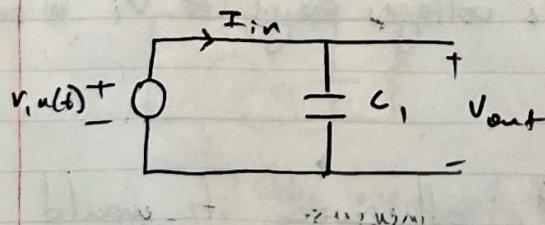

$$I_{\text{in}} = C_1 \frac{dV_{\text{out}}}{dt} = C_1 V_1 \delta(t)$$


Part c) (Capacitive Voltage divider)

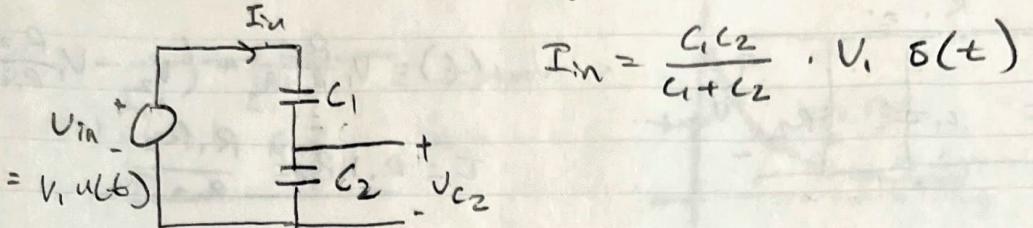


$$V_{C2} = \frac{1}{C_2} \int_0^t I dt$$

$$= \frac{1}{C_2} \int_0^t \frac{C_1 C_2}{C_1 + C_2} V_i \delta(t)$$

$$= \frac{C_1}{C_1 + C_2} V_i$$

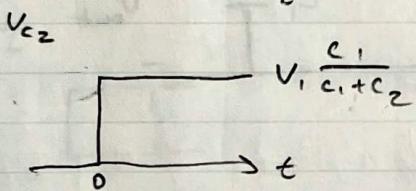

Example

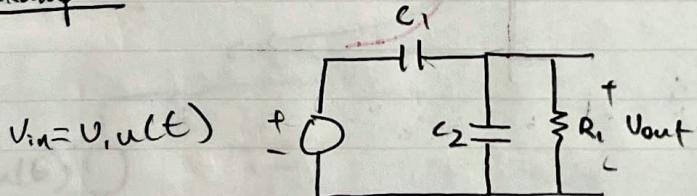

If V_{out} does not jump: C_1 has a voltage change of V_i in zero time,

$$I_{in} \propto \delta(t)$$

* I_{in} cannot flow through R_1 ; otherwise it would create infinite voltage

\Rightarrow impulse must flow through C_2


Charge delivered to R_1 from 0^- to 0^+

$$\int_{0^-}^{0^+} I_{R_1} dt = 0$$

↑
Finite

\Rightarrow Only delivered to C_1, C_2
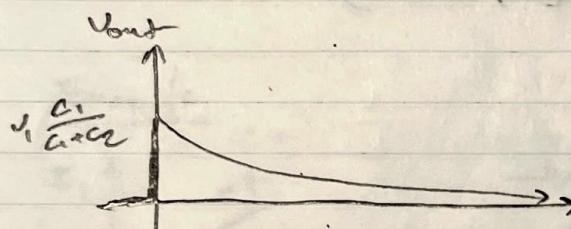
$$V_{C_2}(0^+) = V_i \frac{C_1}{C_1 + C_2}$$




If all voltages become constant at $t = \infty$,
 C_1, C_2 are open

$$\xrightarrow{\quad} \frac{d}{dt} v_{out} = 0$$

Why is system of first order?

$$t < 0 \Rightarrow v_{in} = 0$$

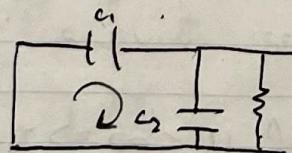


$\xrightarrow{\quad}$ Only one initial condition can be applied independently.

\Rightarrow first order system.

$$y_{\infty} = 0, \quad y_0 = V_1 \frac{c_1}{c_1 + c_2}$$

T : set indep. sources to 0.

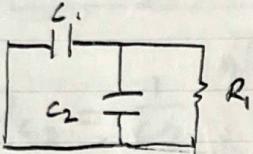


$$T = R \cdot (C_1 + C_2)$$


$$V_{out}(t) = V_1 \frac{C_1}{C_1 + C_2} \exp\left(-\frac{t}{T}\right) u(t)$$

Inductors


Derated:

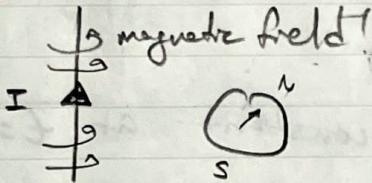

Faraday:

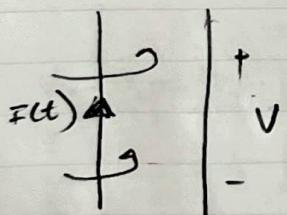


Inductor Basics:

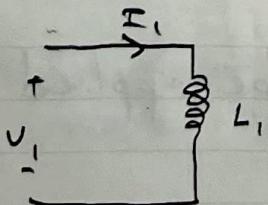

$$V_1 = L_1 \frac{dI_1}{dt}$$

if $V_1 < \infty \Rightarrow I_1$ cannot jump in zero time

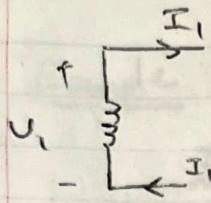If I_1 is constant
 $\Rightarrow V_1 = 0$.
 $\Rightarrow L_1 \equiv \text{short}$





$$V_1 = -L \frac{dI_1}{dt}$$

To find the current of an inductor:


$$I_1 = \frac{1}{L_1} \int V_1 dt$$

One more point: Initial condition: $I_1(0)$


Example

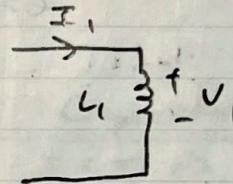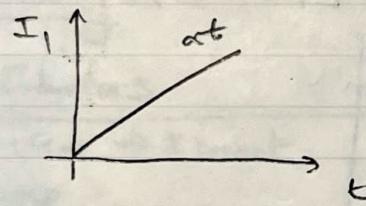


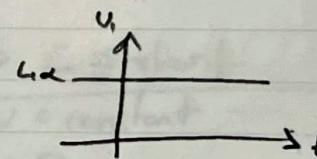
$$V_1 = L_1 \frac{dI_1}{dt} = L_1 \alpha$$





Example

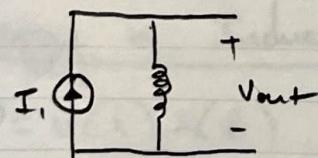

$$V_{out} = L \frac{dI}{dt}$$

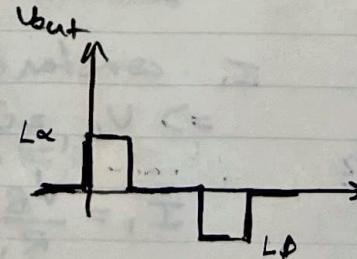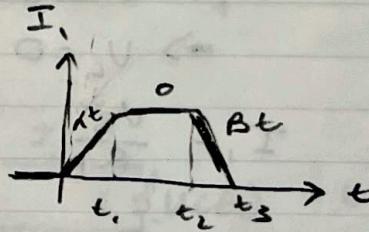


Example

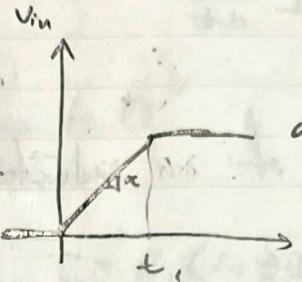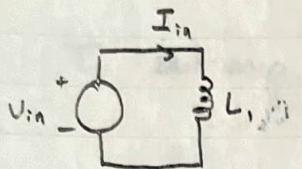


$$I_{in} = \frac{1}{L_1} \int_0^{t_1} \alpha t \, dt \quad t \in (0, t_1)$$

$$= \frac{\alpha t_1^2}{2L_1}$$

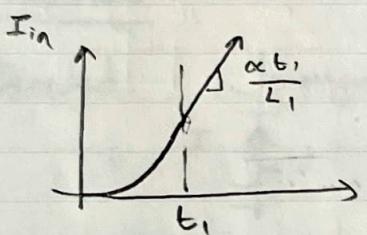

$$t > t_1: \frac{1}{L_1} (\alpha t_1) t - t_1$$

Example

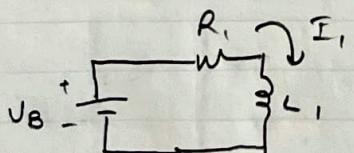


I_1 is constant

$$\Rightarrow V_{L_1} = 0$$

$$I_1 = \frac{V_B}{R_1}$$

Example

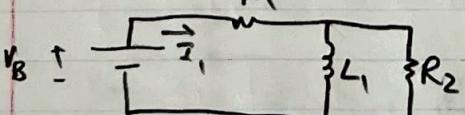

I_1 constant

$$\Rightarrow V_{L_1} = 0 \Rightarrow V_{R_2} = 0$$


$$I_1 = \frac{V_B}{R_1} \text{ (all of } I_1 \text{ flows through } L_1\text{)}$$

Example

Diagram: A circuit diagram showing an inductor L_1 with voltage v_B and current I_1 . The initial condition is $t=0^+$.

$$v_B = \begin{cases} 0 & t < 0 \\ \text{constant} & t = 0^+ \\ \frac{1}{L_1} \int v_B dt & t > 0 \end{cases}$$

$$= \frac{1}{L_1} v_B t.$$

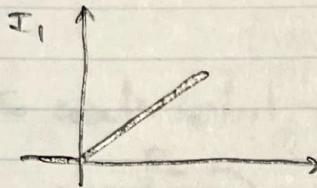

Summary

Inductors

If $V < \infty \Rightarrow I$ cannot jump

$$I = 0 \Rightarrow L \equiv \text{open}$$

If $I = \text{constant}$

$$\Rightarrow V_L = 0$$

$\Rightarrow L \equiv \text{short}$

Capacitors

If $I < \infty \Rightarrow V$ can't jump

$$V = 0 \Rightarrow C \equiv \text{short}$$

If $V = \text{constant}$

$$\Rightarrow I_L = 0$$

$\Rightarrow C \equiv \text{open}$

Energy in Inductors

$$P = V(t) I(t)$$


$$\boxed{\int_{t_1}^{t_2} V(t) I(t) dt = L \frac{dI}{dt}}$$

$$\Sigma = \int_0^t P(t) dt$$

$$= \int_0^t L \frac{dI}{dt} \cdot I dt$$

$$= \boxed{\frac{1}{2} L I^2(t)}$$

Inductors in series

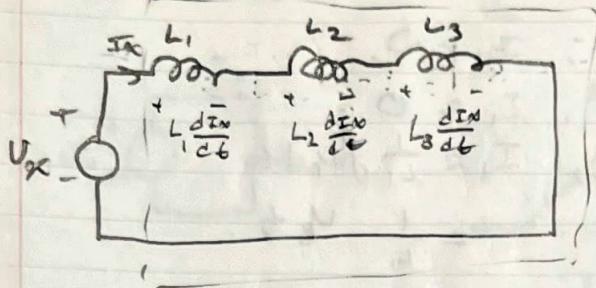


$$V_x = L_1 \frac{dI_x}{dt} + L_2 \frac{dI_x}{dt} + L_3 \frac{dI_x}{dt}$$

$$U_x = (L_1 + L_2 + L_3) \frac{dI_x}{dt}$$

$$L_{eq} = L_1 + L_2 + L_3 + \dots$$

Inductors in parallel

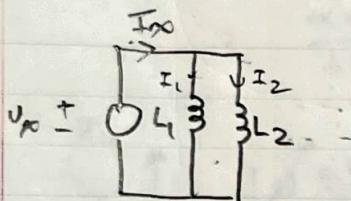


$$I_1 = \frac{1}{L_1} \int V_x dt$$

$$I_2 = \frac{1}{L_2} \int V_x dt$$

$$I_x = \frac{1}{L_{eq}} \int V_x dt$$

$$I_x = I_1 + I_2 \Rightarrow \frac{1}{L_{eq}} = \frac{1}{L_1} + \frac{1}{L_2} + \dots$$

Simple RL circuits (source-free)

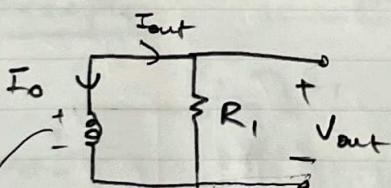

$$I_{out}(\infty) = 0$$

$$V_{out}(\infty) = 0$$


Find I_{out} first:

$$\left\{ -L_1 \frac{dI_{out}}{dt} = I_{out} R_1 \right.$$

$$\left. I_{out}(0^+) = -I_{out0} \right.$$

$$\frac{L_1}{R_1} \frac{dI_{out}}{dt} + I_{out} = 0$$

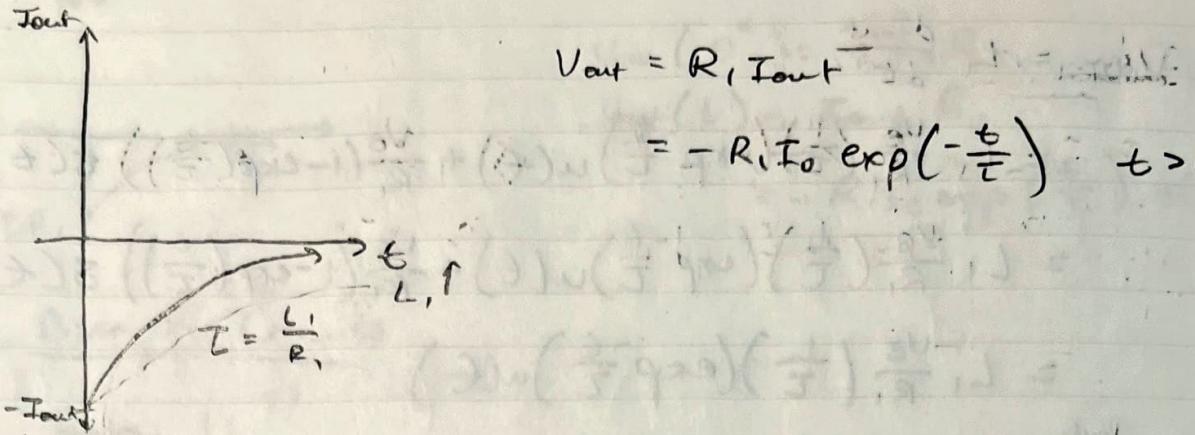
$$I_{out}(t) = -I_{out0} \exp\left(-\frac{t}{\tau}\right), \quad \tau = \frac{L_1}{R_1}$$



$$V_{out} = R_1 I_{out}$$


$$= -R_1 I_0 \exp\left(-\frac{t}{\tau}\right) \quad t > 0$$

To create initial condition:

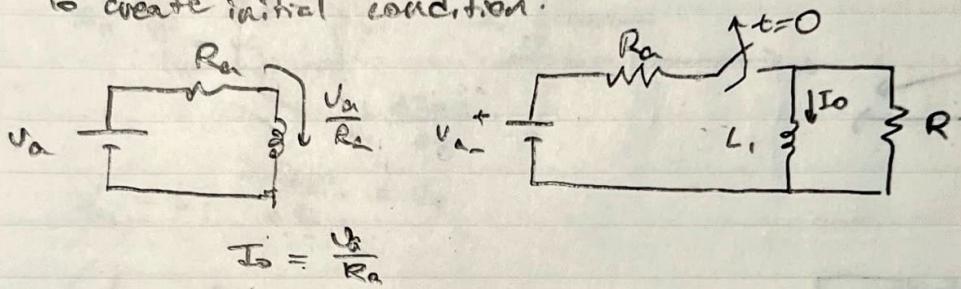


$$I_0 = \frac{V_a}{R_a}$$

Example

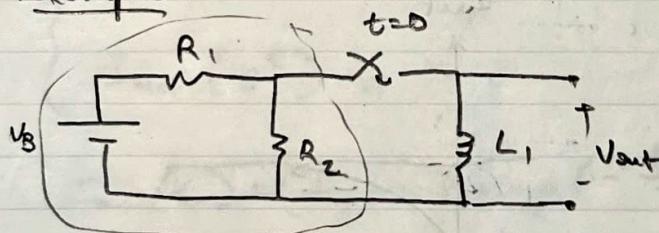

$t < 0$, $V_{out} = 0$ because switch is off.

$$I_{L1} = 0 \text{ at } t = 0^-$$

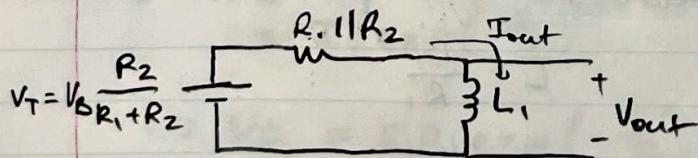

$$I_{out}(0^+) = 0$$

$$I_{out}(\infty) = \frac{V_B}{R_1}$$

$\hookrightarrow L_1$ shorts R_2 .

$$I_{out} = \frac{V_B}{R_1} \left(1 - \exp\left(-\frac{t}{\tau}\right) \right) u(t)$$


$$\tau = \frac{L_1}{R_1 || R_2}$$

$$V_{out} = L_1 \frac{dI_{out}}{dt}$$


$$= L_1 \frac{V_B}{R_1} \left(\frac{1}{C} \right) \left(\exp^{-\frac{t}{C}} \right) u(t) + \frac{V_B}{R_1} \left(1 - \exp(-\frac{t}{C}) \right) \delta(t)$$

$$= L_1 \frac{V_B}{R_1} \left(\frac{1}{C} \right) \left(\exp^{-\frac{t}{C}} \right) u(t) + \frac{V_B}{R_1} \left(1 - \exp(-\frac{t}{C}) \right) \delta(t)$$


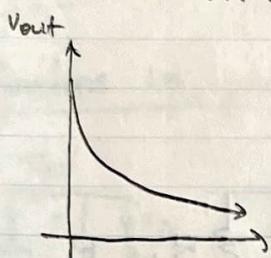
$$= L_1 \frac{V_B}{R_1} \left(\frac{1}{C} \right) \left(\exp^{-\frac{t}{C}} \right) u(t)$$



Example

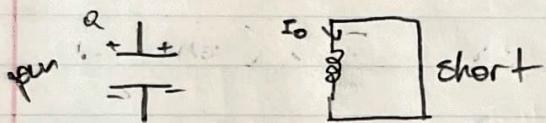


Example

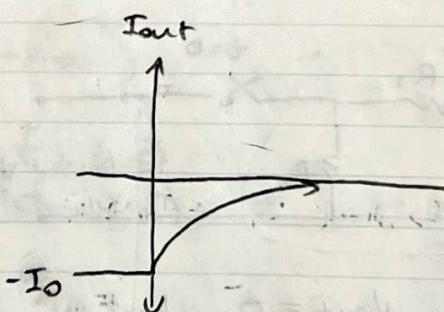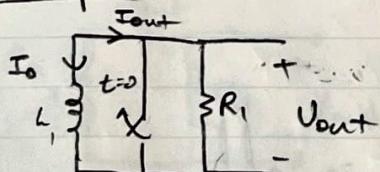


$$t < 0 : I_{out} = -I_o$$

$$I_{out}(t) = -I_o \exp(-\frac{t}{C}) \quad t > 0$$

$$t > 0 :$$

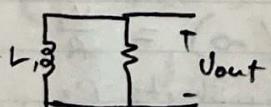


$$C = \frac{L_1}{R_1}$$

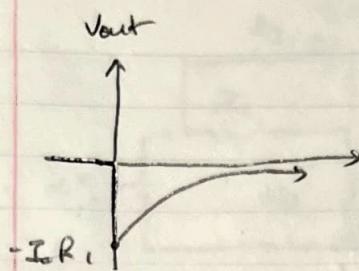


$$\begin{aligned}V_{\text{out}}(0^+) &= -I_0 R_1 \\V_{\text{out}}(t) &= I_{\text{out}} R_1 \\&= -R_1 I_0 \exp\left(\frac{t}{\tau}\right) u(t)\end{aligned}$$

Driven RL Circuits

Topology 1:

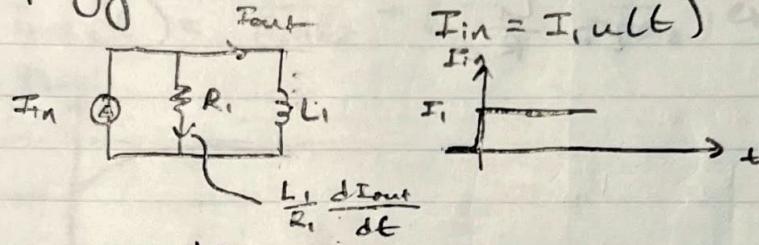

$$I_{\text{in}} = I_1 u(t)$$

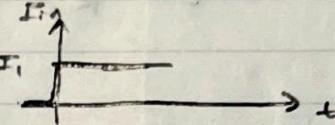

$$V_{L_1} = L_1 \frac{dI_{\text{out}}}{dt} = V_{R_1}$$

$$\left\{ \begin{array}{l} \frac{L_1}{R_1} \cdot \frac{dI_{\text{out}}}{dt} + I_{\text{out}} = I_1 u(t) \quad : \quad I_{\text{out}}(\infty) = I_1 \\ I_{\text{out}}(0^+) = 0 \end{array} \right.$$


$$I_{\text{out}}(t) = (I_1 - I_1 \exp(-\frac{t}{\tau})) u(t)$$

$$\tau = \frac{L_1}{R_1}$$

$$\begin{aligned}I_{R_1} &= I_1 u(t) - I_{\text{out}}(t) \\&= I_1 \exp(-\frac{t}{\tau})\end{aligned}$$

$$\Rightarrow V_{R_1} = I_1 R_1 \exp(-\frac{t}{\tau})$$


Topology 2:

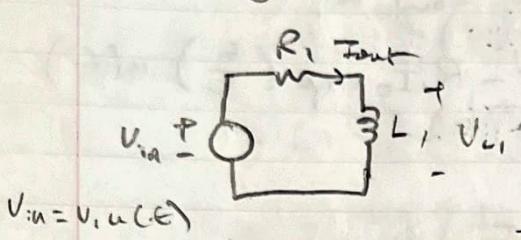


$$I_{out}(t < 0) = 0$$
$$I_{out}(0^+) = 0$$
$$I_{out}(\infty) = \frac{V_{in}}{R_1}$$

$$I_{out}(t) = \frac{V_{in}}{R_1} \left(1 - \exp\left(-\frac{t}{T}\right) \right) u(t)$$

$$T = \frac{L_1}{R_1}$$

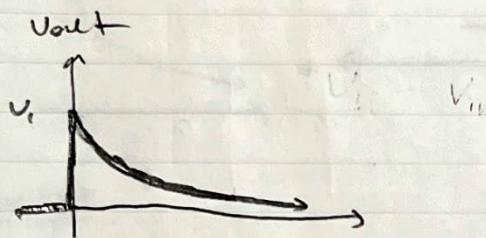

Example

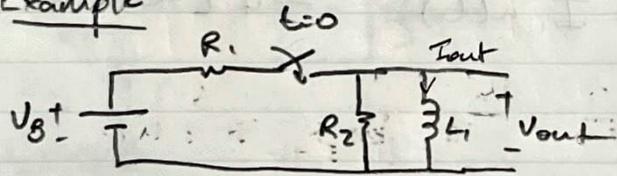


$$I_{out}(0^+) = 0$$
$$I_{out}(\infty) = \frac{V_B}{R_1}$$

$$T = \frac{L_1}{R_1 || R_2}$$

$$I(t) = \frac{V_B}{R_1} \left(1 - \exp\left(-\frac{t}{T}\right) \right) u(t)$$

$$V_{out} = L_1 \frac{dI}{dt}$$
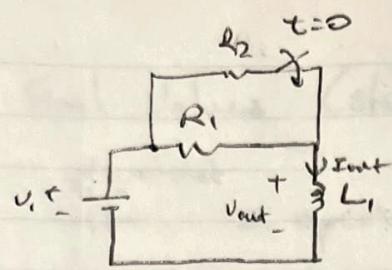
$$= L_1 \cdot \frac{V_B}{R_1} \cdot \left(\frac{1}{T} \right) \exp\left(-\frac{t}{T}\right) u(t)$$




$$I_{out}(0^-) = \frac{V_i}{R_1}$$

$$I_{out}(0^+) = \frac{V_i}{R_1}$$

$$I_{out}(\rightarrow) = \frac{V_i}{R_1||R_2}$$


$$t > 0: \tau = \frac{L_1}{R_1||R_2}$$

$$I_{out}(t) = \frac{V_i}{R_1||R_2} + \left(\frac{V_i}{R_1} - \frac{V_i}{R_1||R_2} \right) \exp\left(-\frac{t}{\tau}\right), t > 0$$

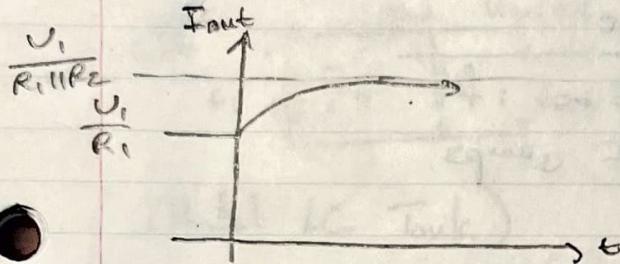

$$V_{out}(t) = L_1 \frac{dI_{out}}{dt}$$


$$= L_1 \left(-\frac{1}{\tau} \right) \left(\frac{V_i}{R_1} - \frac{V_i}{R_1||R_2} \right) \exp\left(-\frac{t}{\tau}\right) u(t)$$

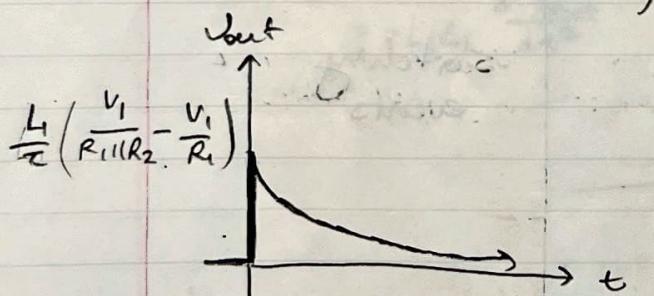

Summary

	R	C	L
Basic eq.	$V = IR$	$I = C \frac{dV}{dt}$	$V = L \frac{dI}{dt}$
Energy stored	—	$\frac{1}{2} CV^2$	$\frac{1}{2} LI^2$
Initial condition	—	V_0	I_0
Singularities	—	$I = \infty$ if V jumps	$V = \infty$ if I jumps

Observations

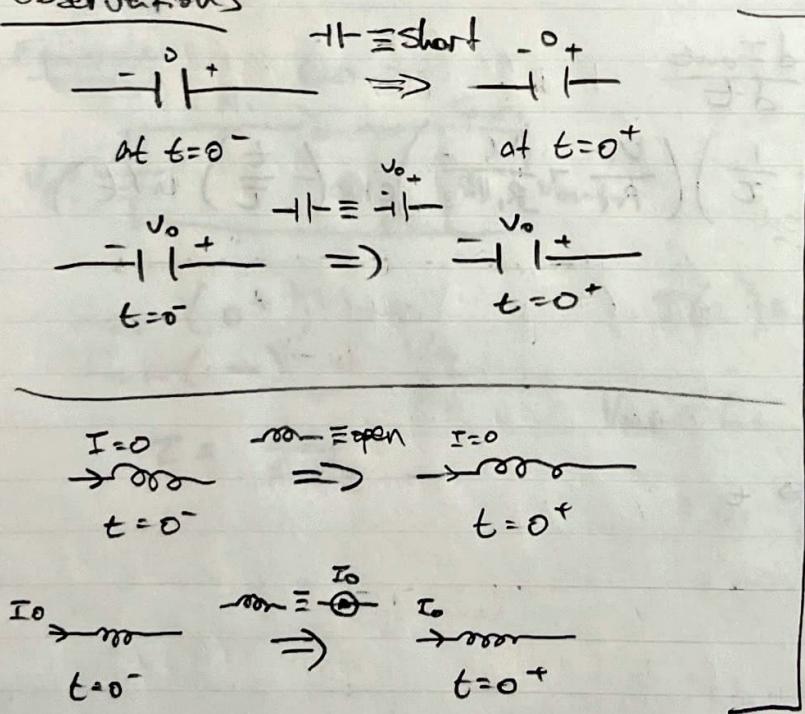

switching events

Final Values (Steady State)

$\frac{V}{+} = \text{constant}$


$\text{---} \parallel = \text{open}$

$I = \text{constant}$


$\text{---} \square = \text{short}$

RLC circuits

- A simple LC circuit

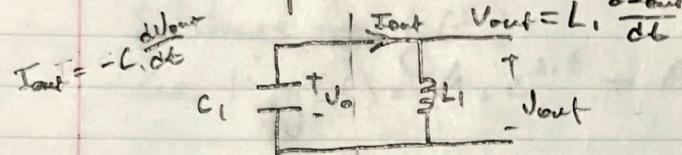

(Parallel LC Tank)

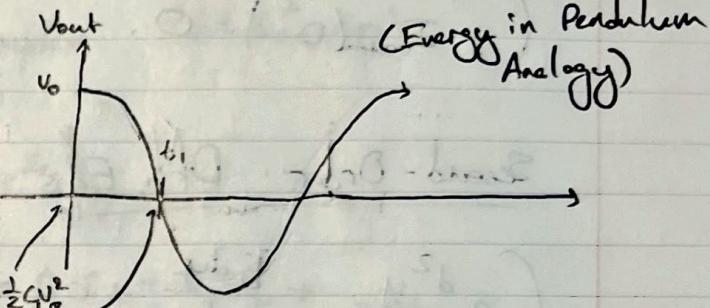


$$E_{\text{cap}} = \frac{1}{2} C_1 V_0^2$$

$$E_{\text{cap}} = 0$$

$$E_{\text{inductor}} = \frac{1}{2} L_1 I^2 = \frac{1}{2} C_1 V_0^2$$

$$I_{\text{out}} = -C_1 \left(L_1 \frac{d^2 I_{\text{out}}}{dt^2} \right)$$
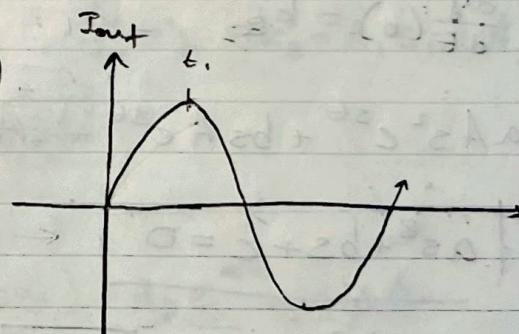
$$= -L_1 C_1 \frac{d^2 I_{\text{out}}}{dt^2}$$



Observations

At $t = t_1$, $\frac{dV_{\text{out}}}{dt} < 0 \Rightarrow I_{\text{out}} > 0$

$$\frac{dI_{\text{out}}}{dt} = 0 \Rightarrow V_{\text{out}} = 0$$

$$V_{out} = L_1 \frac{d I_{out}}{dt}$$

$$= L_1 \left(-C_1 \frac{d V_{out}}{dt} \right)$$

$$\left\{ \begin{array}{l} L_1 C_1 \frac{d^2 V_{out}}{dt^2} + V_{out} = 0 \\ V_{out}(0^+) = V_0 \\ I_{out}(0^+) = 0. \end{array} \right.$$

Second-Order Diff. Eqs.:

$$\left\{ \begin{array}{l} a \frac{d^2 y}{dt^2} + b \frac{dy}{dt} + c y = 0 \\ y(0) = k_1 \\ \frac{dy}{dt}(0) = k_2 \end{array} \right. \quad y(t) = A e^{st}$$

$$a A s^2 e^{st} + b s A e^{st} + c A e^{st} = 0$$

$$\boxed{as^2 + bs + c = 0} \quad \leftarrow \text{characteristic equation}$$

$$s = \frac{-b \pm \sqrt{b^2 - 4ac}}{2a}$$

Guess :

$$y(t) = A_1 e^{s_1 t} + A_2 e^{s_2 t}$$

$$y(0) = k_1 = A_1 + A_2$$

$$\frac{dy}{dt}(0) = k_2 = s_1 A_1 + s_2 A_2$$

$$as^2 + bs + c = 0, \quad s_{1,2} = \frac{-b \pm \sqrt{b^2 - 4ac}}{2a}$$

Three cases:

① $s_1 \neq s_2$, both are real ($b^2 - 4ac > 0$)

② $s_1 = s_2 = -\frac{b}{2a}$ ($b^2 - 4ac = 0$)

③ $s_1 \neq s_2$, both are complex ($b^2 - 4ac < 0$)

Solutions for $y(t)$:

$$\text{Case 1: } y(t) = A_1 e^{s_1 t} + A_2 e^{s_2 t},$$

$$k_1 = A_1 + A_2; \quad k_2 = A_1 s_1 + A_2 s_2$$

$$\text{Case 2: } y(t) = A_1 e^{s_1 t} + A_2 t e^{s_1 t}$$

$$y(0) = k_1 = A_1; \quad \frac{dy}{dt}(0) = k_2 = A_1 s_1 + A_2$$


$$\text{Case 3: } s_{1,2} = \underbrace{\left(\frac{-b}{2a}\right)}_{\alpha} \pm j \underbrace{\left(\frac{\sqrt{4ac-b^2}}{2a}\right)}_{\omega}$$

$$y(t) = A_1 e^{\alpha t} \cos(\omega t) + A_2 e^{\alpha t} \sin(\omega t)$$

$$y(0) = k_1 = A_1; \quad \frac{dy}{dt}(0) = k_2 = A_1 \alpha + A_2 \omega$$

$$\alpha = (0) \frac{2\pi \cdot b}{2\omega} = \omega$$

Ideal LC Tank

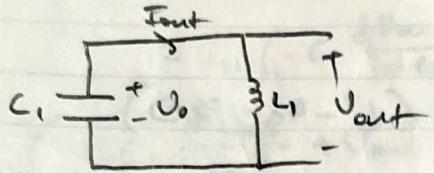

$$V_{\text{out}}(0^+) = V_0$$

$$I_L(0^+) = 0$$

$$I_{\text{out}} = -L_1 \frac{dV_{\text{out}}}{dt}, \quad V_{\text{out}} = L_1 \frac{dI_{\text{out}}}{dt}$$

$$V_{\text{out}} = -L_1 C_1 \frac{d^2 V_{\text{out}}}{dt^2}$$

$$L_1 C_1 \frac{d^2 V_{\text{out}}}{dt^2} + V_{\text{out}} = 0$$

characteristic

$$L_1 C_1 s^2 + 1 = 0$$

$$s_{1,2} = \pm \sqrt{-\frac{1}{L_1 C_1}}$$

$$= \pm j \sqrt{\frac{1}{L_1 C_1}}$$

$$V_{\text{out}}(t) = A_1 \cos \omega_1 t + A_2 \sin \omega_1 t \quad (\omega_1 = \sqrt{\frac{1}{L_1 C_1}})$$

$$V_{\text{out}}(0) = A_1 = V_0$$

$$0 = I_L(0^+) = I_{\text{out}}(0) = -C_1 \frac{dV_{\text{out}}}{dt}(0)$$

$$A_2 \omega_1 = \frac{dV_{\text{out}}}{dt}(0) = 0$$


$$A_2 = 0$$

$$\Rightarrow V_{\text{out}}(t) = V_0 \cos \omega_1 t \quad (\omega_1 = \sqrt{\frac{1}{L_1 C_1}})$$


$$T = 2\pi \sqrt{L_1 C_1}$$

$$\omega_1 = \frac{1}{L_1 C_1} \text{ "radian frequency"}$$
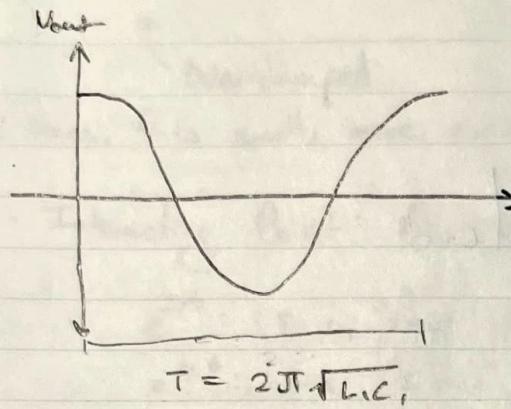
$$f_1 = \frac{1}{2\pi L_1 C_1} \text{ Hz}$$



Lossy LC Tank.

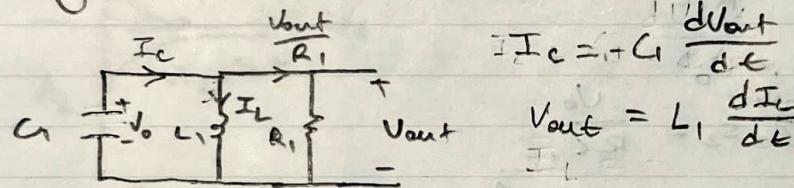

$$I_c = +C_1 \frac{dV_{out}}{dt}$$

$$V_{out} = L_1 \frac{dI_L}{dt}$$

$$I_L = I_c - \frac{V_{out}}{R_1} \Rightarrow V_{out} = L_1 \left(-C_1 \frac{d^2 V_{out}}{dt^2} - \frac{1}{R_1} \frac{dV_{out}}{dt} \right)$$

$$\left\{ L_1 C_1 \frac{d^2 V_{out}}{dt^2} + \frac{L_1}{R_1} \frac{dV_{out}}{dt} + V_{out} = 0 \right.$$

$$V_{out}(0^+) = U_0$$

$$I_L(0^+) = 0$$

$$L_1 C_1 s^2 + \frac{L_1}{R_1} s + 1 = 0$$

$$s^2 + \frac{1}{R_1 C_1} s + \frac{1}{L_1 C_1} = 0$$

$$s_{1,2} = \frac{-1}{2R_1 C_1} \pm \frac{\sqrt{(\frac{1}{R_1 C_1})^2 - 4 \cdot \frac{1}{L_1 C_1}}}{2}$$

$$s_{1,2} < 0 \Rightarrow \text{Decay}$$

Observation:
always negative,
dimension: Hz

$$\text{Case 1: } \frac{1}{R_1^2 C_1^2} > \frac{4}{L_1 C_1} \quad (R_1 < \frac{1}{2} \sqrt{\frac{L_1}{C_1}})$$

$$\Rightarrow V_{\text{out}} = A_1 e^{s_1 t} + A_2 e^{s_2 t}$$

$$V_{\text{out}}(0^+) = V_0 = A_1 + A_2$$


At $t=0^+$



$$\frac{V_0}{R_1} = I_C = -C \cdot \frac{dV_{\text{out}}}{dt} \Big|_{t=0^+}$$

$$\frac{dV_{\text{out}}}{dt} \Big|_{t=0^+} = -\frac{V_0}{R_1 C_1}$$

$$\frac{dV_{\text{out}}}{dt}(0) = -\frac{V_0}{R_1 C_1} = A_1 s_1 + A_2 s_2$$
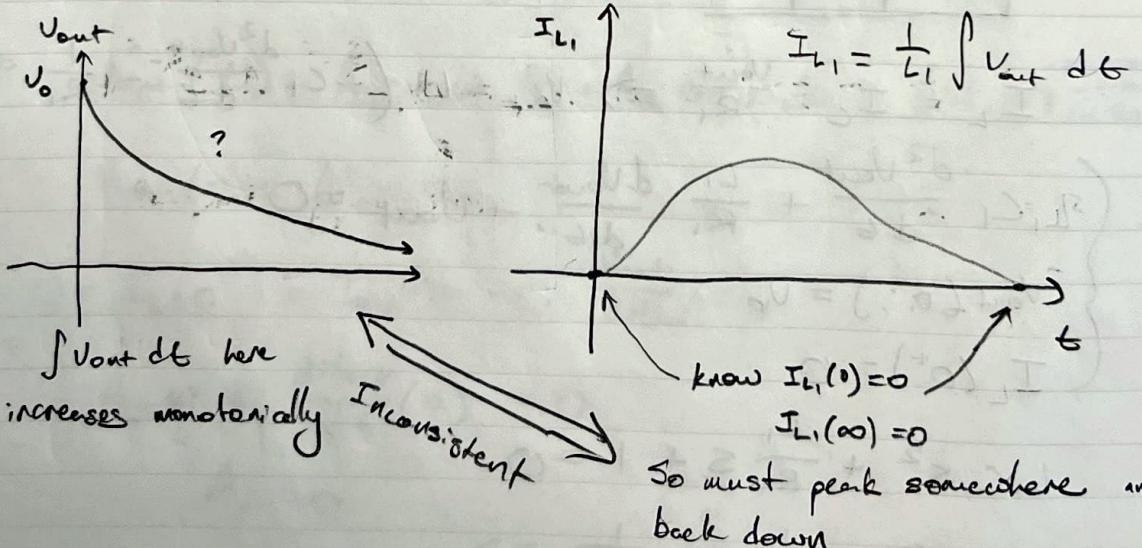
$$\Rightarrow \begin{cases} A_1 + A_2 = V_0 \\ A_1 s_1 + A_2 s_2 = -\frac{V_0}{R_1 C_1} \end{cases}$$



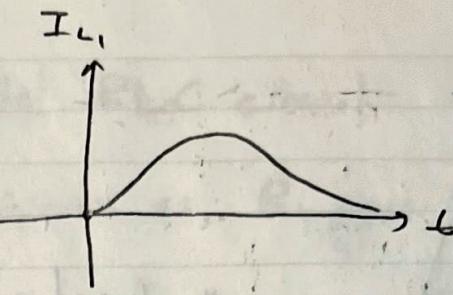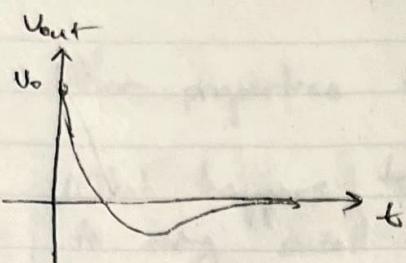


Over-damped

(Since R is small, more current leaks from LC tank)

- Interesting Point: $A_1 > 0, A_2 < 0$.

$e^{s_1 t}$: is a "fast" exp $(s_1 = -\frac{1}{2Rc_1} - \frac{1}{2}\sqrt{\frac{1}{R^2C_1^2} - \frac{4}{Lc_1}})$

$e^{s_2 t}$: is a "slow" exp $(s_2 = -\frac{1}{2Rc_1} + \frac{1}{2}\sqrt{\frac{1}{R^2C_1^2} - \frac{4}{Lc_1}})$

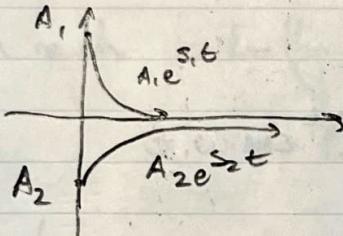


Case 2: $R_1 = \frac{1}{2}\sqrt{\frac{L_1}{C_1}}$ $\Rightarrow V_{out} = A_1 e^{s_1 t} + A_2 e^{s_2 t}$

$$s_1 = -\frac{1}{2R_1 C_1}$$

critically damped


$$\begin{cases} A_1 = V_0 \\ A_1 s_1 + A_2 = -\frac{V_0}{R_1 C_1} \end{cases}$$

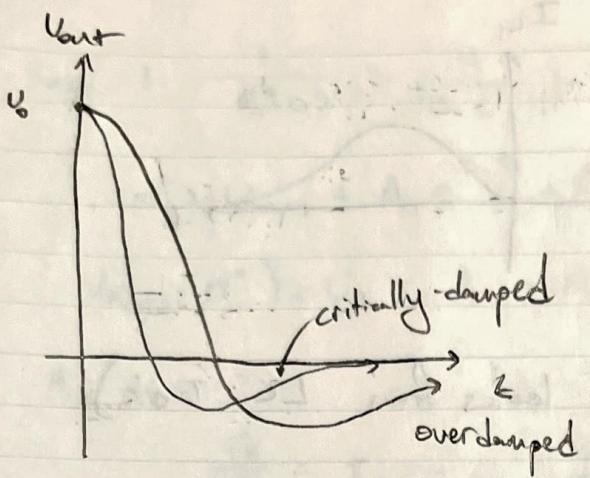

Case 3: $R_1 > \frac{1}{2} \sqrt{\frac{L}{C_1}} \Rightarrow$ roots are complex.

$$\zeta_{1,2} = \left(-\frac{1}{2R_1C_1} \right) \pm j \left(\frac{1}{2} \sqrt{\frac{4}{L_1C_1} - \frac{1}{R_1^2C_1^2}} \right)$$


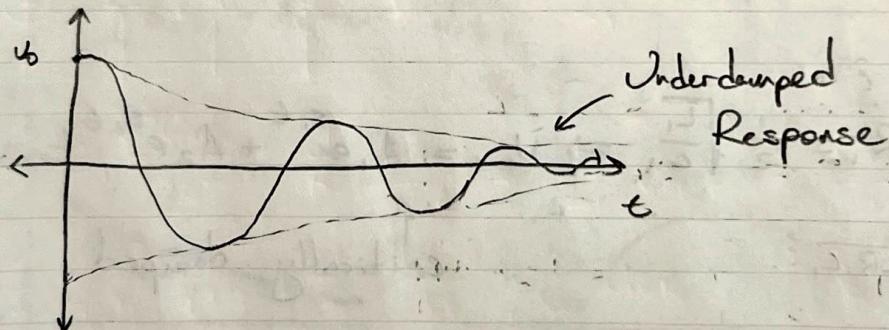
$$V_{out}(t) = A_1 e^{\alpha t} \cos \omega_1 t + A_2 e^{\alpha t} \sin \omega_1 t$$



$$\begin{cases} A_1 = V_0 \\ A_1 \alpha + A_2 \omega_1 = -\frac{V_0}{R_1 C_1} \end{cases}$$

- Other properties of Parallel RLC circuit

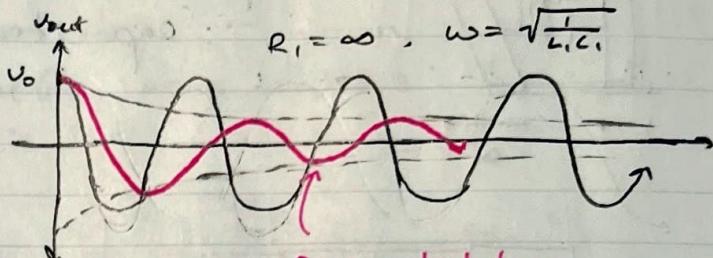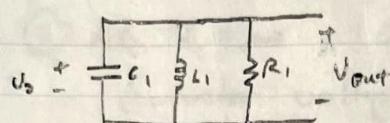What happens to the response as R_1 goes from ∞ to very small values?



Before $R_1 \approx \frac{1}{2\sqrt{L/C_1}}$, oscillations damped more and more...

$R_1 < \infty$ but large

$$(R_1 > \frac{1}{2\sqrt{L/C_1}})$$

$$\left(\omega = \frac{1}{2} \sqrt{\frac{1}{L/C_1} - \frac{1}{R^2 C^2}} \right)$$



$$\left(\omega < \sqrt{\frac{1}{L/C_1}} \right)$$

Then reach critically damped & over-damped
reach 0 faster

Example

1 oscillator

Periodic

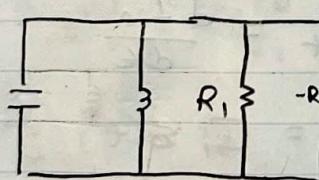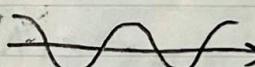


Electronic Circuit (Resistance $-R_1$)

models losses


$$R_{eq} = \frac{R_1(-R_1)}{R_1 - R_1} \rightarrow -\infty \Rightarrow \text{open circuit.}$$

- How do we measure capacitance?

e.g. Accelerometer

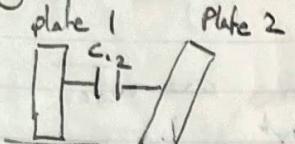

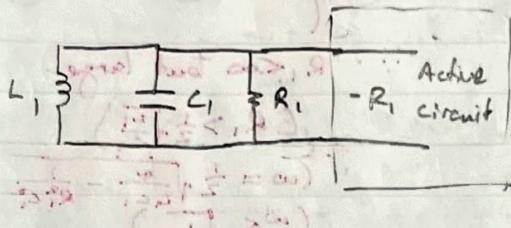Acceleration causes change in capacitance ...



Measure the change in frequency ($\omega = \frac{1}{\sqrt{L_1 C_1}}$).

- Driven Parallel RLC circuit

$$\text{I}_{in} \quad \begin{array}{c} \text{C}_1 \\ \parallel \\ \text{L}_1 \\ \parallel \\ \text{R}_1 \end{array} \quad + \quad \frac{\text{V}_{out}}{\text{R}_1} + \frac{1}{\text{L}_1} \int \text{V}_{out} dt + \text{C}_1 \frac{d\text{V}_{out}}{dt} = \text{I}_{in}$$

($\text{I}_{in} = \text{I}_1 u(t)$)

$$\text{C}_1 \frac{d^2 \text{V}_{out}}{dt^2} + \frac{1}{\text{R}_1} \frac{d\text{V}_{out}}{dt} + \frac{1}{\text{L}_1} \text{V}_{out} = \frac{d \text{I}_{in}}{dt}$$

$$- \text{C}_1 \frac{d^2 \text{V}_{out}}{dt^2} + \frac{1}{\text{R}_1} \frac{d\text{V}_{out}}{dt} + \frac{1}{\text{L}_1} \text{V}_{out} = \text{I}_1 \delta(t)$$

Case 1: Overdamped $\text{R}_1 < \frac{1}{2} \sqrt{\frac{\text{L}_1}{\text{C}_1}}$

$$(s_{1,2} = -\frac{1}{2\text{R}_1\text{C}_1} \pm \frac{1}{2} \sqrt{\frac{1}{\text{R}_1^2\text{C}_1^2} - \frac{4}{\text{L}_1\text{C}_1}})$$




$$\text{V}_{out} = (A_1 e^{s_1 t} + A_2 e^{s_2 t}) u(t)$$

Observations:

$$\begin{aligned} \textcircled{1} \quad V_{\text{out}}(0^+) &= 0 \\ I_L(0^+) &= 0 \end{aligned}$$

\textcircled{2} All of $I_u(t)$ flows through C_1 at $t=0^+$

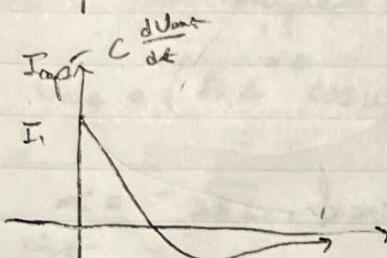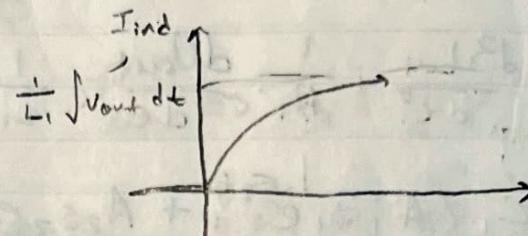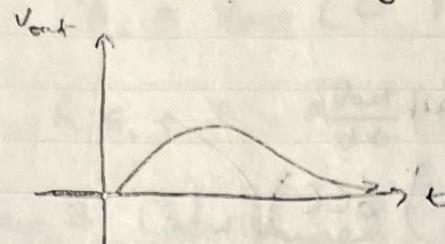\textcircled{3} At $t=\infty$, $I_u(t)$ flows through L ,
(inductor voltage is 0).



$$\begin{cases} V_{\text{out}}(0^+) = 0 = A_1 + A_2 \\ \left. \frac{dV_{\text{out}}}{dt} \right|_{t=0} = \frac{I_{C_1}(0^+)}{C_1} = \frac{I_1}{C_1} = A_1 s_1 + A_2 s_2 \end{cases}$$

Verifying diff. eq.:

$$\begin{aligned} \frac{dV_{\text{out}}}{dt} &= (A_1 s_1 e^{s_1 t} + A_2 s_2 e^{s_2 t}) u(t) + (A_1 + A_2) \delta(t) \\ &= (A_1 s_1 e^{s_1 t} + A_2 s_2 e^{s_2 t}) u(t) \end{aligned}$$

$$\begin{aligned} \frac{d^2 V_{\text{out}}}{dt^2} &= (A_1 s_1^2 e^{s_1 t} + A_2 s_2^2 e^{s_2 t}) u(t) + (A_1 s_1 + A_2 s_2) \delta(t) \\ &= (A_1 s_1^2 e^{s_1 t} + A_2 s_2^2 e^{s_2 t}) u(t) + \left(\frac{I_1}{C_1} \right) \delta(t) \end{aligned}$$

Note that when evaluating

$$C_1 \frac{d^2 V_{out}}{dt^2} + \frac{1}{R_1} \frac{dV_{out}}{dt} + \frac{1}{L_1} V_{out},$$

All parts of $\frac{d^2 V_{out}}{dt^2}$, $\frac{dV_{out}}{dt}$, V_{out} with $u(t)$ will add to 0. (They add up to characteristic equation)

$$C_1 \frac{d^2 V_{out}}{dt^2} + \frac{1}{R_1} \frac{dV_{out}}{dt} + \frac{1}{L_1} V_{out}$$

$$= C_1 (A_1 s_1 e^{s_1 t} + A_2 s_2 e^{s_2 t}) \underline{s(t)}$$

$$= C_1 \left(\frac{I_1}{C_1} \right) \underline{s(t)}$$

$$= I_1 \underline{s(t)} \quad \checkmark \quad \text{As desired.}$$

$$I_{cap}(t) = C_1 (A_1 s_1 e^{s_1 t} + A_2 s_2 e^{s_2 t}) u(t)$$

$$I_L(t) = \frac{1}{L_1} \int_0^t V_{out} dt$$

$$= \frac{1}{L_1} \left(\frac{A_1}{s_1} e^{s_1 t} + \frac{A_2}{s_2} e^{s_2 t} \right) u(t) - \frac{1}{L_1} \left(\frac{A_1}{s_1} + \frac{A_2}{s_2} \right)$$

$$\frac{A_1}{s_1} + \frac{A_2}{s_2} = A_1 \left(\frac{1}{s_1} - \frac{1}{s_2} \right)$$

$$= A_1 \left(\frac{s_2 - s_1}{s_1 s_2} \right)$$

$$= \left(\frac{-\frac{I_1}{C_1}}{\frac{1}{L_1 C_1}} \right)$$

$$= -I_1 L_1$$

$$s_1 s_2 = \frac{1}{L_1 C_1} \text{ by Vieta's}$$

$$A_1(s_1 - s_2) = \frac{I_1}{C_1}$$

$$\Rightarrow I_1(t) = \frac{1}{L} \left(\frac{A_1}{s_1} e^{s_1 t} + \frac{A_2}{s_2} e^{s_2 t} \right) u(t) + I_1^+$$

Case 2: Critically-Damped Response ($R_1 = \frac{1}{2} \sqrt{\frac{L}{C_1}}$)

$$V_{out} = [A_1 e^{s_1 t} + A_2 t e^{s_1 t}] u(t) \quad (s_1 = \frac{-1}{2R_1 C_1})$$


$$A_1 = V_{out}(0^+) = 0$$

$$A_1 s_1 + A_2 = \frac{dV_{out}}{dt}(0^+) = \frac{I_1}{C_1} \Rightarrow A_2 = \frac{I_1}{C_1}$$

Case 3: Underdamped Response ($R_1 > \frac{1}{2} \sqrt{\frac{L}{C_1}}$)

$$V_{out} = (A_1 e^{\alpha t} \cos \omega_1 t + A_2 e^{\alpha t} \sin \omega_1 t) u(t)$$
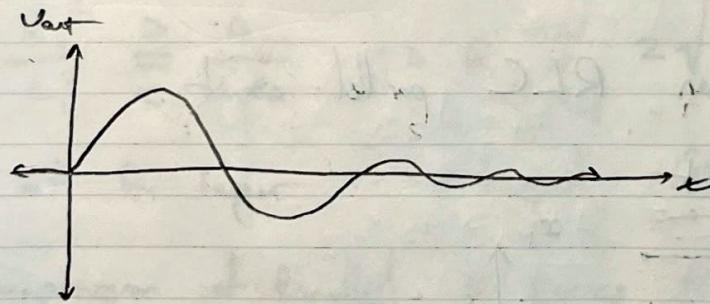
$$\alpha = -\frac{1}{2R_1 C_1} \quad \omega = \frac{1}{2} \sqrt{\frac{1}{4R_1 C_1} - \frac{1}{R_1^2 C_1^2}}$$




$$A_1 = V_{out}(0^+) = 0$$

$$A_1 \alpha + A_2 \omega_1 = \frac{dV_{out}}{dt}|_{t=0^+} = \frac{I_1}{C_1}$$

$$A_2 \omega_1 = \frac{I_1}{C_1}$$

Impulse Response

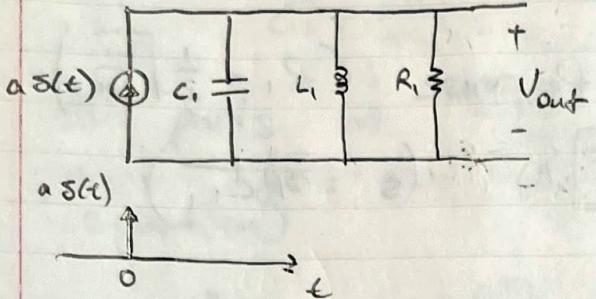

$$V_{out} = L_1 \frac{dI_L}{dt}$$


↳ derivative of impulse \Rightarrow
 (out still governed by C_1)
 \rightarrow All current through C_1

$$I_{cap} = C_1 \frac{dV_{out}}{dt}$$

$$V_{out} = \frac{1}{C_1} \int_{0^-}^{0^+} I_{cap} dt$$



$$= \frac{1}{C_1} \int_{0^-}^{0^+} a\delta(t) dt$$

$$= \frac{a}{C_1}$$

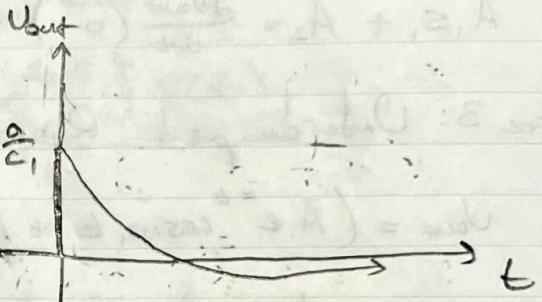

\Rightarrow Same as undriven RLC parallel circuit.


Series RLC circuit

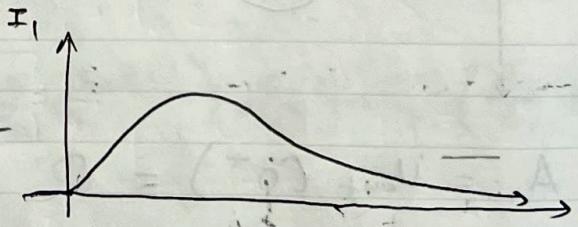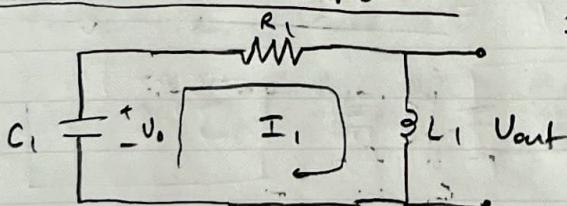

$$I_L(0^+) = 0$$

$$I_1(\infty) = 0$$

$$V_{out}(0^+) = V_0$$

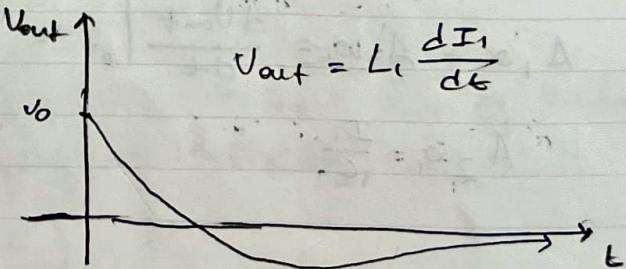

$$V_{out} = L_1 \frac{dI_1}{dt}$$

• Quantitative Analysis

$$V_0 - \frac{1}{C_1} \int I_1 dt - I_1 R_1 - L_1 \frac{dI_1}{dt} = 0$$

$$\left\{ \begin{array}{l} \frac{1}{C_1} I_1 + \frac{dI_1}{dt} R_1 + L_1 \frac{d^2 I_1}{dt^2} = 0 \\ I_1(0^+) = 0 \\ V_{cap}(0^+) = V_0 \end{array} \right.$$

$$L_1 s^2 + R_1 s + \frac{1}{C_1} = 0$$


$$s^2 + \frac{R_1}{L_1} s + \frac{1}{L_1 C_1} = 0$$

$$s_{1,2} = -\frac{R_1}{2L_1} \pm \frac{1}{2} \sqrt{\left(\frac{R_1}{L_1}\right)^2 - \frac{4}{L_1 C_1}}$$

$$\frac{R_1^2}{L_1^2} \geq \frac{4}{L_1 C_1} \Rightarrow R_1 \geq 2\sqrt{\frac{L_1}{C_1}}$$

If R_1 larger \Rightarrow over-damped (since, intuitively, in series)

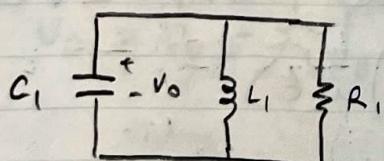
• Comparison of Parallel & series RLC Circuits



$R_1 = \infty \Rightarrow$ LC ideal oscillates

$R_1 < \frac{1}{2} \sqrt{\frac{L_1}{C_1}}$ dampens

the oscillation (underdamped)

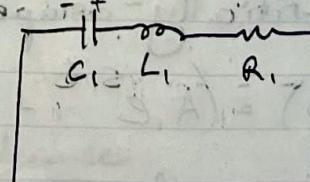

$R_1 = 0 \Rightarrow$ LC ideal oscillates

$R_1 > 2\sqrt{\frac{L_1}{C_1}}$ dampens

the oscillation (overdamped)

$$V_0 = V_{cap}(0^+) = V_L(0^+) = L_1 \frac{dI_1}{dt} \Big|_{t=0^+}$$

$$\Rightarrow -\frac{dI_1}{dt} \Big|_{t=0^+} = \frac{V_0}{L_1}$$

$$\left\{ \begin{array}{l} L_1 \frac{d^2 I_1}{dt^2} + R_1 \frac{dI_1}{dt} + \frac{1}{C_1} I_1 = 0 \\ I_1(0^+) = 0 \\ \frac{dI_1}{dt}(0^+) = \frac{V_0}{L_1} \end{array} \right.$$

Three Natural Responses:

Case 1: Overdamped response ($R_1 > 2\sqrt{\frac{L_1}{C_1}}$)

$$\Rightarrow I_1(t) = (A_1 e^{s_1 t} + A_2 e^{s_2 t}) u(t)$$

$$0 = I_1(0^+) = A_1 + A_2$$

$$\frac{V_0}{L_1} = \frac{dI_1}{dt}(0^+) = (A_1 s_1 + A_2 s_2) u(0)$$

$$= A_1 s_1 + A_2 s_2$$

Case 2: Critically-damped response ($R_1 = 2\sqrt{\frac{L_1}{C_1}}$)

$$\Rightarrow I_1(t) = (A_1 e^{s_1 t} + A_2 t e^{s_1 t}) u(t)$$

$$0 = I_1(0^+) = A_1$$

$$\frac{V_0}{L_1} = \frac{dI_1}{dt}(0^+) = A_1 s_1 + A_2$$

$$\Rightarrow A_2 = \frac{V_0}{L_1}$$

Case 3: Underdamped response ($R_1 < 2\sqrt{\frac{L_1}{C_1}}$)



$$\Rightarrow I_1 = (A_1 e^{\alpha t} \cos(\omega_1 t) + A_2 e^{\alpha t} \sin(\omega_1 t)) u(t)$$

$$s_{1,2} = \left(-\frac{R_1}{2L_1} \right) \pm j \sqrt{\frac{1}{2} \sqrt{\frac{4}{L_1 C_1} - \left(\frac{R_1}{L_1} \right)^2}} \quad \omega_1$$

$$0 = I_1(0^+) = A_1$$

$$\frac{V_0}{L_1} = \frac{dI_1}{dt}|_{t=0^+} = A_1 \alpha + A_2 \omega_1$$
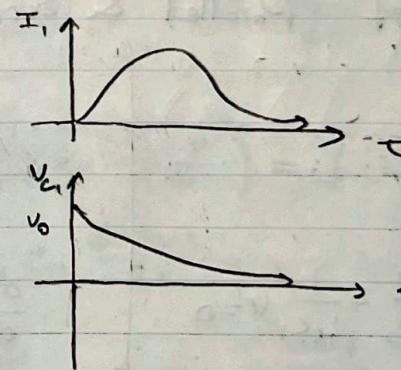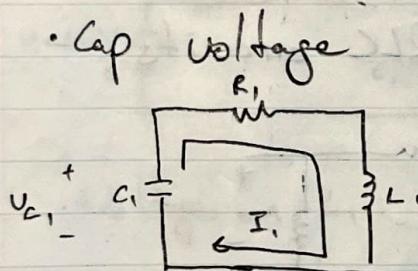
$$\Rightarrow A_2 \omega_1 = \frac{V_0}{L_1}$$




$$V_{C1} = V_0 - \frac{1}{C_1} \int_0^t I_1(\epsilon) d\epsilon$$

Starting voltage

voltage lost because
of lost charge
(between 0 and t)

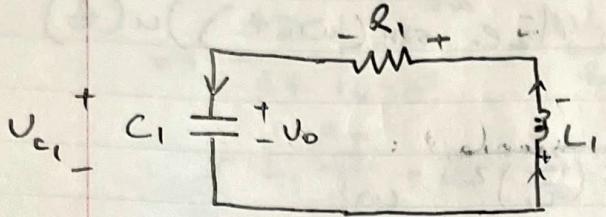Alternative Method: Find V_{C_1} directly ($\omega \neq I_1$)



$C_1 \frac{dV_{C_1}}{dt}$: current through C_1 ,
 $R_1 C_1 \frac{dV_{C_1}}{dt}$: voltage across R ,


$$L_1 \frac{dI}{dt} = L_1 \frac{d}{dt} \left(C_1 \frac{dV_{C_1}}{dt} \right) = L_1 C_1 \frac{d^2 V_{C_1}}{dt^2} : \text{voltage across } L,$$

$$\left. L_1 C_1 \frac{d^2 V_{C_1}}{dt^2} + R_1 C_1 \frac{dV_{C_1}}{dt} + V_{C_1} \right| = 0 \quad (\text{KVL})$$

$$V_{C_1}(0^+) = V_0$$

$$I_{L_1}(0^+) = 0 \Rightarrow I_{C_1}(0^+) = 0 \Rightarrow \left. C_1 \frac{dV_{C_1}}{dt} \right|_{t=0^+} = 0$$

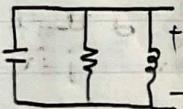Summary of Parallel & Series RLC circuits.




$$\frac{d^2 V}{dt^2} + \frac{1}{R_1 C_1} \frac{dV}{dt} + \frac{1}{L_1 C_1} V = 0$$

$$s_{1,2} = -\frac{1}{2R_1 C_1} \pm \frac{1}{2} \sqrt{\frac{1}{R_1^2 C_1^2} - \frac{4}{L_1 C_1}}$$

$R_1 < \frac{1}{2} \sqrt{\frac{L_1}{C_1}}$: Over-damped

$R_1 = \frac{1}{2} \sqrt{\frac{L_1}{C_1}}$: Critically-damped

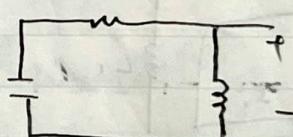$R_1 > \frac{1}{2} \sqrt{\frac{L_1}{C_1}}$: Under-damped



$$\frac{d^2 V}{dt^2} + \frac{R_1}{L_1} \frac{dV}{dt} + \frac{1}{L_1 C_1} V = 0$$

$$s_{1,2} = -\frac{R_1}{2L_1} \pm \frac{1}{2} \sqrt{\frac{R_1^2}{L_1^2} - \frac{4}{L_1 C_1}}$$

$R_1 > 2\sqrt{\frac{L_1}{C_1}}$: Over-damped

$R_1 = 2\sqrt{\frac{L_1}{C_1}}$: Critically-damped

$R_1 < 2\sqrt{\frac{L_1}{C_1}}$: Under-damped

A Note on Dif. Eqs.:


- First-Order Eqs. $\frac{dy}{dt} + \alpha y = \beta$

$$y(\infty) = \frac{\beta}{\alpha} \text{ (if } y \text{ becomes constant)}$$

- Second-Order Eqs. $\frac{d^2y}{dt^2} + \alpha \frac{dy}{dt} + \beta y = \gamma$

$$y(\infty) = \frac{\gamma}{\beta} \text{ (if } y \text{ becomes constant)}$$

Step Response

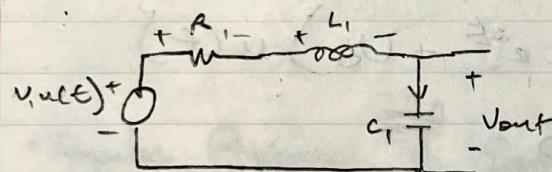

Current through cap:

$$C_1 \frac{dV_{out}}{dt}$$


$$\text{Voltage on } L_1: L_1 \frac{d}{dt} \left(C_1 \frac{dV_{out}}{dt} \right) = L_1 C_1 \frac{d^2 V_{out}}{dt^2}$$

$$\text{Voltage on } R_1 = R_1 C_1 \frac{dV_{out}}{dt}$$

$$- V_{u(t)} - R_1 C_1 \frac{dV_{out}}{dt} - L_1 C_1 \frac{d^2 V_{out}}{dt^2} - V_{out} = 0$$

$$\left\{ L_1 C_1 \frac{d^2 V_{out}}{dt^2} + R_1 C_1 \frac{dV_{out}}{dt} + V_{out} = V_{u(t)} \right.$$

$$\left. \begin{aligned} V_{out}(0^+) &= 0 \\ I_{L_1}(0^+) &= 0 \Rightarrow C \frac{dV_{out}}{dt} \Big|_{0^+} = 0 \Rightarrow \frac{dV_{out}}{dt} \Big|_{0^+} = 0 \end{aligned} \right.$$

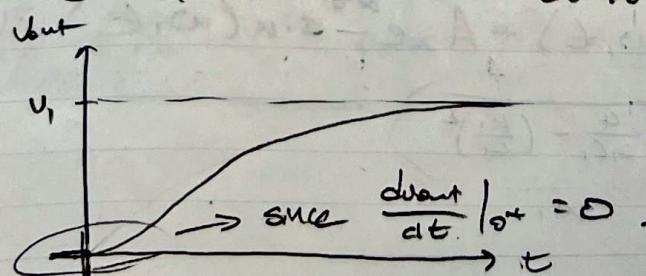

$$\text{Characteristic Eq: } s^2 + \frac{R_1}{L_1} s + \frac{1}{L_1 C_1} = 0$$

Case 1: Overdamped $R_1 > 2\sqrt{\frac{L_1}{C_1}}$

$$V_{out} = (A_1 e^{s_1 t} + A_2 e^{s_2 t} + V_0) u(t)$$

$$A_1 + A_2 + V_0 = V_{out}(0^+) = 0$$

$$(A_1 s_1 + A_2 s_2) u(t) + V_{out}(0^+) \delta(t) = \frac{dV_{out}}{dt}|_{0^+} = 0$$

$$A_1 s_1 + A_2 s_2 = 0$$


Case 2: Critically-damped $R_1 = 2\sqrt{\frac{L_1}{C_1}}$

$$V_{out}(t) = (A_1 e^{s_1 t} + A_2 t e^{s_1 t} + V_0) u(t)$$

$$A_1 + V_0 = V_{out}(0^+) = 0$$

$$(A_1 s_1 + A_2) u(t) + V_{out}(0^+) \delta(t) = \frac{dV_{out}}{dt}|_{0^+} = 0$$

$$A_1 s_1 + A_2 = 0$$

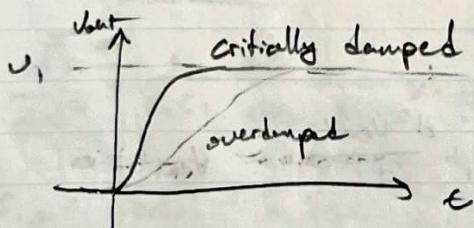

Case 3: Underdamped $R_1 < 2\sqrt{\frac{L_1}{C_1}}$


$$V_{out}(t) = (A_1 e^{\alpha t} \cos(\omega_1 t) + A_2 e^{\alpha t} \sin(\omega_1 t) + V_0) u(t)$$

$$s_{1,2} = -\frac{R_1}{2L_1} \pm j \frac{1}{2} \sqrt{\frac{4}{L_1 C_1} - (\frac{R_1}{C_1})^2}$$



$$\alpha \quad \omega_1$$

$$A_1 + V_0 = V_{out}(0^+) = 0$$

$$A_1 \alpha + A_2 \omega = \frac{dV_{out}}{dt}|_{t=0^+} = 0$$

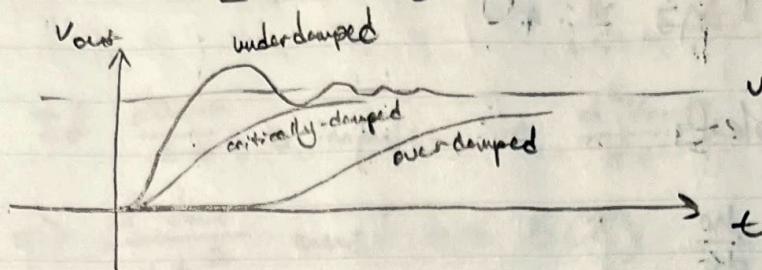

• Robotics Analogy

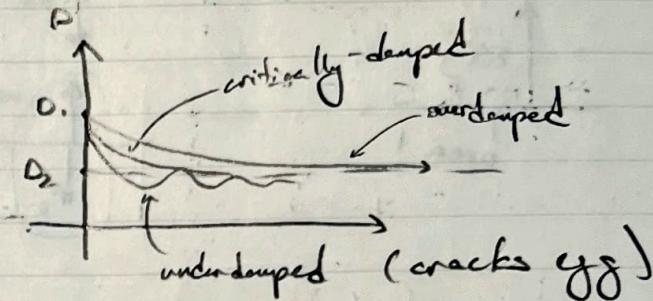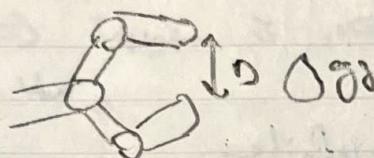


• Impulse Response of Series RLC circuit

Approach 1: $\int \rightarrow \boxed{\quad} \rightarrow g(t)$

$\uparrow \rightarrow \boxed{\quad} \rightarrow \frac{dy}{dt}$

RLC is Linear Time Invariant system.



Approach 2:

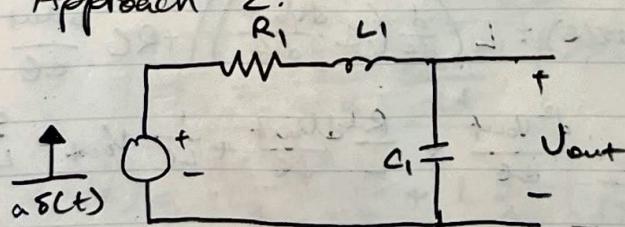



Voltage on L_1 can't jump because requires ∞ current
 \hookrightarrow can only jump current here because on L_1 ($I_{L_1} \neq \infty \Rightarrow$ best can't jump)

Since $\delta(t)$ jumps to ∞ and resistor/cap do not
 \Rightarrow All of impulse through inductor



- Impulses & Doublets

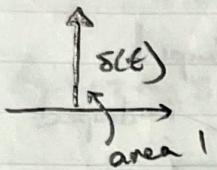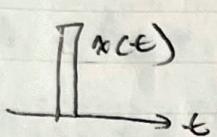


$$\frac{d\delta}{dt}$$

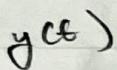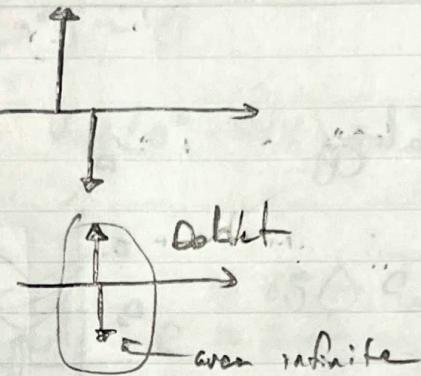

$$\frac{dy}{dt}$$

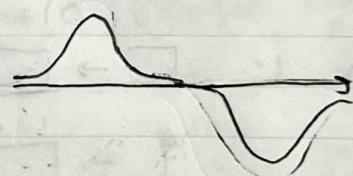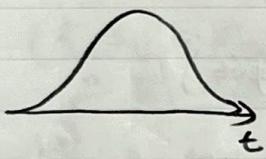

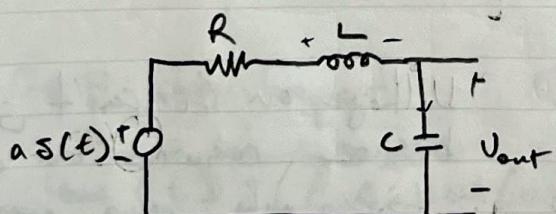- Impulse Response of Series RLC circuit ctd.



$$a\delta(t) = L \left(\frac{d}{dt} \left(C \frac{dV_{out}}{dt} \right) \right) + RC \frac{dV_{out}}{dt} + V_{out}$$

$$\frac{d^2 V_{out}}{dt^2} + \frac{R}{L} \frac{dV_{out}}{dt} + \frac{1}{LC} V_{out} = \frac{a}{LC} \delta(t)$$

If V_{out} is impulse $\rightarrow \frac{dV_{out}}{dt}$ is doublet


$\rightarrow \frac{1}{LC} \delta(t)$ cannot match doublet

If $\frac{dV_{out}}{dt}$ is impulse $\rightarrow \frac{d^2V_{out}}{dt^2}$ is doublet


$\Rightarrow \frac{d^2V_{out}}{dt^2}$ must have $\delta(t)$

$\Rightarrow \frac{dV_{out}}{dt}$ has a step

$\Rightarrow V_{out}$ is continuous

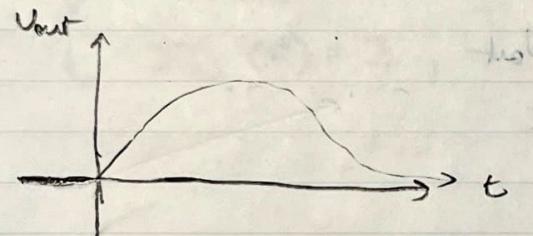

Example

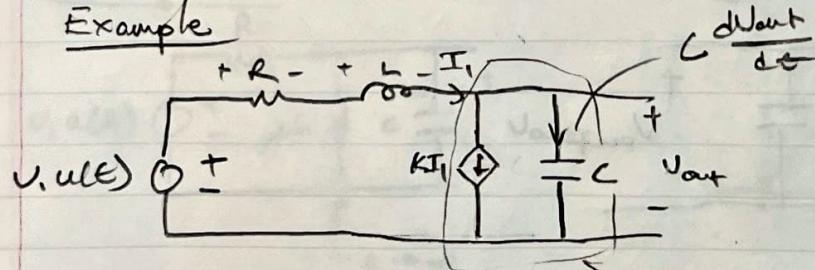

$$I_1 = KI_1 + C \frac{dV_{out}}{dt}$$

$$C_{eq} = \frac{C}{1-K}$$

$$I_1 = \frac{C}{1-K} \frac{dV_{out}}{dt}$$

$$V_{in}(t) = \frac{RC}{1-K} \frac{dV_{out}}{dt} + L \frac{d}{dt} \left(\frac{C}{1-K} \frac{dV_{out}}{dt} \right) + V_{out}$$


$$\frac{LC}{1-K} \frac{d^2V_{out}}{dt^2} + \frac{RC}{1-K} \frac{dV_{out}}{dt} + V_{out} = V_{in}(t)$$

$$\frac{d^2 V_{out}}{dt^2} + \frac{R}{L} \frac{dV_{out}}{dt} + \frac{1}{L \frac{C}{1-k}} V_{out} = \frac{V_1}{L \frac{C}{1-k}} u(t)$$

\Rightarrow Only C changed to $\frac{C}{1-k}$


What if $k=1$?

\Rightarrow cap is shorted

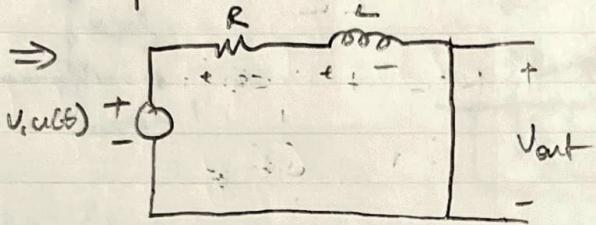


$$V_{out} = 0.$$

Example

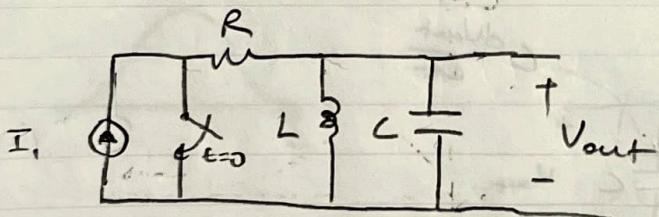

$$t < 0$$

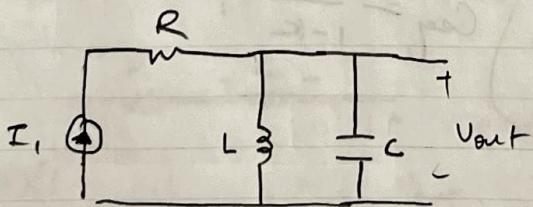

Since all quantities are constant

$$\Rightarrow I_{cap} = 0$$


$$\Rightarrow I_L = I_s$$

Since I_L is constant $\Rightarrow V_L = 0 \Rightarrow V_{out} = 0$

$t > 0$

$$V_{\text{out}}(0) = 0$$

I₁: initial condition

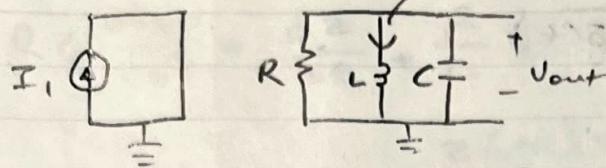

⇒ Parallel RLC circuit

$$\left\{ \begin{array}{l} \frac{d^2 V_{\text{out}}}{dt^2} + \frac{1}{RC} \frac{d V_{\text{out}}}{dt} + \frac{1}{LC} V_{\text{out}} = 0 \\ V_{\text{out}}(0) = 0 \end{array} \right.$$



$$I_{\text{in}}(0) = I_1$$

KCL at $t = 0^+$:

$$I_1 + C \frac{d V_{\text{out}}}{dt} \Big|_{0^+} = 0$$

$$\Rightarrow \frac{d V_{\text{out}}}{dt} \Big|_{0^+} = - \frac{I_1}{C}$$

Example

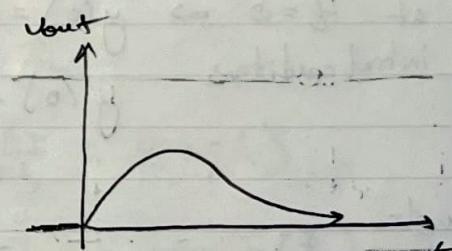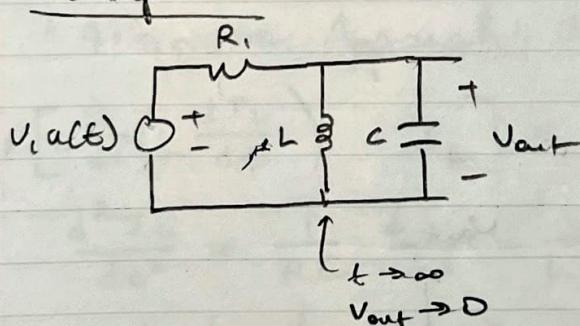

• Diff. Eqs. with Impulses

$$\alpha \frac{d^2z}{dt^2} + \beta \frac{dz}{dt} + \gamma z = \delta(t)$$

Procedure:

① Replace $\delta(t)$ with $u(t)$

② Create a new diff. eq.

$$\alpha \frac{d^2z}{dt^2} + \beta \frac{dz}{dt} + \gamma z = u(t) \Rightarrow z(\infty) = \frac{1}{\gamma}$$

e.g., overdamped: $z(t) = A_1 e^{s_1 t} + A_2 e^{s_2 t} + \frac{1}{\gamma}$

③ $\frac{dz}{dt} = y(t)$ add this so $z(\infty) = \frac{1}{\gamma}$



e.g., overdamped: $y(t) = A_1 s_1 e^{s_1 t} + A_2 s_2 e^{s_2 t}$

at $t=0 \rightarrow y(0) = k_1$

initial conditions

$$y'(0) = k_2$$

Example

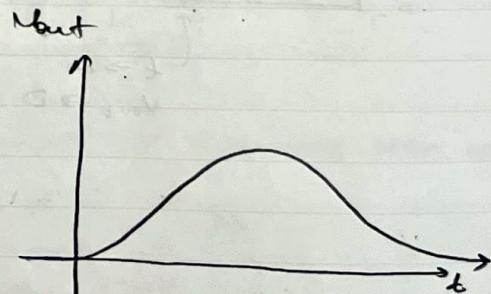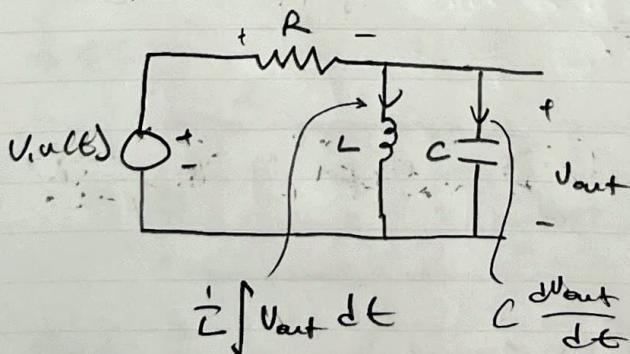

$$R \left(\frac{1}{L} \int V_{out} dt + C \frac{dV_{out}}{dt} \right) + V_{out} = V_{in} u(t)$$

$$RC \frac{d^2 V_{out}}{dt^2} + \frac{dV_{out}}{dt} + \frac{R}{L} V_{out} = V_1 \delta(t)$$


$$RC \frac{d^2 z}{dt^2} + \frac{dz}{dt} + \frac{R}{L} z = V_1 u(t)$$

$$z(\infty) = V_1 \cdot \frac{L}{R}$$

e.g. overdamped $z(t) = (A_1 e^{s_1 t} + A_2 e^{s_2 t} + V_1 \frac{L}{R}) u(t)$.

$$\frac{dz}{dt} = V_{out}(t) = (A_1 s_1 e^{s_1 t} + A_2 s_2 e^{s_2 t}) u(t)$$

Find initial conditions: $V_{out}(0^+) = 0$
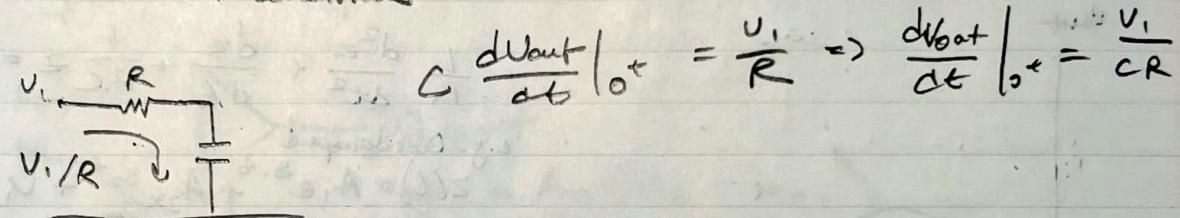
$$C \frac{dV_{out}}{dt}|_{0^+} = \frac{V_1}{R} \Rightarrow \frac{dV_{out}}{dt}|_{0^+} = \frac{V_1}{CR}$$


Alternative Approach: Using I_L .

$$R \left[C \frac{d}{dt} \left(L \frac{dI_L}{dt} \right) + I_L \right] + L \frac{dI_L}{dt} = V_1 u(t)$$

$$\frac{d^2 I_L}{dt^2} + \frac{1}{RC} \frac{dI_L}{dt} + \frac{1}{LC} I_L = \frac{V_1}{RCL} u(t)$$

Avoids the $\delta(t)$ ---

e.g. overdamped $I_L(t) = (A_1 e^{s_1 t} + A_2 e^{s_2 t} + \frac{V_1}{R}) u(t)$


$$I_L(0^+) = 0$$

$$L \frac{dI_L}{dt}|_{0^+} = V_{out}(0^+) = 0$$

$$\Rightarrow \frac{dI_L}{dt}|_{0^+} = 0$$


$$\frac{1}{C} \int \frac{V_{out}}{R} dt$$

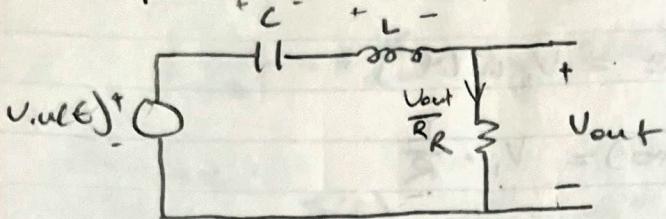Example $L \frac{d}{dt} \left(\frac{V_{out}}{R} \right)$



$$\frac{1}{C} \int \frac{V_{out}}{R} dt + \frac{L}{R} \frac{d V_{out}}{dt} + V_{out} = U_i(t)$$
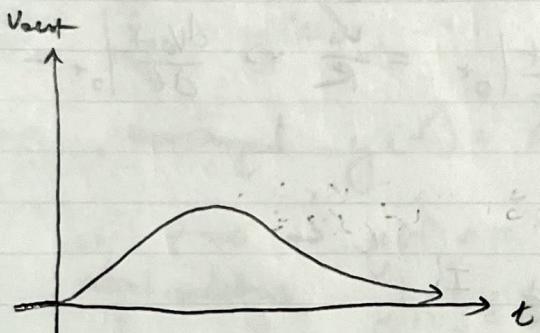
$$\frac{L}{R} \frac{d^2 V_{out}}{dt^2} + \frac{d V_{out}}{dt} + \frac{1}{RC} V_{out} = U_i(t)$$



$$\frac{L}{R} \frac{d^2 z}{dt^2} + \frac{dz}{dt} + \frac{1}{RC} z = U_i(t)$$

e.g. Overdamped

$$z(t) = A_1 e^{s_1 t} + A_2 e^{s_2 t} + U_i / RC$$


$$V_{out}(t) = A_1 s_1 e^{s_1 t} + A_2 s_2 e^{s_2 t}$$

Initial conditions: $V_{out}(0^+) = 0$

$$L \frac{d}{dt} \left(\frac{V_{out}}{R} \right) \Big|_{0^+} = U_i \quad (\text{Voltage on cap \& resistor} = 0)$$


$$\Rightarrow \frac{d}{dt} (V_{out}) \Big|_{0^+} = U_i \cdot \frac{R}{L}$$

• Basic Amplifier Concepts

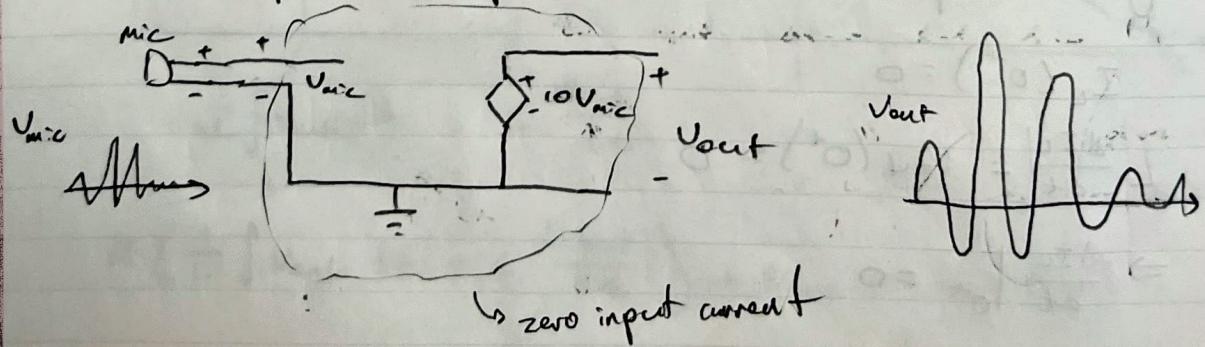


Notes: ① Voltage gain (A_o)

Output / Input

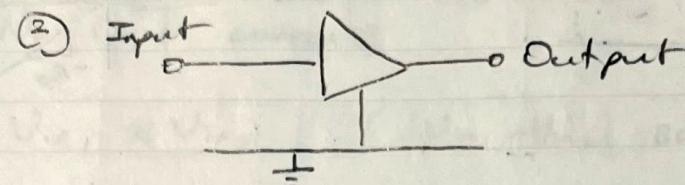


③ Amplifier has a zero input current

• Operational Amplifier

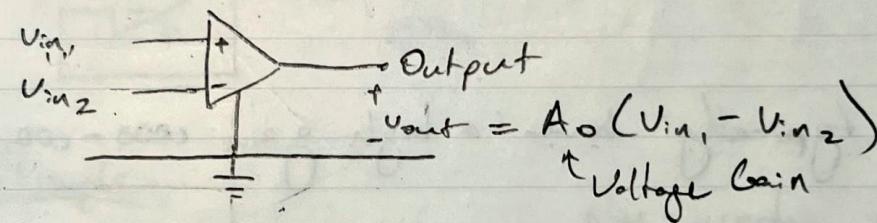




Model:

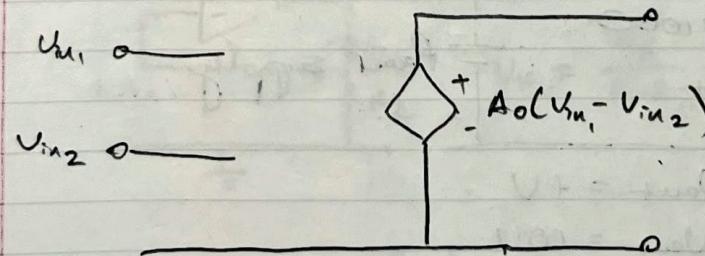

• Op Amp has zero input currents.

Study

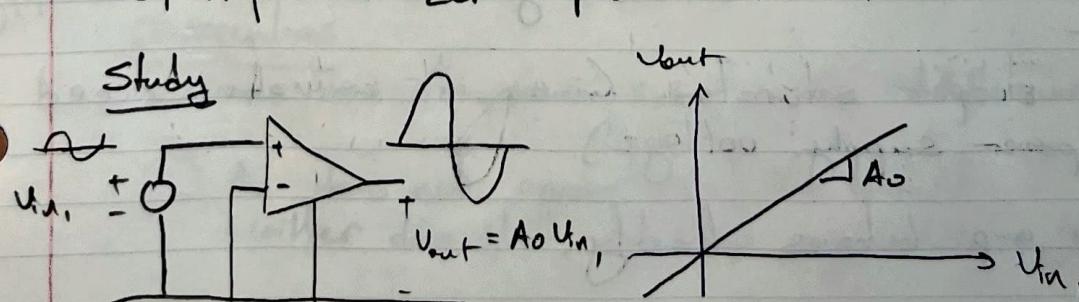


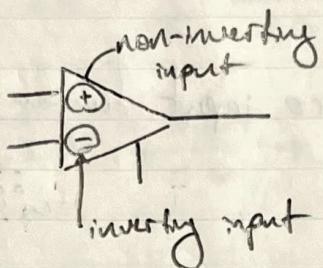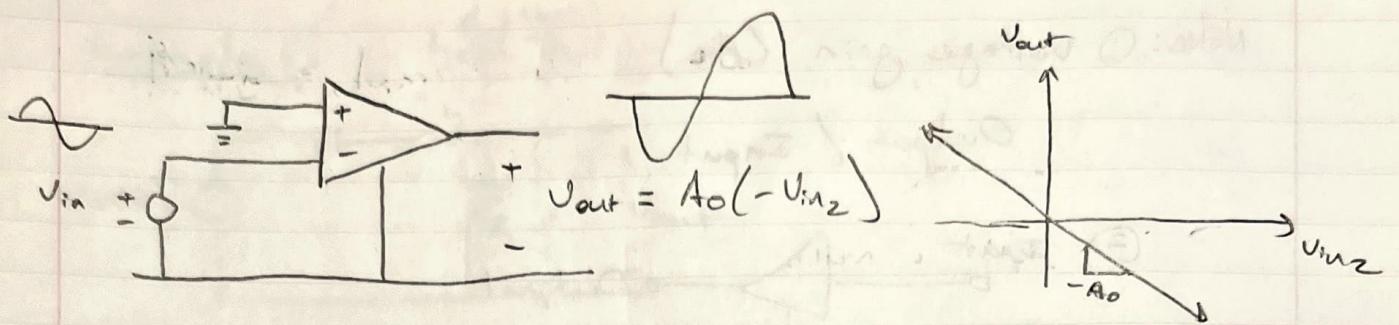

• Observation

Op amps typically have a high gain: 1000 - 100,000.

Example

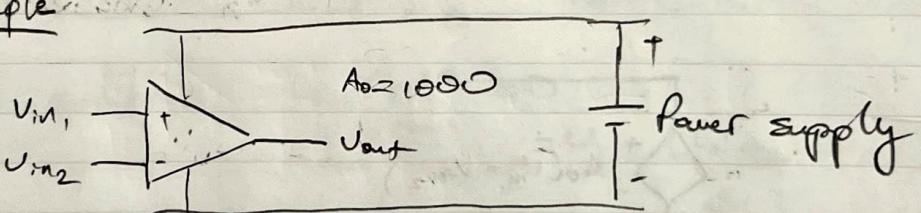

$$V_{in1} - V_{in2} = 1mV \Rightarrow V_{out} = 1V$$

$$V_{in1} - V_{in2} = 10mV \Rightarrow V_{out} = 10V$$

$$V_{in1} - V_{in2} = 100mV \Rightarrow V_{out} = 100V !!$$

↳ cannot generate because Power supply < 100V

Op-amp output saturated (i.e. it cannot exceed its power supply voltage)

⇒ Op-amp behaves badly.

In a well-designed circuit $|V_{in1} - V_{in2}|$ is small


Ideal Op Amp

① No input currents

② $V_{in1} \approx V_{in2}$ ($|V_{in1} - V_{in2}|$ small)


\Rightarrow simpler analysis

Example

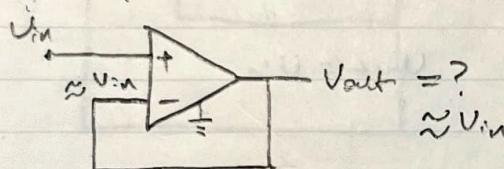

Unity Gain Buffer

Example

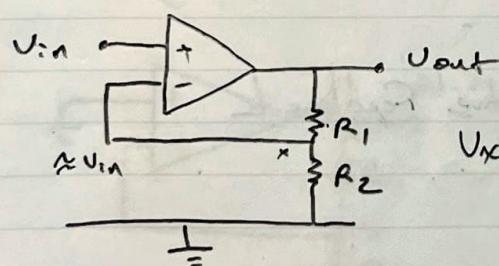

Non-inverting Amplifier

$$V_{in} \approx V_{in} \quad V_{out} = \frac{R_1}{R_1 + R_2} V_{in} \quad V_{out} \approx V_{in}$$


$$V_{out} = \left(1 + \frac{R_1}{R_2}\right) V_{in} \quad \text{Gain} = 1 + \frac{R_1}{R_2}$$

Observations

① V_{out} has the same sign as $V_{in} \Rightarrow$ Non-inverting


② A_o does not appear in the result
Neither does the op amp equivalent

③ what happens if $R_1 \rightarrow 0$?

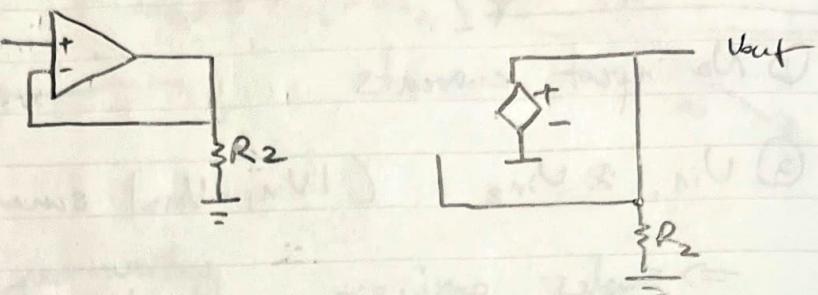


$$V_{out} = V_{in}$$

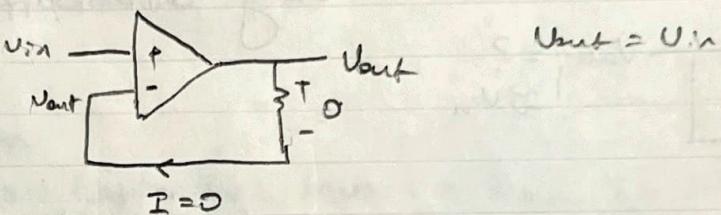
④ what happens if $R_2 \rightarrow \infty$




⑤ Feedback

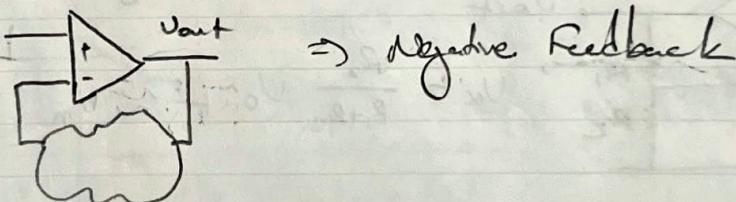


Twists on the Non-inverting amplifier

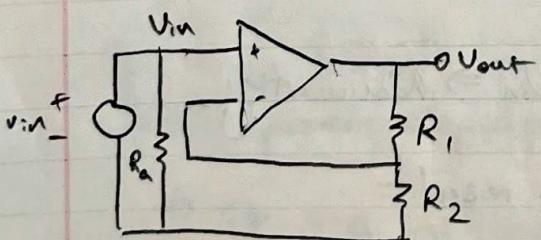

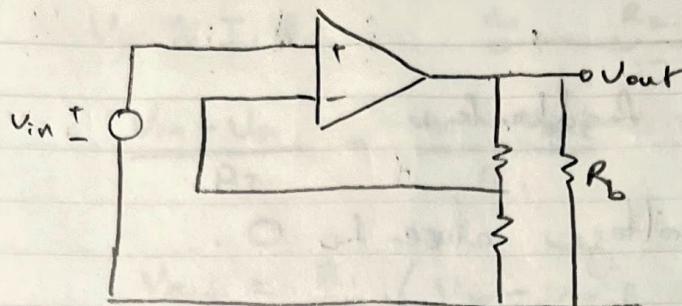R_a makes no difference
(Voltage at non-inv. input
still V_{in})





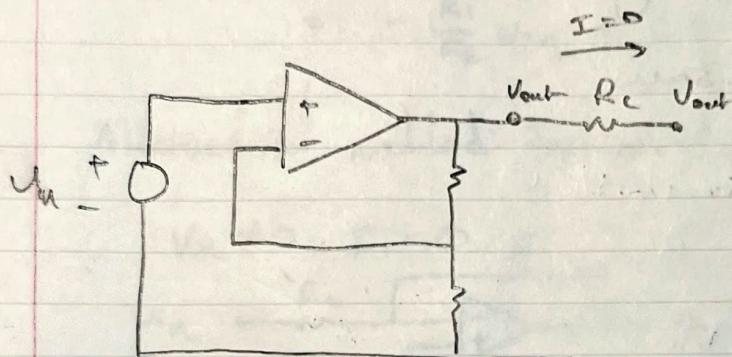R_b makes no difference
because V_{out} is always
fixed by dependent
voltage source (in node 1)




R_c makes no difference
($V_{out}' = V_{out}$) because
 $I = 0$.

Inverting Amplifier

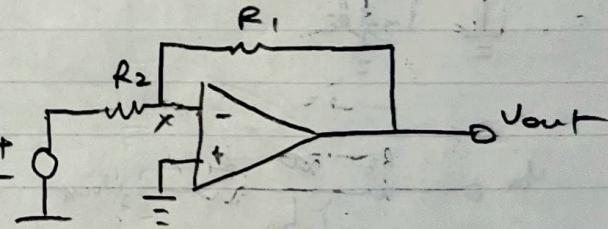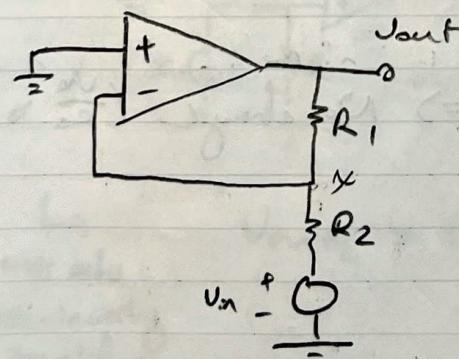


$$U_x \approx 0.$$

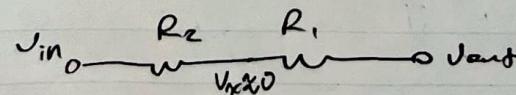


$$\frac{V_{in} - 0}{R_2} = \frac{0 - V_{out}}{R_1} \Rightarrow V_{out} = \frac{-R_1}{R_2} V_{in}$$

Observations

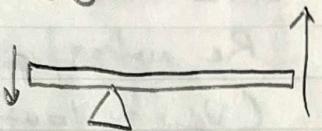- ① Circuit has negative feedback.
- ② Node X has a voltage close to 0.
↳ called a "virtual" ground
- ③ Analogy with seesaw




• Twists

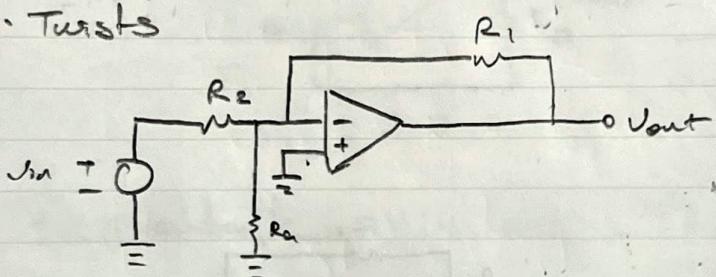


$$V_{in} \xrightarrow{R_2 \propto 0} I_{in} \xrightarrow{R_a} V_{out} \Rightarrow \text{No change } (\frac{V_o}{R_a} \text{ is small})$$

• Other Examples

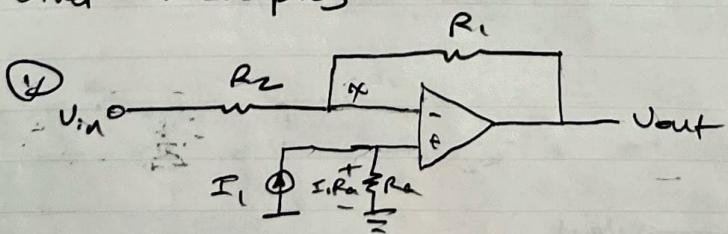

$$V_x \approx I_a R_a$$

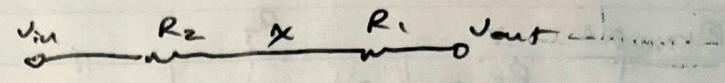


$$\frac{V_{in} - V_x}{R_2} = \frac{V_x - V_{out}}{R_1}$$

$$\begin{aligned} V_{out} &= \frac{R_1}{R_2} (V_x - V_{in}) + V_x \\ &= -\frac{R_1}{R_2} V_{in} + \left(1 + \frac{R_1}{R_2}\right) (I_a R_a) \end{aligned}$$


Alternative method: Superposition ..

$$V_{in} \neq 0, I_a = 0, R_a$$

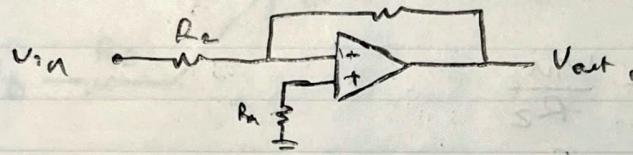

$$V_{out,1} = -\frac{R_1}{R_2} V_{in}$$

$$V_{in} = 0, I_a \neq 0, R_a$$


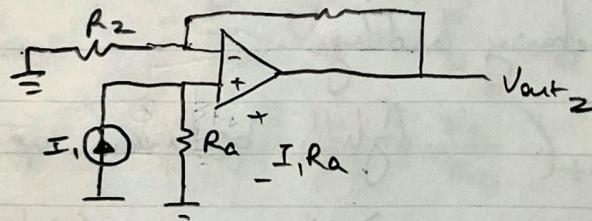


$$\xrightarrow{\text{maps onto}} V_{out,2} = \left(1 + \frac{R_1}{R_2}\right) (I_a R_a)$$

non-inverting
amplifier

$$V_{out} = V_{out,1} + V_{out,2} = -\frac{R_1}{R_2} V_{in} + \left(1 + \frac{R_1}{R_2}\right) (I_a R_a)$$

Example

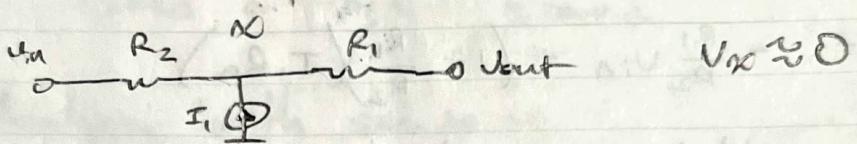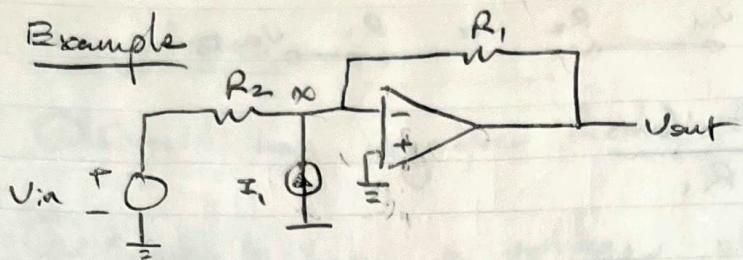


$$\frac{V_{in} - 0}{R_2} + I_1 = \frac{0 - V_{out}}{R_1}$$

$$\frac{V_{out}}{R_1} = -I_1 - \frac{V_{in}}{R_2}$$

$$V_{out} = -I_1 R_1 - \frac{R_1}{R_2} V_{in}$$


Example Op amps behaving badly

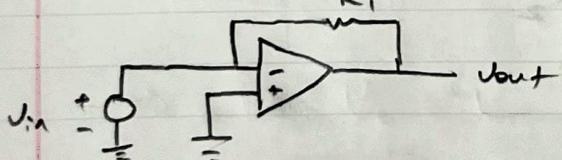


fight between op amp & V_{in} .

$\Rightarrow V_{in}$ wins (ideal)


$\Rightarrow V_{out}$ huge
→ saturated

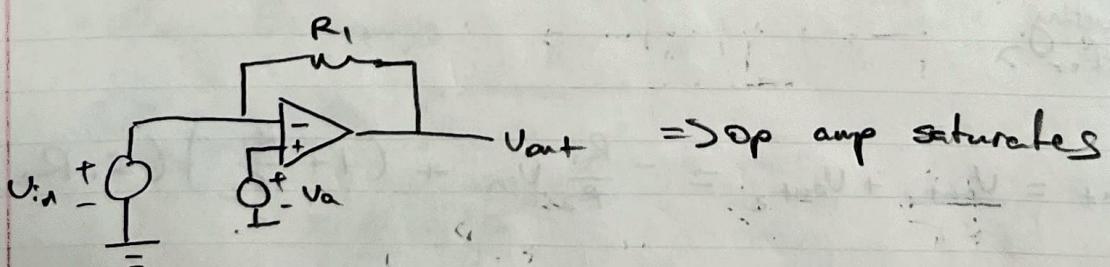

Adder (Summer)

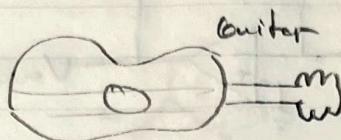


Π mic.
 V_G

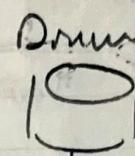

Π mic.
 V_D


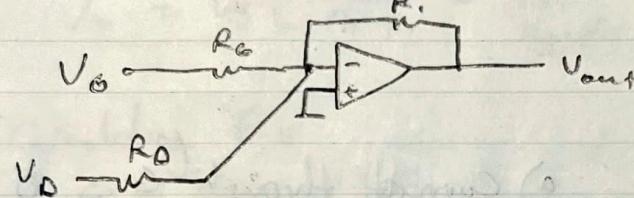
How do we "mix" V_G and V_D ? ($V_G + V_D$)




Easy to see w/ superposition:

$$\begin{aligned} V_{\text{out}} &= -\frac{R_1}{R_0} V_G - \frac{R_1}{R_0} V_D \\ &= -R_1 \left(\frac{V_G}{R_0} + \frac{V_D}{R_0} \right) \end{aligned}$$

Cascaded Stages

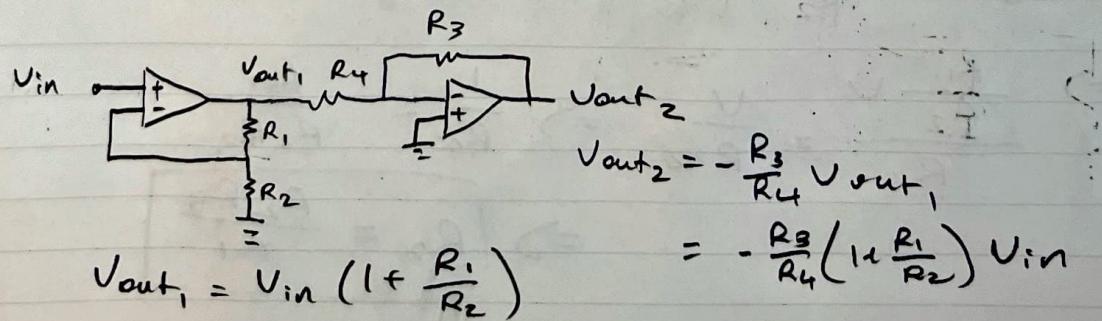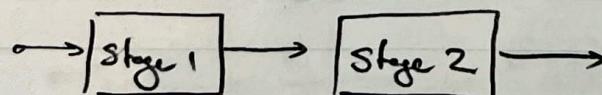

Another Example:

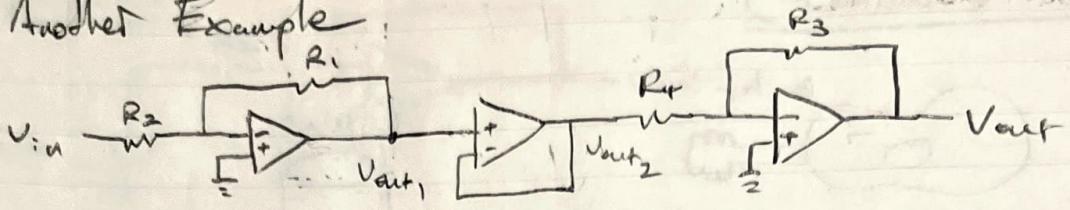


$$V_{out_1} = -\frac{R_1}{R_2} V_{in}$$

$$V_{out_2} = V_{out_1}$$

$$V_{out} = -\frac{R_3}{R_4} V_{out_2} = -\frac{R_3}{R_4} \left(-\frac{R_1}{R_2} V_{in} \right)$$

Practice Problems

1)

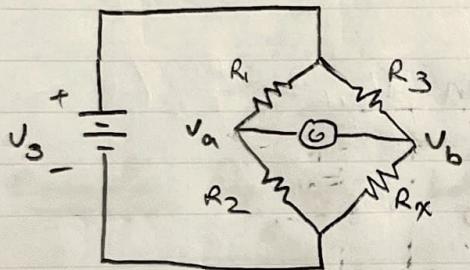

a) Current through G is 0.
 $R_x = ?$

\Rightarrow No voltage difference
 between V_a & V_b .

$$\Rightarrow V_a = V_b = V$$


$$\Rightarrow \frac{V_s - V}{R_1} = \frac{V}{R_2} \quad \text{and} \quad \frac{V_s - V}{R_3} = \frac{V}{R_x}$$

$$V_s - V = \frac{R_1}{R_2} V$$

$$\Rightarrow \frac{\frac{R_1}{R_2} V}{R_3} = \frac{V}{R_x} \Rightarrow \frac{1}{R_x} = \frac{R_1}{R_2 R_3}$$

$$\Rightarrow R_x = \frac{R_2 R_3}{R_1}$$

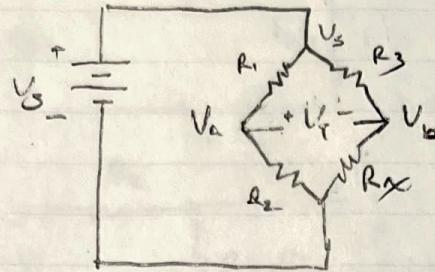b) Find the Thevenin equivalent seen by G.






$$V_a - V_b = V_T$$

$$V_a = \frac{V_s}{R_1 + R_2} \cdot R_2$$


$$V_b = \frac{V_s}{R_3 + R_x} \cdot R_x$$

$$V_T = V_s \left(\frac{R_2}{R_1 + R_2} - \frac{R_x}{R_3 + R_x} \right)$$





Calculating R_T :

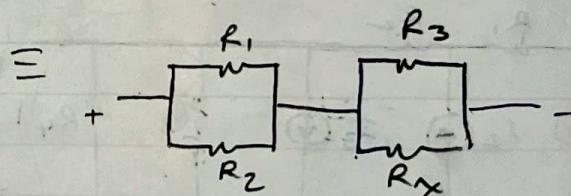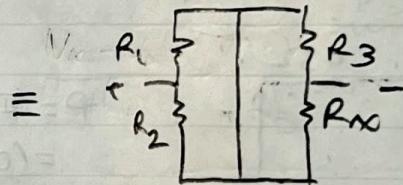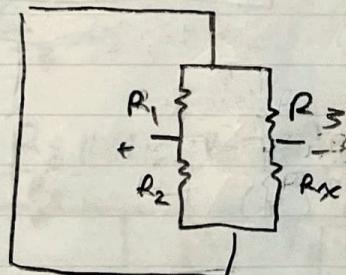


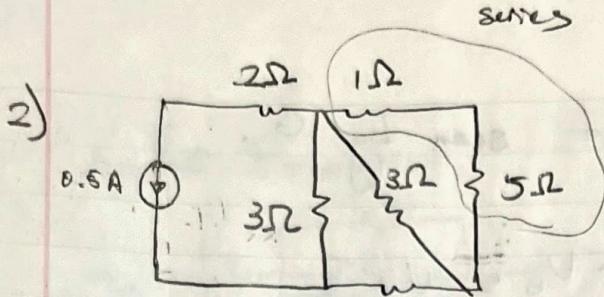
$$\Rightarrow R_T = \frac{R_1 R_2}{R_1 + R_2} + \frac{R_3 R_x}{R_3 + R_x}$$




Power delivered by current source = ?

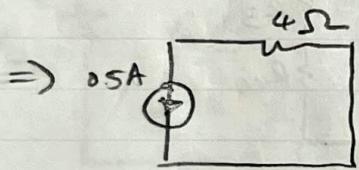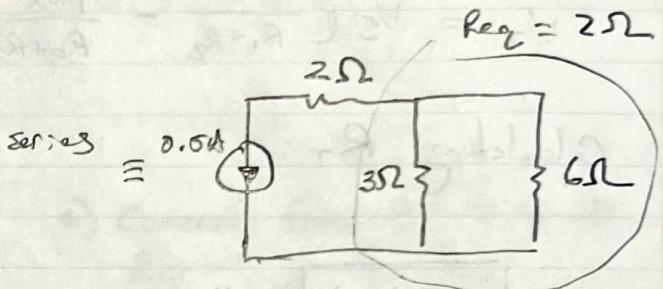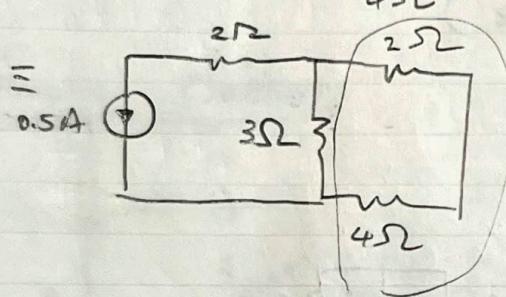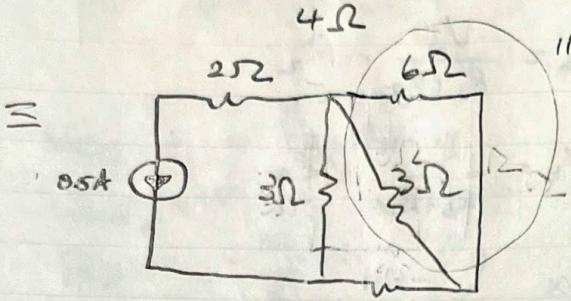

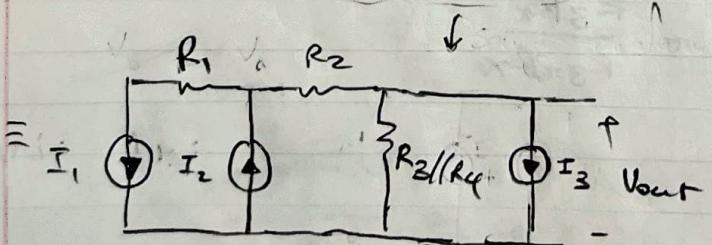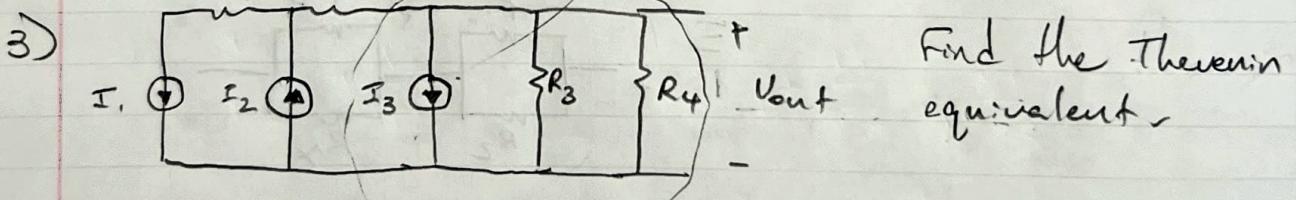
$$\begin{aligned} P &= I^2 R \\ &= (0.5)^2 (4) \\ &= 1W \end{aligned}$$




Superposition:

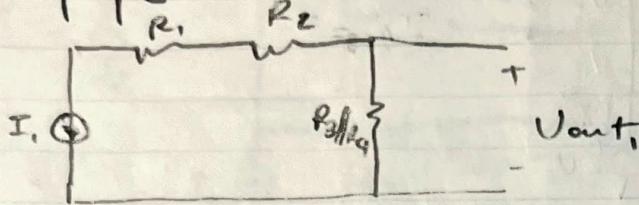
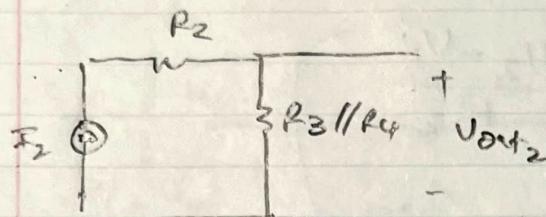
$$V_{\text{out}1} = -I_1 (R_3 \parallel R_4)$$





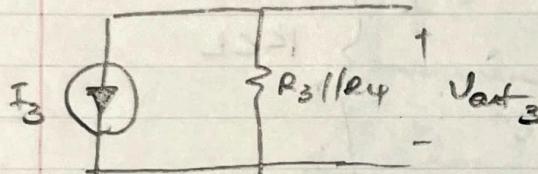
$$V_{\text{out}2} = I_2 (R_3 \parallel R_4)$$



$$V_{\text{out}3} = -I_3 (R_3 \parallel R_4)$$

$$V_T = (I_2 - I_1 - I_3) \left(\frac{R_3 R_4}{R_3 + R_4} \right)$$
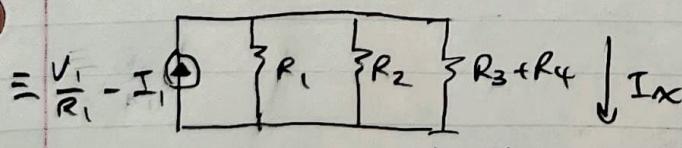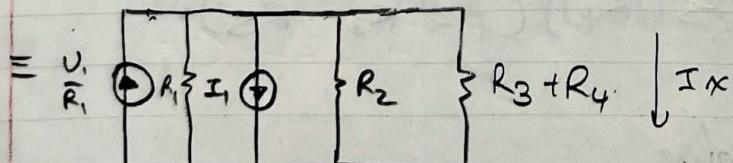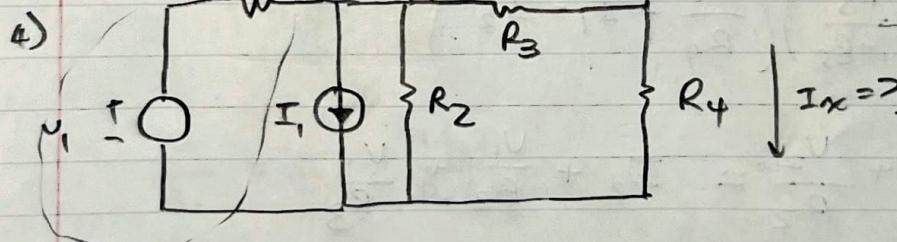
$$R_T = R_3 \parallel R_4 = \frac{R_3 R_4}{R_3 + R_4}$$




↳ current divider

$$I_x = \left(\frac{V_1}{R_1} - I_1 \right) \left(\frac{R_1 \parallel R_2}{R_1 \parallel R_2 + R_3 + R_4} \right)$$

$$= \left(\frac{V_1}{R_1} - I_1 \right) \left(\frac{R_1 R_2}{R_1 R_2 + (R_3 + R_4)(R_1 + R_2)} \right)$$

5)

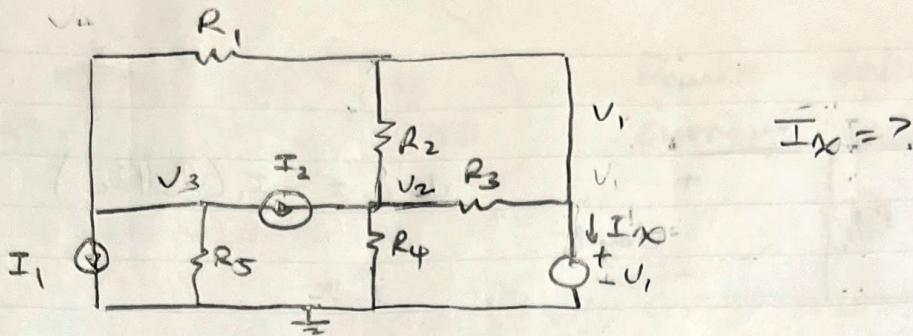

$$\textcircled{1} \quad I_x = \frac{V_2 - V_1}{R_3} + \frac{V_3 - V_1}{R_1} + \frac{V_2 - V_1}{R_2}$$

$$\textcircled{2} \quad I_2 + \frac{V_1 - V_2}{R_2} + \frac{V_1 - V_2}{R_3} = \frac{V_2}{R_4}$$

$$\textcircled{3} \quad \frac{V_3}{R_5} + I_1 + I_2 = \frac{V_1 - V_3}{R_1}$$

KCL




$$\textcircled{3} \quad \frac{V_3}{R_5} + \frac{V_3}{R_1} = \frac{V_1}{R_1} - I_1 - I_2$$

$$V_3 = \left(\frac{R_1 R_5}{R_1 + R_5} \right) \left(\frac{V_1}{R_1} - I_1 - I_2 \right)$$

$$\textcircled{2} \quad \frac{V_2}{R_4} + \frac{V_2}{R_3} + \frac{V_2}{R_2} = I_2 + \frac{V_1}{R_2} + \frac{V_1}{R_3}$$

$$V_2 = (R_2 || R_3 || R_4) \left(I_2 + \frac{V_1}{R_2} + \frac{V_1}{R_3} \right)$$

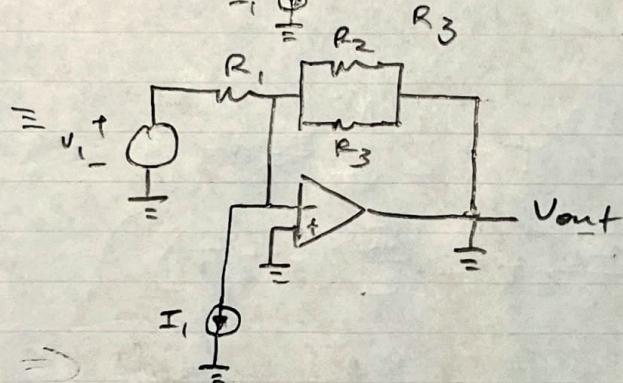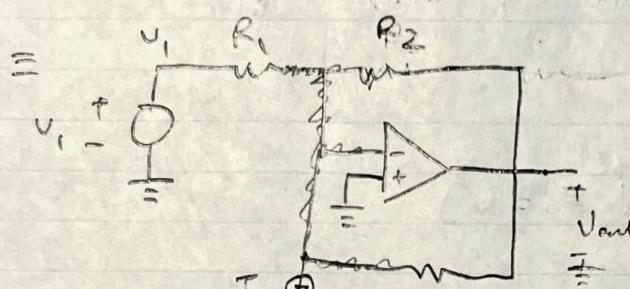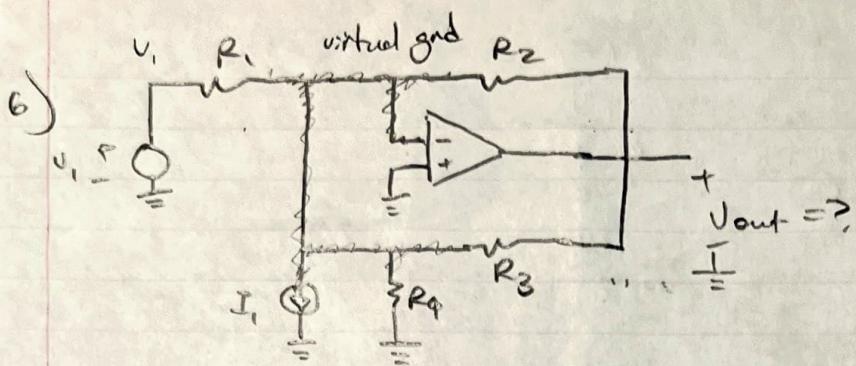\textcircled{1} \quad I_x = ? \quad \text{plug \& solve.}



$$\frac{v_1}{R_1} = I_1 - \frac{V_{out}}{R_2 \| R_3}$$

$$V_{out} = \left(I_1 - \frac{v_1}{R_1} \right) \left(\frac{R_2 R_3}{R_2 + R_3} \right)$$